



Family Name

Given Name

Student No.

Signature

THE UNIVERSITY OF NEW SOUTH WALES
School of Electrical Engineering & Telecommunications

FINAL EXAMINATION

Term 1, 2020

ELEC1111
Electrical and Telecommunications Engineering

TIME ALLOWED:	2 hours
TOTAL MARKS:	100
TOTAL NUMBER OF QUESTIONS:	5

THIS EXAM CONTRIBUTES 50% TO THE TOTAL COURSE ASSESSMENT

Reading Time: 10 minutes.

This paper contains 6 pages.

Candidates must **ATTEMPT ALL** questions.

Answer each question in a **separate answer booklet**.

Marks for each question are indicated beside the question.

This paper **MAY NOT** be retained by the candidate.

Print your name, student ID and question number on the front page of each answer book.

Authorised examination materials:

Candidates should use their own UNSW-approved electronic calculators.

This is a closed book examination.

Assumptions made in answering the questions should be stated explicitly.

All answers must be written in ink. Except where they are expressly required, pencils **may only be used** for drawing, sketching or graphical work.

QUESTION 1 [20 marks]

a. (10 marks) For the circuit shown in Figure 1,

i. (7 marks) Apply mesh analysis and write down the mesh equations using the labels provided. Simplify the equations in the form $ai_1 + bi_2 + ci_3 = d$, where coefficients a, b, c and d can be positive or negative.

Note: DO NOT solve the equations.

ii. (3 marks) Given the values of mesh currents as $i_1 = 3.5\text{ A}$, $i_2 = -0.5\text{ A}$ and $i_3 = 2.5\text{ A}$ find the power in the dependent voltage source.

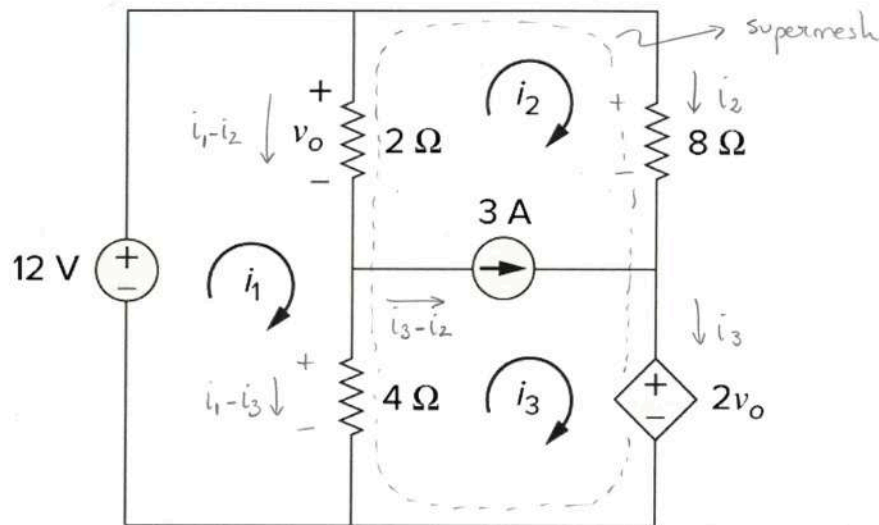


Figure 1

i)

$$\text{KVL @ mesh 1: } -12 + 2(i_1 - i_2) + 4(i_1 - i_3) = 0 \quad (1)$$

$$\text{KVL @ supermesh: } -4(i_1 - i_3) - 2(i_1 - i_2) + 8i_2 + 2v_o = 0, \text{ where } v_o = 2(i_1 - i_2) \quad (2)$$

$$\text{Constraint equation: } i_3 - i_2 = 3 \quad (3)$$

We simplify the equations:

$$6i_1 - 2i_2 - 4i_3 = 12 \quad (1)$$

$$-4(i_1 - i_3) - 2(i_1 - i_2) + 8i_2 + 4(i_1 - i_2) = 0 \Rightarrow -2i_1 + 6i_2 + 4i_3 = 0 \quad (2)$$

$$-i_2 + i_3 = 3 \quad (3)$$

Putting them together:

$$\left. \begin{aligned} 6i_1 - 2i_2 - 4i_3 &= 12 \\ -2i_1 + 6i_2 + 4i_3 &= 0 \\ -i_2 + i_3 &= 3 \end{aligned} \right\}$$

ii)

$$P_{ds} = +V_{ds} \times i_{ds} = 2v_o \times i_3 = 2 \times 2(i_1 - i_2) \times i_3 = 4 \times (3.5 + 0.5) \times 2.5 = 40\text{ W}$$

- b. (10 marks) Transistors can serve as amplifiers, producing both current gain and voltage gain. They can be used to furnish a considerable amount of power to devices that convert energy, such as loudspeakers or control motors. Calculate the gain (i.e. v_o/v_s) of the transistor amplifier circuit shown in Figure 2 when $v_s = 2V$.

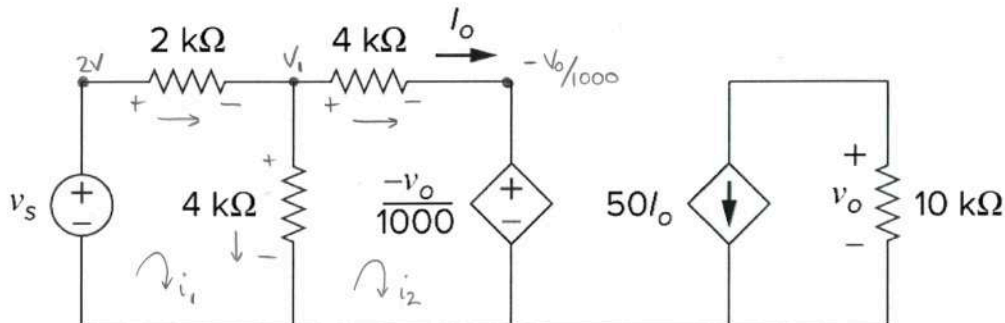


Figure 2

$$V_o = -10K \times 50 I_o$$

We calculate I_o from the left hand side of the circuit:

* Using mesh analysis

$$-2 + 2K i_1 + 4K(i_1 - i_2) = 0$$

$$-4K(i_1 - i_2) + 4K i_2 + \left(\frac{-V_o}{1000}\right) = 0$$

$$\text{where } i_2 = I_o \text{ and } V_o = -500K I_o$$

We simplify the equations:

$$\left. \begin{aligned} 6000 i_1 - 4000 I_o &= 2 \\ -4000 i_1 + 8000 I_o + \frac{500K I_o}{1000} &= 0 \end{aligned} \right\} \begin{aligned} 6000 i_1 - 4000 I_o &= 2 \\ -40 i_1 + 85 I_o &= 0 \end{aligned} \Rightarrow \begin{aligned} 6000 i_1 - 4000 I_o &= 2 \\ -6000 i_1 + 12750 I_o &= 0 \end{aligned}$$

$$8750 I_o = 2$$

$$I_o = 228.57 \mu A$$

From I_o we calculate V_o :

$$V_o = -10K \times 50 I_o = -0.5 \times 10^6 I_o = -0.5 \times 10^6 \times 228.57 \times 10^{-6} = -114.285 V$$

Then, we calculate the gain:

$$\boxed{\frac{V_o}{V_s} = \frac{-114.285}{2} = -57.142}$$

* Using nodal analysis:

$$\frac{2 - V_1}{2k} = \frac{V_1 - \left(\frac{-V_0}{1000}\right)}{4k} + \frac{V_1}{4k}$$

where $V_0 = -500k I_0$ and $I_0 = \frac{V_1 - \left(\frac{-V_0}{1000}\right)}{4k}$, which leads to $\frac{-V_0}{500k} = \frac{V_1 + \frac{V_0}{1000}}{4k}$

We simplify the equations:

$$\left. \begin{aligned} 4 - 2V_1 &= V_1 + \frac{V_0}{1000} + V_1 \\ -V_0 &= 125V_1 + \frac{125V_0}{1000} \end{aligned} \right\} \begin{aligned} \frac{V_0}{1000} &= 4 - 4V_1 \\ -1000V_0 &= 125000V_1 + 125V_0 \end{aligned} \right\} \begin{aligned} 4000V_1 + V_0 &= 4000 \quad (\times (-1125)) \\ 125000V_1 + 1125V_0 &= 0 \end{aligned}$$

↓

$$\begin{aligned} -4500000V_1 - 1125V_0 &= -4500000 \\ 125000V_1 + 1125V_0 &= 0 \end{aligned}$$

$$-4375000V_1 = -4500000$$

$$V_1 = \underline{1.0286V}$$

We calculate V_0 from V_1 :

$$V_0 = 4000 - 4000V_1 = \underline{-114.4V}$$

Then, we calculate the gain:

$$\boxed{\frac{V_0}{V_s} = \frac{-114.4V}{2V} = -57.2}$$

QUESTION 2 [20 marks]

- a. **(8 marks)** A magnetically controlled switch is called a *relay*. A relay is essentially an electromagnetic device used to open or close a switch that controls another circuit (see Figure 3(a)). The coil circuit is an RL circuit like that in Figure 3(b), where R and L are the resistance and inductance of the coil.

A certain relay has a resistance of 200Ω and an inductance of 500 mH . The relay contacts close when the current through the coil reaches 175 mA . What time elapses between the application of 110V to the coil (when S_1 closes at $t = 0$) and contact closure?

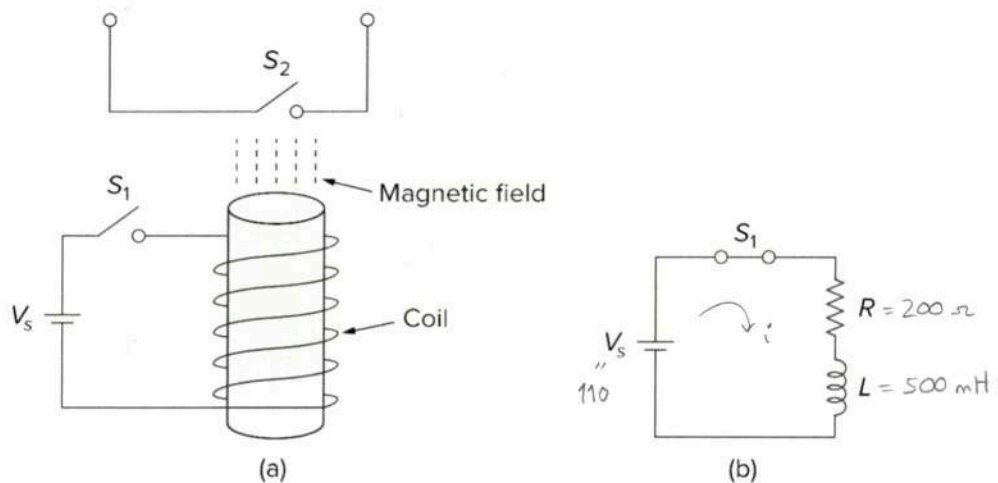


Figure 3


When S_1 closes at $t = 0$ (i.e. $t > 0$) $\Rightarrow$ step response

$$i(t) = i(\infty) + (i(0) - i(\infty))e^{-t/\tau}, \text{ where } \tau = L/R$$

* Calculate $i(0)$:

$$i(0) = 0\text{ A}$$

* Calculate $i(\infty)$:

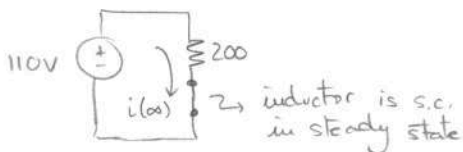

$$i(\infty) = \frac{110}{200} = 0.55\text{ A}$$

* Calculate τ :

$$\tau = L/R = \frac{500\text{ mH}}{200\Omega} = 2.5\text{ ms}$$

* Substituting in the equation: $i(t) = 0.55(1 - e^{-t/0.0025})\text{ A}$

Contacts close when $i(t) = 175\text{ mA}$, so: $0.55(1 - e^{-400t}) = 0.175$

$$+ 0.55e^{-400t} = + 0.375$$

$$e^{-400t} = 0.6818$$

$$+ 400t = + 0.383$$

$$t = 957.5\text{ }\mu\text{s}$$

b. (12 marks) For the circuit shown in Figure 4,

- (2.5 marks) Find the initial voltage $v(0^-)$ across the capacitor under steady-state condition.
- (2.5 marks) Find the final voltage $v(\infty)$ across the capacitor under steady-state condition.
- (4 marks) Derive an expression for the voltage of the capacitor $v(t)$ for all time (i.e., for both $t < 0$ and $t \geq 0$).
- (3 marks) Derive an expression for the current $i(t)$ for $t \geq 0$.



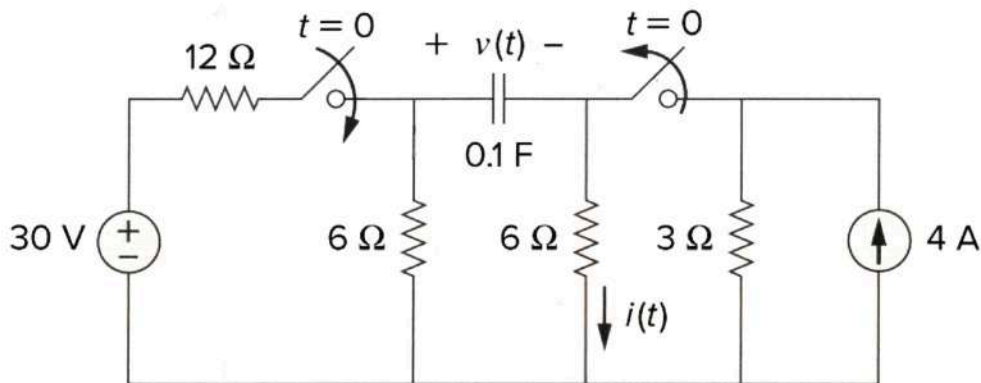


Figure 4

i) $t < 0$

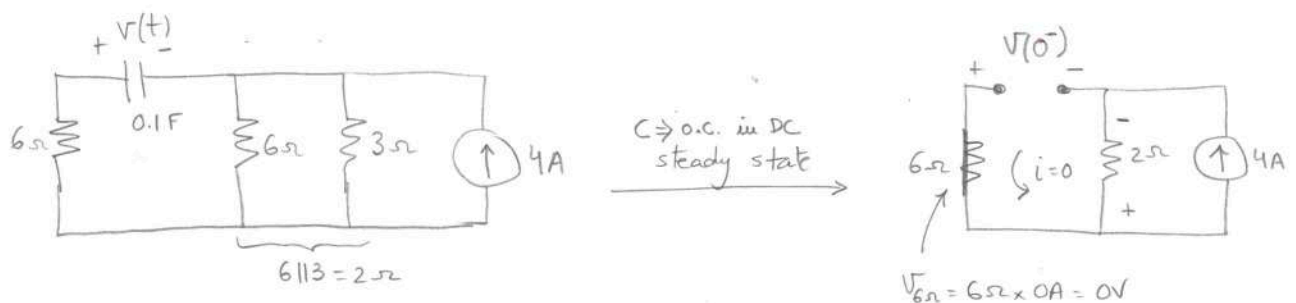

ii) $t > 0$

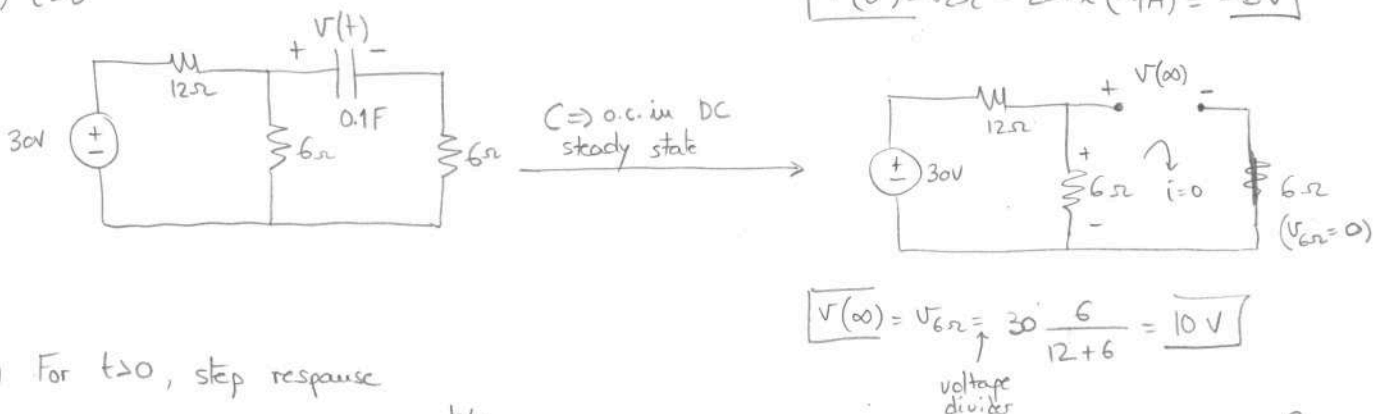


iii) For $t > 0$, step response

$$v(t) = v(\infty) + (v(0^-) - v(\infty)) e^{-t/\tau} \quad \text{where } \tau = R_{th} \times C$$

$$v(t) = 10 + (-8 - 10) e^{-t/\tau} = 10 - 18 e^{-t/\tau}$$

We calculate τ from circuit @ $t > 0$
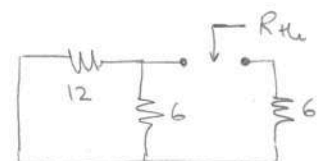
$$R_{th} = (12 \parallel 6) + 6 = 4 + 6 = 10\Omega \Rightarrow \tau = R_{th} \times C = 10 \times 0.1 = 1s$$



We substitute in the step response equation:

$$v(t) = 10 - 18e^{-t/\tau} = 10 - 18e^{-t} \text{ V for } t \geq 0$$

Including the info for $t < 0$:

$$\begin{cases} v(t) = -8 \text{ V}, & t < 0 \\ v(t) = 10 - 18e^{-t} \text{ V}, & t \geq 0 \end{cases}$$

iv) $i = C \frac{dv}{dt}$

$$i(t) = 0.1 \times \frac{d}{dt} (10 - 18e^{-t}) = 0.1 \times (-18) e^{-t} / (-1) = 1.8 e^{-t}$$

QUESTION 3 [25 marks]

a. (12 marks) In the circuit of Figure 5, calculate the voltage v_o if $v_s = 2V$.

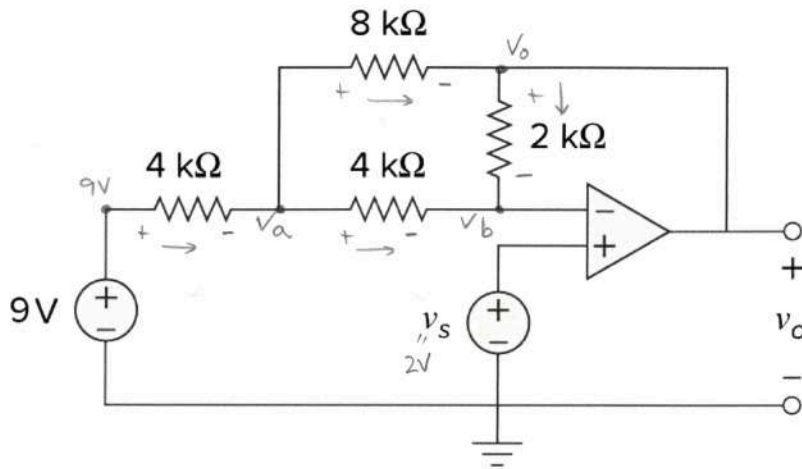


Figure 5

KCL @ node a:

$$\frac{9 - V_a}{4k} = \frac{V_a - V_o}{8k} + \frac{V_a - V_b}{4k} \quad (1)$$

KCL @ node b:

$$\frac{V_a - V_b}{4k} + \frac{V_o - V_b}{2k} = 0 \quad (2)$$

Also, $V_b = V^- = V^+ = 2V$

We substitute and simplify:

From (2):

$$\frac{V_a}{4} - \frac{1}{2} + \frac{V_o}{2} - 1 = 0 ; \quad V_a - 2 + 2V_o - 4 = 0$$

Substituting in (1): $V_a = 6 - 2V_o$

$$\begin{aligned} \times 8 \quad & \frac{9}{4} - \left(\frac{1}{4} + \frac{1}{8} + \frac{1}{4}\right)(6 - 2V_o) + \frac{V_o}{8} + \frac{1}{2} = 0 \\ & 18 - 5(6 - 2V_o) + V_o + 4 = 0 \end{aligned}$$

$$18 - 30 + 10V_o + V_o + 4 = 0$$

$$-8 + 11V_o = 0 \Rightarrow \boxed{V_o = \frac{8}{11} = 0.727 V}$$

- b. (13 marks)** Woofers or bass speakers are used to reproduce low frequency sounds, typically from 40 Hz up to 500 Hz. The circuit in Figure 6 is used to set up a woofer speaker using a Sallen-Key low pass filter. If V_{in} is an AC signal with RMS value $V_{in_{RMS}} = 500 \text{ mV}$ and frequency $f = 500 \text{ Hz}$, calculate:

- (2 marks)** Input voltage V_{in} as a function of time and then as a phasor.
- (8 marks)** Output voltage V_o of the Sallen-Key low pass filter.
- (3 marks)** Average power absorbed by the woofer speaker (i.e. 8Ω resistor).

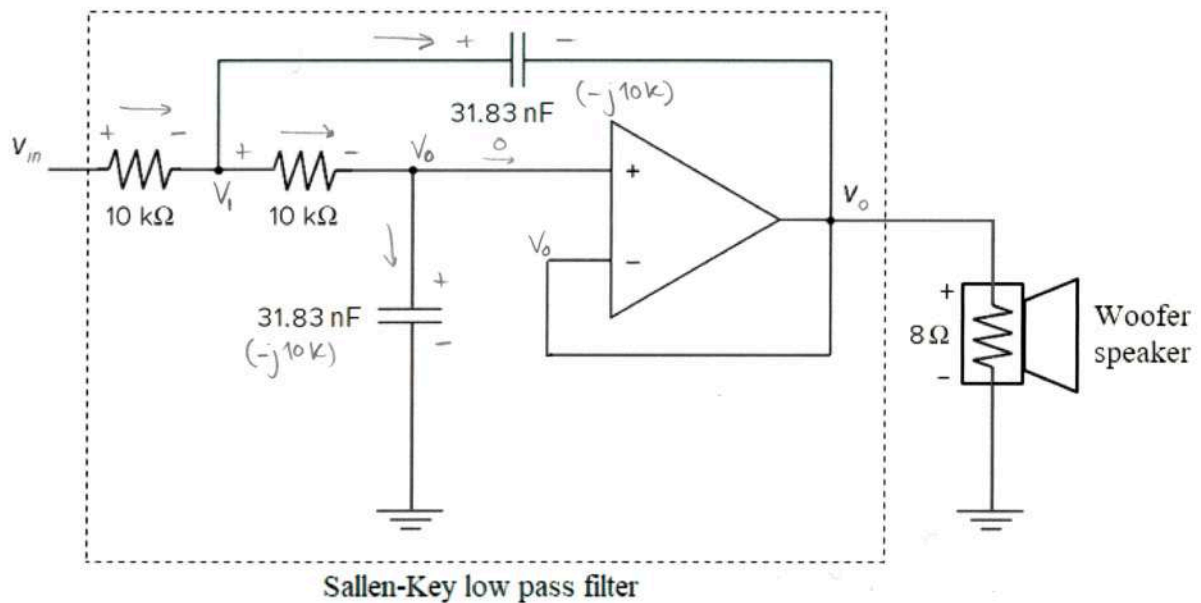


Figure 6

i) $V_{in_{RMS}} = \frac{V_{in_m}}{\sqrt{2}} \Rightarrow V_{in_m} = \sqrt{2} \times 500 \text{ mV} = 0.707 \text{ V}$

$$V_{in} = 0.707 \cos(1000\pi t) \text{ V} \Rightarrow V_{in} = 0.707 \angle 0^\circ \text{ V}$$

- ii) First, calculate the impedance of the capacitor:

$$Z_{C1} = Z_{C2} = -j \frac{1}{\omega C} = -j \frac{1}{2\pi \times 500 \times 31.83 \times 10^{-9}} = -j 10k$$

Then, do nodal analysis to find V_o :

$$\text{KCL @ node } V_1: \frac{V_{in} - V_1}{10k} = \frac{V_1 - V_o}{10k} + \frac{V_1 - V_o}{-j10k} \Rightarrow -jV_{in} + jV_1 = -jV_1 + jV_o + V_1 - V_o$$

$$\text{KCL @ node } V_o: \frac{V_1 - V_o}{10k} = \frac{V_o}{-j10k} \Rightarrow -jV_1 + jV_o = V_o$$

Substitute V_{in} and simplify

$$\begin{aligned} -j0.707 + (-1+2j)V_1 &= (-1+j)V_o \\ -jV_1 &= (1-j)V_o \end{aligned}$$

$$-j0.707 + (-1+j)V_1 = 0$$

$$V_1 = \frac{j0.707}{-1+j} = \frac{0.707 \angle 90^\circ}{1.414 \angle 135^\circ} = 0.5 \angle -45^\circ$$

$$V_o = \frac{-jV_1}{(1-j)} = \frac{0.5 \angle -135^\circ}{1.414 \angle -45^\circ} = 0.354 \angle -90^\circ \text{ V}$$

- iii)

$$P_{avg_{8\Omega}} = \frac{1}{2} \frac{|V_o|^2}{8\Omega} = \frac{1}{2} \frac{0.354^2}{8} = 7.83 \text{ mW}$$

QUESTION 4 [25 marks]

- a. **(10 marks)** A phase shifting circuit is often employed to correct an undesirable phase shift already present in a circuit or to produce special desired effects. The circuit in Figure 7 shows an RC phase shift circuit with a certain lagging phase shift. Calculate the value of V_o as a function of V_i and state the phase shift introduced by the circuit.


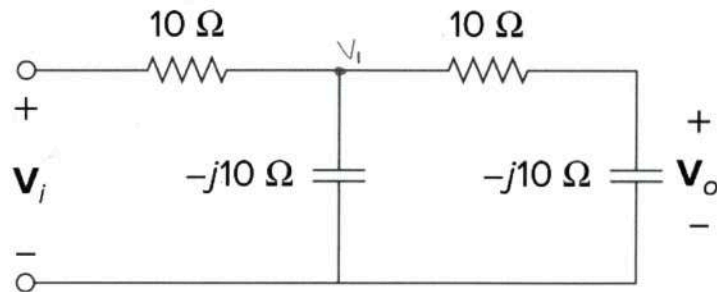


Figure 7

Calculate V_1 using voltage division:

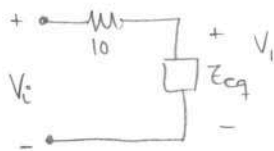

$$V_1 = V_i \frac{Z_{eq}}{10 + Z_{eq}}, \text{ where } Z_{eq} = -j10 \parallel (10 - j10)$$

$$Z_{eq} = \frac{-j10(10 - j10)}{-j10 + 10 - j10} = \frac{-j(10 - j10)}{1 - 2j} = \frac{-10 - j10}{1 - j2} = \frac{14.142 \angle -135^\circ}{2.23 \angle -63.43^\circ} = 6.342 \angle -71.57^\circ = 2 - j6$$

$$V_1 = V_i \frac{6.342 \angle -71.57^\circ}{12 - j6} = V_i \frac{6.342 \angle -71.57^\circ}{13.42 \angle -26.56^\circ} = 0.472 \angle -45^\circ \times V_i$$

Then, calculate V_o from V_1 using voltage division again:

$$V_o = V_1 \frac{-j10}{10 - j10} = V_i \times 0.472 \angle -45^\circ \times \frac{10 \angle -90^\circ}{14.14 \angle -45^\circ} = 0.334 \angle -90^\circ \times V_i$$

b. (15 marks) For the circuit shown in Figure 8,

i. (5 marks) Calculate the load impedance Z_L that will ensure the maximum transfer of power from the circuit to the load.

ii. (10 marks) Find the maximum average power received by Z_L .


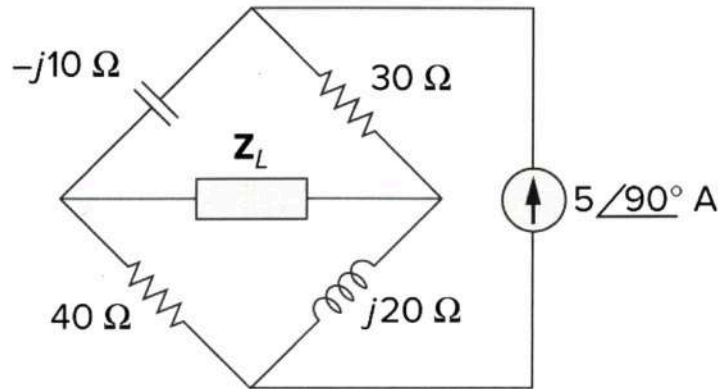


Figure 8

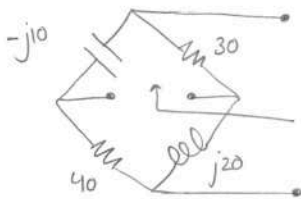i) $Z_L = Z_{th}^*$

We turn off current source and calculate equivalent impedance to calculate Z_{th} :




$$Z_{th} = (30 - j10) \parallel (40 + j20) = \frac{(30 - j10)(40 + j20)}{30 - j10 + 40 + j20} = \frac{1200 + j600 - j400 + 200}{70 + j10}$$

$$= \frac{1400 + j200}{70 + j10} = 20 \Omega$$

ii) $P_{max} = \frac{|V_{th}|^2}{8 R_{th}}$

$Z_L = Z_{th}^* = 20 \Omega$

We calculate V_{th} :

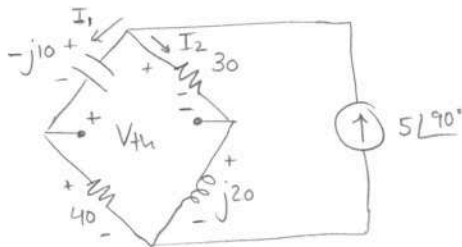

Calculate I_1 and I_2 using current division:

$$I_1 = 5 \angle 90^\circ \frac{30 + j20}{30 + j20 + 40 - j10} = 5 \angle 90^\circ \frac{30 + j20}{70 + j10} = -1.1 + j2.3 = 2.55 \angle 115.56^\circ \text{ A}$$

$$I_2 = 5 \angle 90^\circ \frac{40 - j10}{70 + j10} = 1.1 + j2.7 = 2.92 \angle 67.83^\circ \text{ A}$$

Calculate V_{th} doing KVL in the upper mesh:

$$-j10 I_1 + V_{th} - 30 I_2 = 0 \Rightarrow V_{th} = j10 I_1 + 30 I_2$$

$$V_{th} = 10 \angle 90^\circ \times 2.55 \angle 115.56^\circ + 30 \times 2.92 \angle 67.83^\circ = 25.5 \angle -154.44^\circ + 87.6 \angle 67.83^\circ = (-23 - j11) + (33.06 + j81.12) = 10.06 + j70.12 = 70.84 \angle 81.84^\circ$$

Then calculate P_{max} :

$P_{max} = \frac{70.84^2}{8 \times 20} = 31.36 \text{ W}$

IGNORE THIS QUESTION

QUESTION 5 [10 marks]

a. (4 marks) Simplify the following logical expression:

$$Z = \overline{A + \overline{B}C + \overline{C}}$$

b. (6 marks) Consider the logical diagram shown in Figure 9.

i. (1.5 marks) Derive the logical expression for Y.

ii. (4.5 marks) Construct the truth table relating Y to inputs A, B and C.

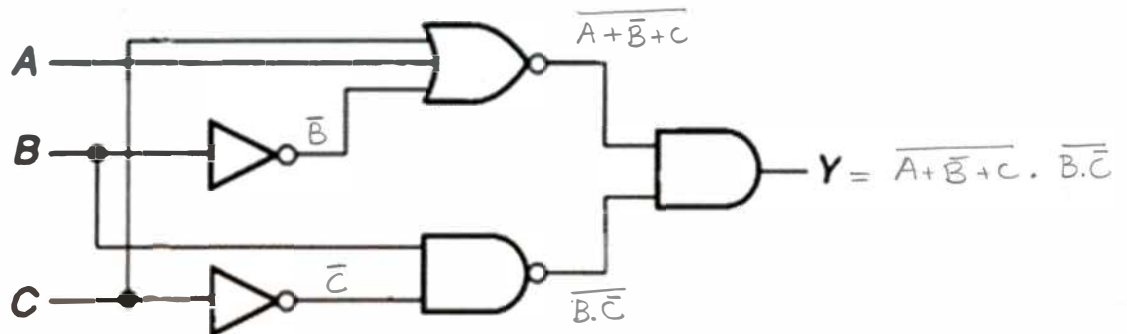


Figure 9

a)

$$Z = \overline{A + \overline{B}C + \overline{C}} = \overline{A} \cdot \overline{\overline{B}C} \cdot \overline{\overline{C}} = \overline{A} \cdot (\overline{\overline{B}} + \overline{\overline{C}}) \cdot C = \overline{A} \cdot B \cdot C + \overline{A} \cdot \overline{C} \cdot C = \overline{A}BC + 0 = \overline{A}BC$$

$\uparrow$ De Morgan's $\uparrow$ De Morgan's $\uparrow$ Distributive law $\uparrow$ $\overline{C}C = 0$ $\uparrow$ $X+0 = X$
 $\overline{\overline{C}} = C$ $\overline{\overline{B}} = B$ $\overline{C}C = 0$ $X \cdot 0 = 0$

b)

i) $Y = \overline{A + \overline{B}C} \cdot \overline{B.C}$ (see diagram for intermediate steps)

ii)

A	B	C	$\overline{B}$	$\overline{C}$	$A + \overline{B}C$	$\overline{A + \overline{B}C}$	$B.C$	$\overline{B.C}$	Y
0	0	0	1	1	1	0	0	1	0
0	0	1	1	0	1	0	0	1	0
0	1	0	0	1	0	1	1	0	0
0	1	1	0	0	1	0	0	1	0
1	0	0	1	1	1	0	0	1	0
1	0	1	1	0	1	0	0	1	0
1	1	0	0	1	1	0	1	0	0
1	1	1	0	0	1	0	0	1	0