

QUESTION 1 [25 marks]

(i) [12 marks] For the circuit shown in Figure 1,

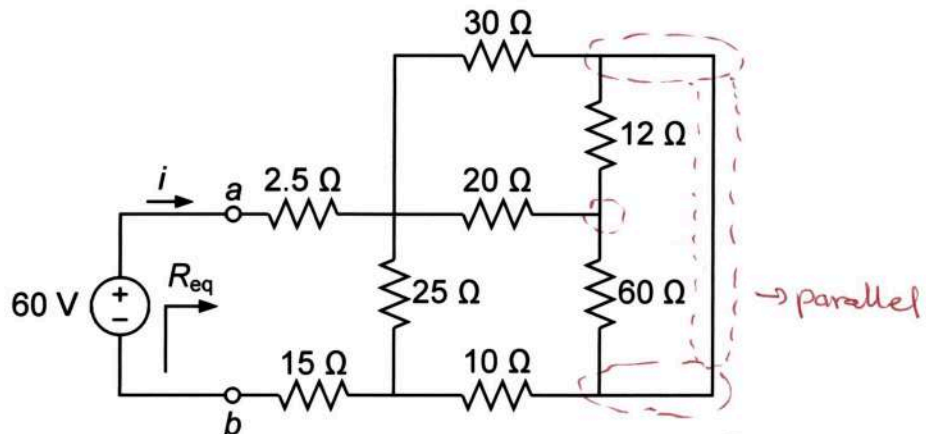
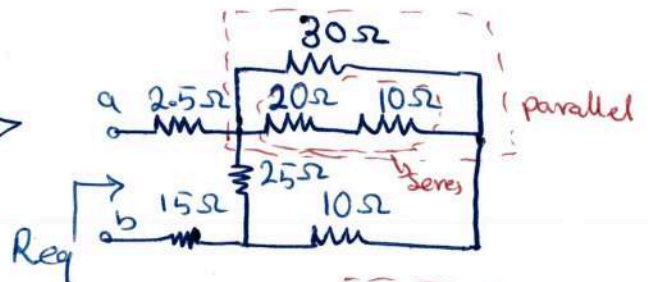
a. (10 marks) Calculate the equivalent resistance R_{eq} as seen from terminals a-b.b. (2 marks) Find the current i through the network using the result of part (a).


Figure 1

$$a) \quad 12\Omega \parallel 60\Omega = \frac{12 \times 60}{12 + 60} = 10\Omega \Rightarrow$$




$$20 + 10 = 30 \rightarrow 30 \parallel 30 = \frac{30 \times 30}{30 + 30} = 15\Omega \Rightarrow$$

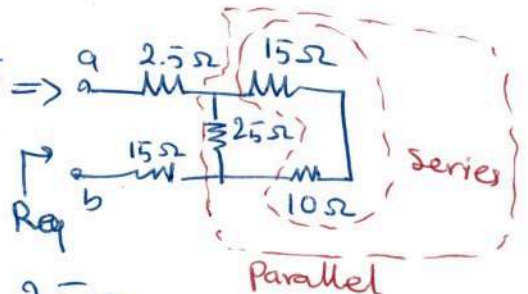
$$\Rightarrow 15 + 10 = 25 \rightarrow 25 \parallel 25 = \frac{25 \times 25}{25 + 25} = 12.5\Omega$$


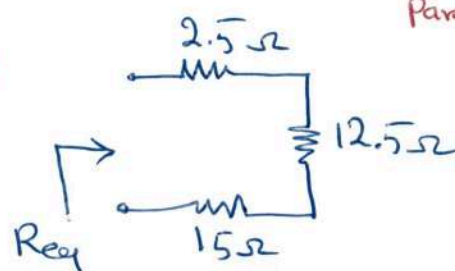
$$\Rightarrow R_{eq} = 2.5 + 12.5 + 15 = 30\Omega$$



b) Equivalent circuit

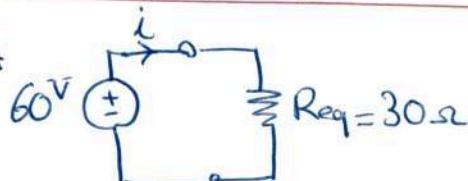


$$i = \frac{V}{R} = \frac{60}{R_{eq}} = \frac{60}{30} = 2A$$

QUESTION 1 [25 marks] Continued

(ii) [13 marks] For the circuit shown in Figure 2,

- a. (10 marks) Calculate all the powers absorbed and/or supplied by the elements.
 b. (3 marks), Verify the law of conservation of energy.

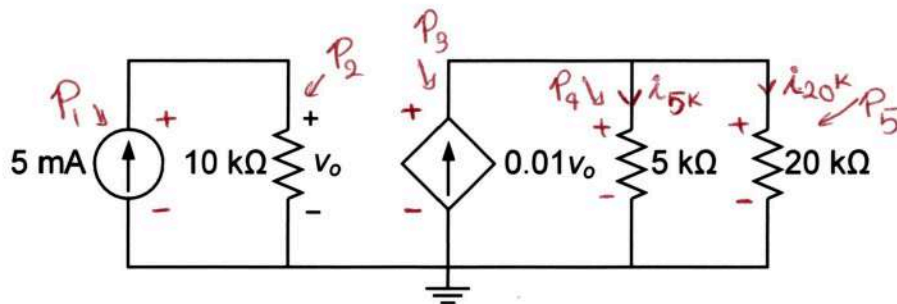Figure 2

a) $P = V \cdot i = \frac{V^2}{R} = R i^2$ (passive sign convention)

$$V_o = 10^k \times 5^m = \boxed{50V} \quad \leftarrow \text{Ohm's Law}$$

$$i_{5k} = \frac{20^k}{5^k + 20^k} \times 0.01 V_o = \frac{20 \times 0.5}{25} = \boxed{0.4A} \quad \leftarrow \text{Current division}$$

$$i_{20k} = 0.01 V_o - i_{5k} = 0.5 - 0.4 = \boxed{0.1A} \quad \leftarrow \text{KCL}$$

$$V_{5k} = V_{20k} = V_{\text{dependent source}} = 5^k \times 0.4A = \boxed{2^kV = 2000V}$$

Now find powers of each element

* 5mA Source: $P_1 = V_o \times 5^m = 50^V \times 5^m = 250 \text{ mW} = 0.25 \text{ W}$ Supplied (passive sign convention for active elements)

* 10-kΩ resistor: $P_2 = \frac{V_o^2}{10^k} = 10^k \times (5^m)^2 = 250 \text{ mW} = 0.25 \text{ W}$ absorbed

* 0.01V_o Source: $P_3 = V_{5k} \times 0.01 V_o = 2000 \times 0.01 \times 50 = 1000 \text{ W} = 1 \text{ kW}$ Supplied


* 5-kΩ resistor: $P_4 = 5^k \times (i_{5k})^2 = 5^k \times (0.4)^2 = 800 \text{ W}$ absorbed

* 20-kΩ resistor: $P_5 = 20^k \times (i_{20k})^2 = 20^k \times (0.1)^2 = 200 \text{ W}$ absorbed

b) Conservation of energy $\rightarrow \sum P_{\text{supplied}} = \sum P_{\text{absorbed}}$
 $\Rightarrow 0.25^W + 1000^W = 0.25^W + 800^W + 200^W \Rightarrow 1000.25 = 1000.25$
Confirmed

QUESTION 2 [30 marks]**(i) [14 marks]** For the circuit shown in Figure 3,**a. (10 marks)** Apply nodal analysis and show that the nodal equations are given as below,

$$\begin{cases} 9v_1 - 5v_2 = 120 \\ v_1 - 5v_2 = -40 \end{cases}$$

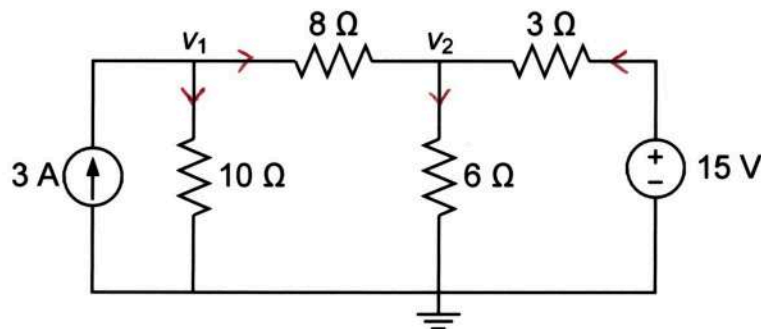b. (4 marks) Given the values of node voltages as $v_1 = 20$ V and $v_2 = 12$ V, calculate the total power supplied by the sources.**Figure 3****a)**

$$\text{KCL@}v_1: 3 = \frac{v_1}{10} + \frac{v_1 - v_2}{8} \xrightarrow{\times 40} 120 = 4v_1 + 5v_1 - 5v_2$$

$$\Rightarrow \boxed{9v_1 - 5v_2 = 120}$$

$$\text{KCL@}v_2: \frac{v_1 - v_2}{8} + \frac{15 - v_2}{3} = \frac{v_2}{6} \xrightarrow{\times 24} 3v_1 - 3v_2 + 120 - 8v_2 = 4v_2$$

$$\Rightarrow 3v_1 - 15v_2 = -120 \xrightarrow{\times \frac{1}{3}} \boxed{v_1 - 5v_2 = -40}$$


$$\text{b) } P_{3A} = v_1 \times 3 = 20 \times 3 = 60 \text{ W supplied}$$

$$P_{15V} = 15 \times \left(\frac{15 - v_2}{3} \right) = 5 \times (15 - 12) = 15 \text{ W supplied}$$

$$\Rightarrow P_{\text{Total}} = 60 + 15 = \boxed{75 \text{ W}} \text{ supplied}$$

QUESTION 2 [30 marks] Continued**(ii) [16 marks]** For the circuit shown in Figure 4,**a. (12 marks)** Apply mesh analysis and show that the mesh equations are given as below,

$$\begin{cases} i_1 + 3i_2 - 2i_3 = 8 \\ i_1 + i_2 - 4i_3 = -1 \\ i_1 - i_2 = -4 \end{cases}$$

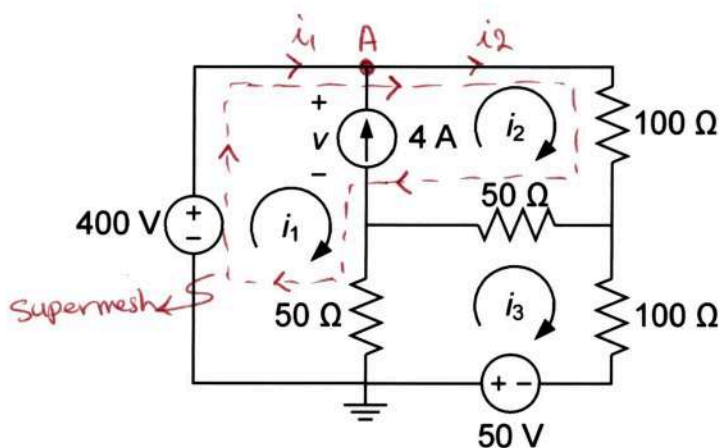b. (4 marks) Given the values of mesh currents as $i_1 = -0.5$ A, $i_2 = 3.5$ A, and $i_3 = 1$ A, find the voltage v across 4-A current source.**Figure 4****a) * KVL in Supermesh:**

$$-400 + 100i_2 + 50(i_2 - i_3) + 50(i_1 - i_3) = 0$$

$$\xrightarrow{\times 50} -8 + 2i_2 + i_2 - i_3 + i_1 - i_3 = 0$$

$$\Rightarrow i_1 + 3i_2 - 2i_3 = 8$$

(Polarities are chosen based on passive sign convention for each KVL)

(direction of currents in shared branches are chosen based on the mesh for which KVL is written)

$$* \text{KVL in mesh 3: } -50 + 50(i_3 - i_1) + 50(i_3 - i_2) + 100i_3 = 0$$

$$\xrightarrow{\times 50} -1 - i_1 + i_3 - i_2 + i_3 + 2i_3 = 0 \Rightarrow i_1 + i_2 - 4i_3 = -1$$

$$* \text{KCL @ node A: } i_1 + 4 = i_2 \Rightarrow i_1 - i_2 = -4$$


b) * KVL in mesh 1: $v_1 + 50(i_1 - i_3) - 400 = 0$

$$\xrightarrow{\substack{i_1 = -0.5 \text{ A} \\ i_3 = 1 \text{ A}}} v = 50(1 + 0.5) + 400 = 475 \text{ V}$$

QUESTION 3 [25 marks]

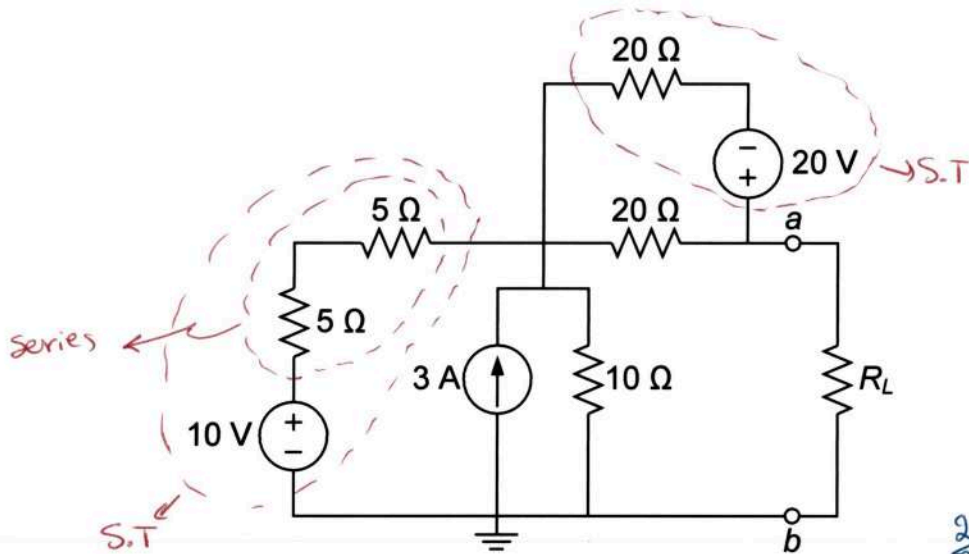
(i) [15 marks] In the circuit of Figure 5,

- [12 marks] Use only **source transformation** to reduce the circuit into a single resistor in series with a single voltage source as seen from terminals a - b , and then determine Thevenin voltage V_{Th} and Thevenin resistance R_{Th} at the terminals a - b .
- [3 marks] Find the value of load resistance R_L for maximum power transfer, and then calculate the maximum power that can be delivered to R_L .



a) 2 source transformations (S.T.s) Figure 5
 $5 + 5 = 10\Omega$



$$i_s = \frac{V_s}{R}$$

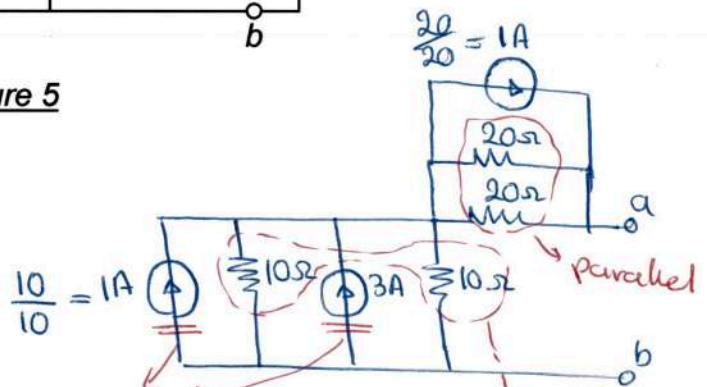

$$10 \parallel 10 = \frac{10 \times 10}{10 + 10} = 5\Omega$$

$$20 \parallel 20 = \frac{20 \times 20}{20 + 20} = 10\Omega$$

$$1A + 3A = 4A$$

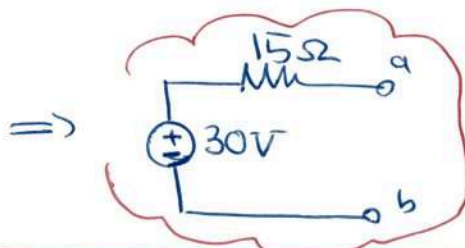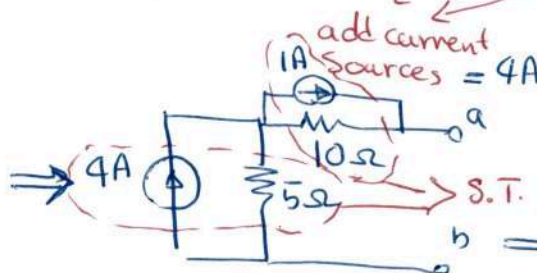

$$\Rightarrow V_{Th} = 30V$$

$$R_{Th} = 15\Omega$$

b) $R_L = R_{Th} = 15\Omega$ for max power transfer

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{30^2}{4 \times 15} = 15W$$

QUESTION 3 [25 marks] Continued

- (ii) [10 marks] For the circuit shown in Figure 6, obtain the Norton equivalent circuit as seen from terminal a-b and draw the Norton equivalent circuit.


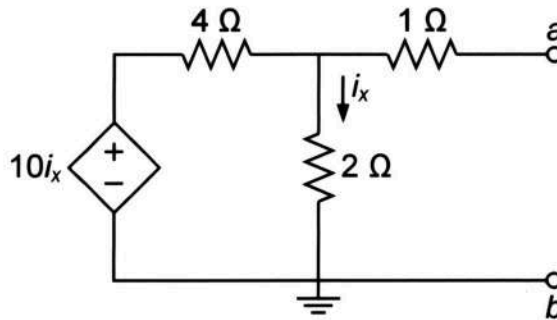


Figure 6

$I_N = 0A$ → No independent source

For $R_N = R_{eq}$, attach an external source

Method 1: Voltage Source

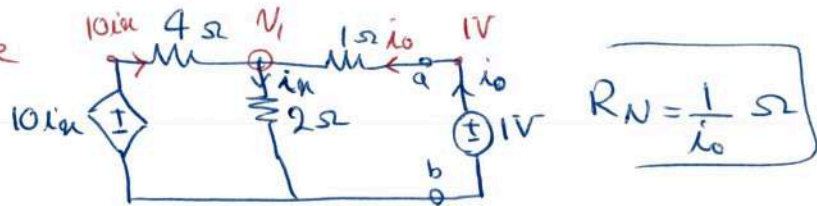

$R_N = \frac{1}{i_0} \Omega$

Nodal analysis:


Find V_1 then find i_0 to find R_N

$$\begin{cases} \frac{10i_x - V_1}{4} + i_0 = \frac{V_1}{2} \\ i_0 = \frac{1 - V_1}{1}, i_x = \frac{V_1}{2} \end{cases} \Rightarrow \frac{5V_1 - V_1}{4} + 1 - V_1 = \frac{V_1}{2}$$

$\times \frac{1}{4} \rightarrow 4V_1 + 4 - 4V_1 = 2V_1 \Rightarrow V_1 = 2V$ (I) $i_0 = \frac{1 - 2}{1} = -1A$

$\Rightarrow R_N = -1\Omega = \frac{1}{-1}$

Method 2: Current Source

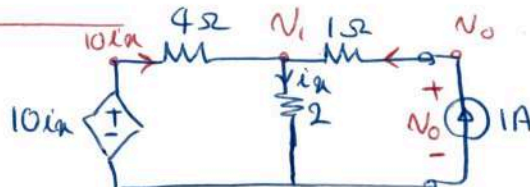

$R_N = \frac{V_0}{1} \Omega$

Nodal analysis:


Find V_1 then find V_0 to find R_N

$$\begin{cases} \frac{10i_x - V_1}{4} + 1 = \frac{V_1}{2} \\ i_x = \frac{V_1}{2}, \frac{V_0 - V_1}{1} = 1 \end{cases} \Rightarrow \frac{5V_1 - V_1}{4} + 1 = \frac{V_1}{2} \times 4, 4V_1 + 4 = 2V_1$$

$$= V_1 = -2V$$
 (I) $V_0 = 1 + V_1 = -1V$


$\Rightarrow R_N = -1\Omega = \frac{-1}{1}$

* Norton equivalent circuit

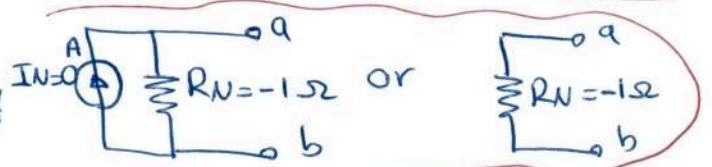

QUESTION 4 [20 marks]

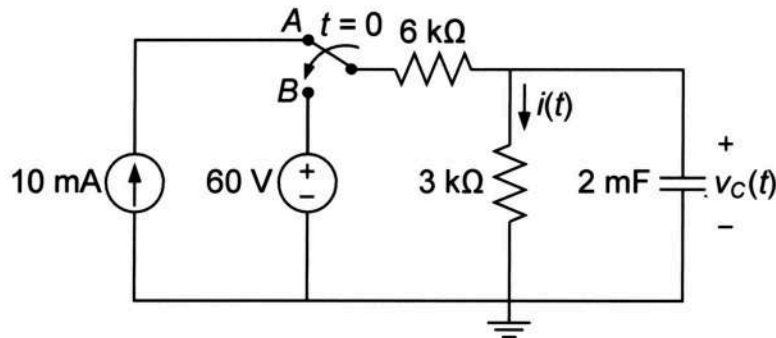- (i) **[8 marks]** In circuit shown in Figure 7, the switch has been in position A for a long time. At $t = 0$, the switch moves to position B.
- (4 marks)** Find the voltage $v_C(t)$ across the capacitor immediately after the switch changes to position B, $v_C(0^+)$, and its final voltage when $t \rightarrow \infty$, $v_C(\infty)$.
 - (3 marks)** Derive an expression for the capacitor voltage $v_C(t)$ for $t > 0$.
 - (1 marks)** Find the current $i(t)$ through 3-k Ω resistor for $t > 0$.




a) * for $t < 0$

Switch is at A

and $v_C(0^+) = v_C(0^-)$ No sudden change in $v_C(t)$


Figure 7

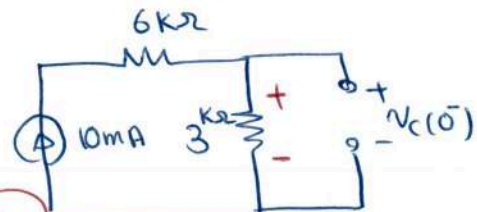

$$\Rightarrow v_C(0^-) = v_{3k\Omega} = 3k \times 10^{-3} = 30V = v_C(0^+)$$

* for $t > 0$

Switch is at B
 $t \rightarrow \infty$

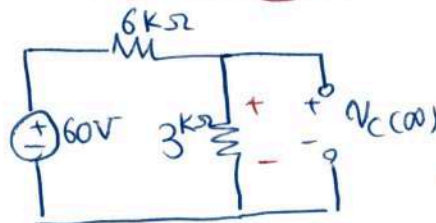


$$v_C(\infty) = \frac{3k}{6k + 3k} \times 60V = 20V$$

$$b) v_C(t) = v_C(\infty) + [v_C(0^+) - v_C(\infty)]e^{-t/\tau} \quad t > 0$$

$$\tau = R_{Th}\hat{C} \quad t > 0$$
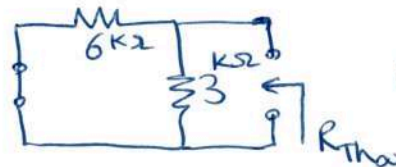
$$\Rightarrow \tau = 2k\Omega \times 2mF = 4s$$



$$R_{Th} = 3k \parallel 6k = \frac{3 \times 6}{3 + 6} = 2k\Omega$$

$$\Rightarrow v_C(t) = 20 + [30 - 20]e^{-t/4} = 20 + 10e^{-t/4} V \quad t > 0$$

$$c) i(t) = \frac{v_{3k}}{3k\Omega} = \frac{v_C(t)}{3k\Omega} \Rightarrow i(t) = \frac{20}{3} + \frac{10}{3}e^{-t/4} mA \quad t > 0$$

3k Ω is parallel with capacitor

QUESTION 4 [20 marks] Continued

(ii) [12 marks] In the circuit of Figure 8, the switch has been closed for a long time before being opened at $t = 0$.

- a. (10 marks) Derive an expression for the inductor current $i_L(t)$ for all time (i.e., for both $t < 0$ and $t > 0$) and sketch $i_L(t)$ as a function of time showing all critical points in the sketch.
- b. (2 marks) Find the total energy stored or released by the inductor for $t \geq 0$, i.e., from $t = 0$ to $t \rightarrow \infty$.


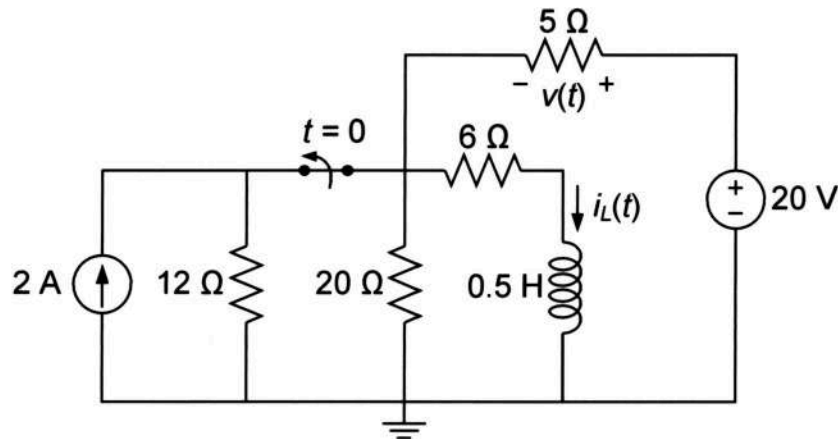



Figure 8

a) * For $t < 0$
Switch is closed

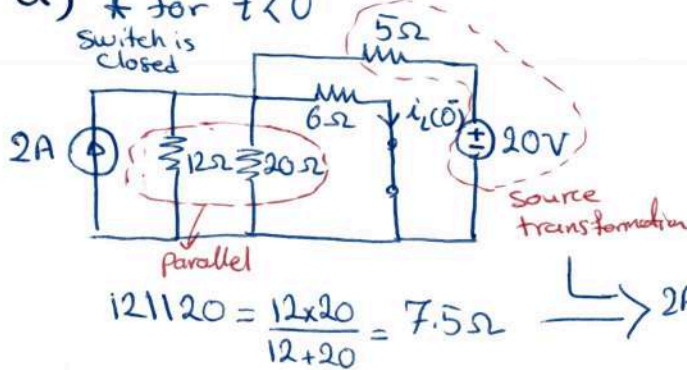


$$i_L(t) = i_L(\infty) + [i_L(0^+) - i_L(\infty)] e^{-\frac{t}{\tau}}$$

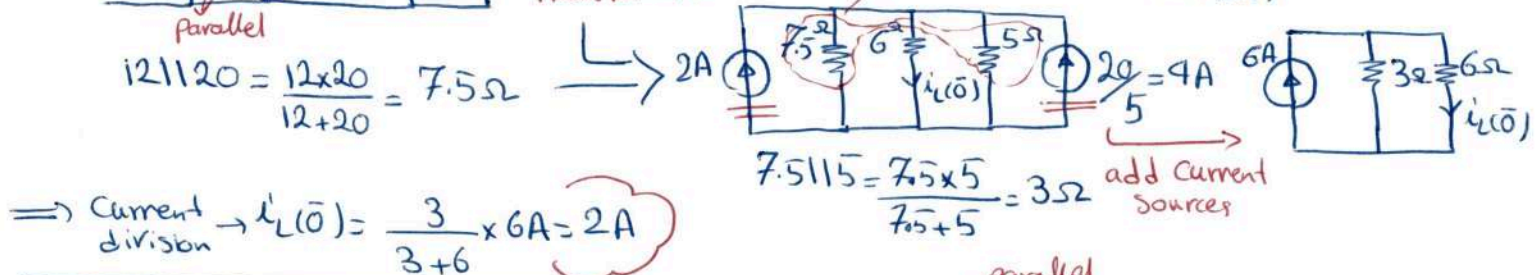$\tau = \frac{L}{R_{Th}}$ and $i_L(0^+) = i_L(0^-)$
no sudden change in $i_L(t)$



* For $t > 0$
Switch is open

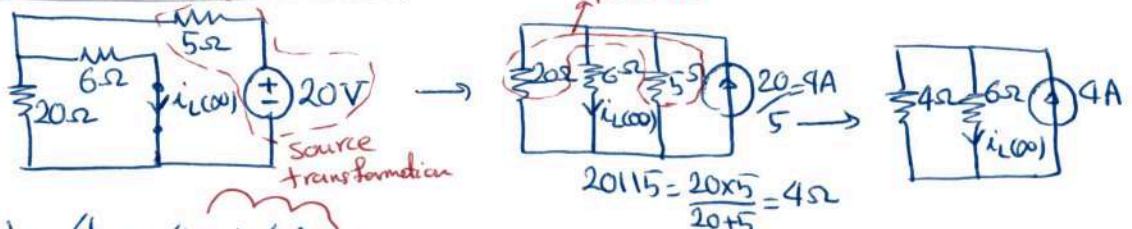

* $\tau = \frac{L}{R_{Th}}$ $t > 0$

Parallel

$$R_{Th} = 6 + 5 \parallel 20 = 6 + \frac{5 \times 20}{5 + 20} = 10 \Omega$$


$$\Rightarrow \tau = \frac{0.5H}{10\Omega} = \frac{1}{20} s = 50ms$$

$$\Rightarrow i_L(t) = 1.6 + (2 - 1.6) e^{-\frac{t}{50ms}} A = 1.6 + 0.4 e^{-\frac{20t}{50}} A$$

$\Rightarrow i_L(t) = \begin{cases} 2A & t < 0 \\ 1.6 + 0.4 e^{-\frac{20t}{50}} A & t \geq 0 \end{cases}$

→ next page

Part (ii)-a Continued

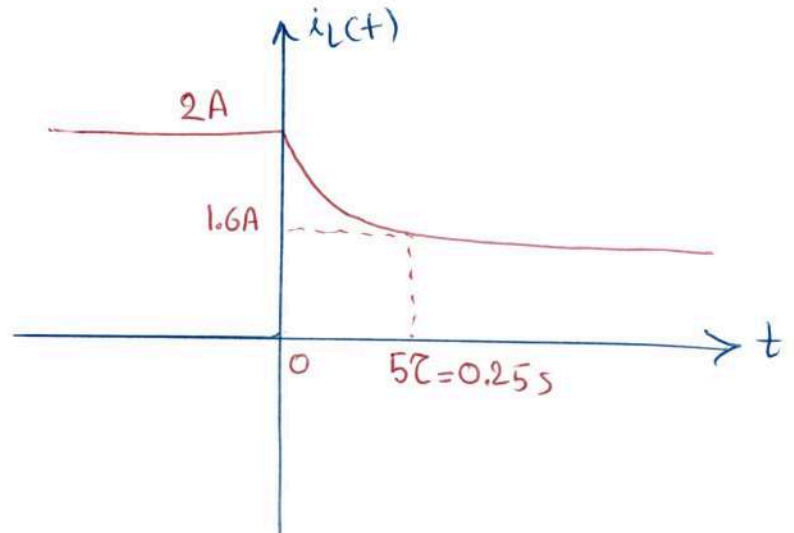

b) $W_\infty = \frac{1}{2} L i_L^2(\infty)$ and $W_0 = \frac{1}{2} L i_L^2(0)$ also $W = \int_{-\infty}^t p(\tau) d\tau = \int_0^\infty L i_L di_L$

$$\Rightarrow W_T = \frac{1}{2} L (i_L^2(\infty) - i_L^2(0))$$

$$= \frac{1}{2} \times 0.5 (1.6^2 - 2^2) = -0.36 \text{ J}$$

$= \frac{1}{2} L (i_L^2(\infty) - i_L^2(0))$
assuming $i_L(-\infty) = i_L(0)$

Thus, the inductor releases 0.36 J from $t=0$ to $t \rightarrow \infty$