

QUESTION 1 [15 marks]

- a. (9 marks) For the circuit shown in Figure 1,
- (6 marks) Calculate the equivalent resistance R_{eq} as seen from terminal $a-b$.
 - (3 marks) Find the voltage drop V_o using the result of part (i).

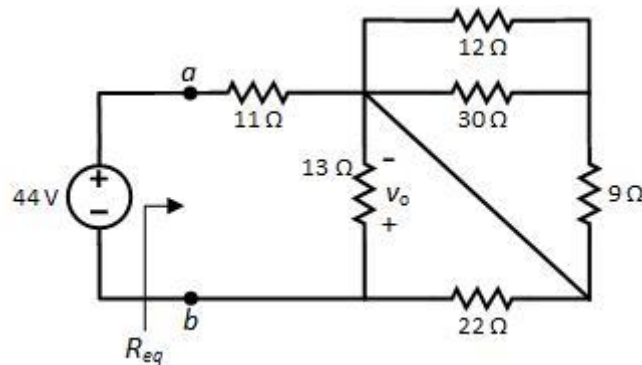


Figure 1

- b. (6 marks) A kitchen has three appliances connected to a 120 V circuit with a 15 A circuit breaker: an 800 W coffee maker, a 1200 W microwave and an 850W toaster, as shown in Figure 2. Which of these appliances can be operated simultaneously without tripping the circuit breaker? Note that a circuit breaker trips when the circuit draws more current than its amperage rating.

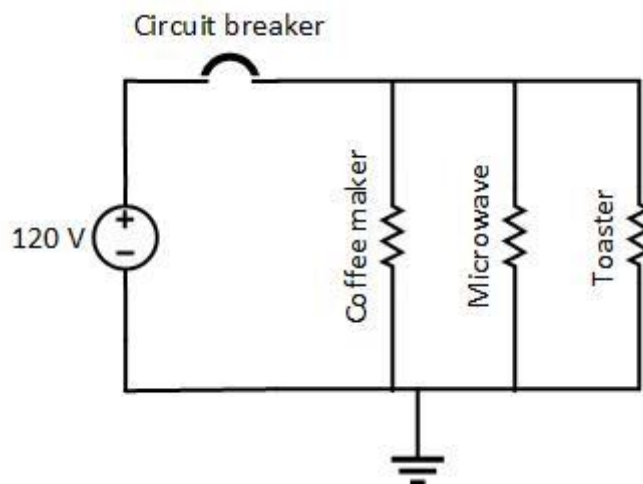


Figure 2

QUESTION 2 [20 marks]

The circuit in Figure 3 represents a solar-powered water fountain. The water fountain is powered by a solar panel during the day, and by a battery at night. The wiring resistances are as shown in Figure 3.

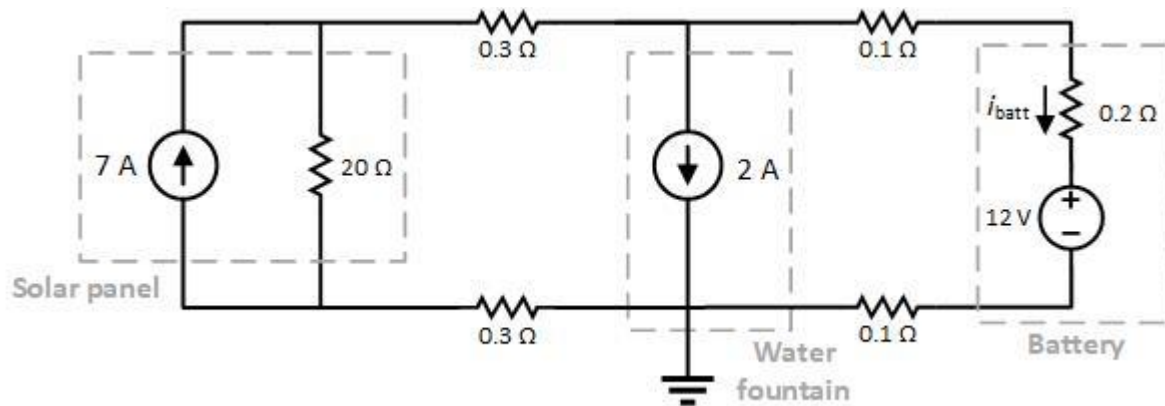


Figure 3

- (10 marks)** Calculate the current through the battery, i_{batt} , during the daytime using mesh analysis.
- (5 marks)** How much total energy will be available from the battery if, during the day, the solar panel delivers its rated current (7A) for 8 hours?
- (5 marks)** Calculate the power of the solar panel.

QUESTION 3 [25 marks]

- a. (12 marks) For the circuit shown in Figure 4, use superposition to calculate the voltage v_x .

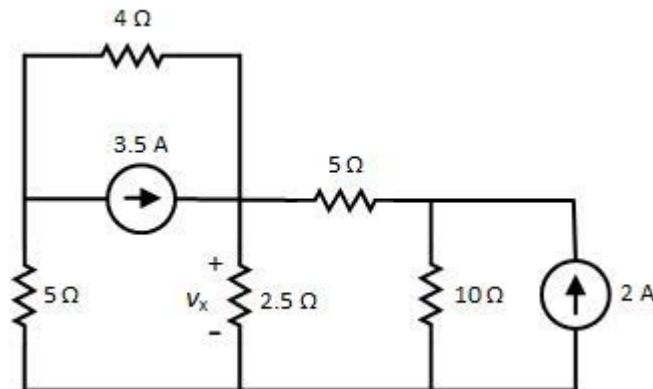


Figure 4

- b. (13 marks) Apply nodal analysis and write down the nodal equations using the labelled node voltages.

Note: Simplify the equations in the form $aV_1 + bV_2 + cV_3 = d$, where coefficients a , b , c and d can be positive or negative numbers, but **DO NOT** solve them.

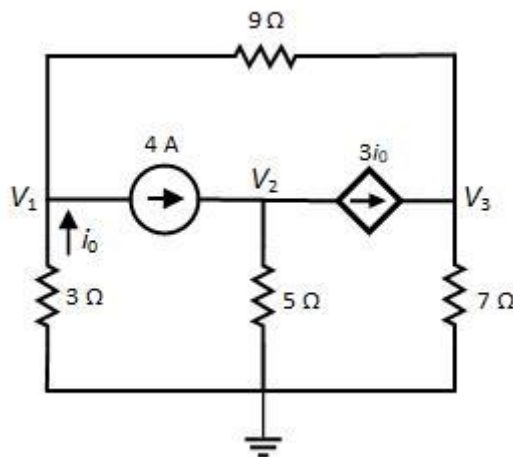


Figure 5

QUESTION 4 [20 marks]

The circuit shown in Figure 6 is being used to power a Christmas lighting system. The lighting system can be modelled as a single resistor connected to terminals a - b .

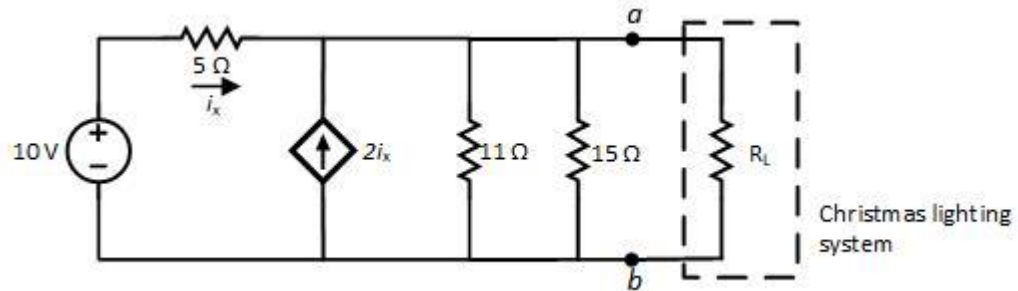


Figure 6

- (9 marks)** Calculate the Thevenin voltage at terminals a - b .
- (9 marks)** Calculate the lighting system resistance that will ensure the maximum transfer of power from the circuit to the lights.
- (2 marks)** Find the maximum power that can be delivered to the lights.

QUESTION 5 [20 marks]

- a. **(8 marks)** Find the currents i_1 and i_2 and voltage v_0 in the circuit of Figure 7 under DC steady-state conditions.

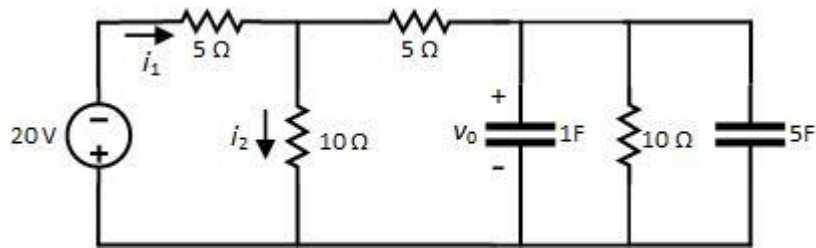


Figure 7

- b. **(12 marks)** In the circuit below, the switch has been open for a long time and it is closed at $t=0$.
- (10 marks)** Find $v(t)$ for $t > 0$.
 - (2 marks)** Calculate $v(t)$ at $t=0.2s$.

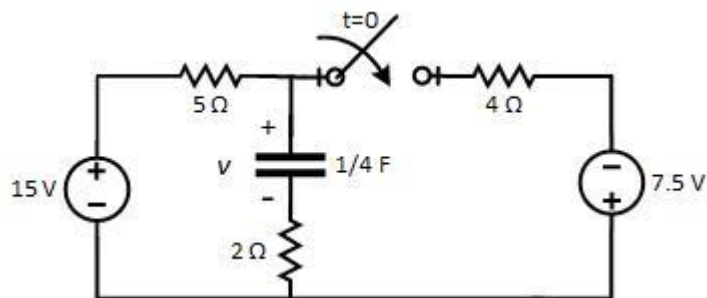


Figure 8