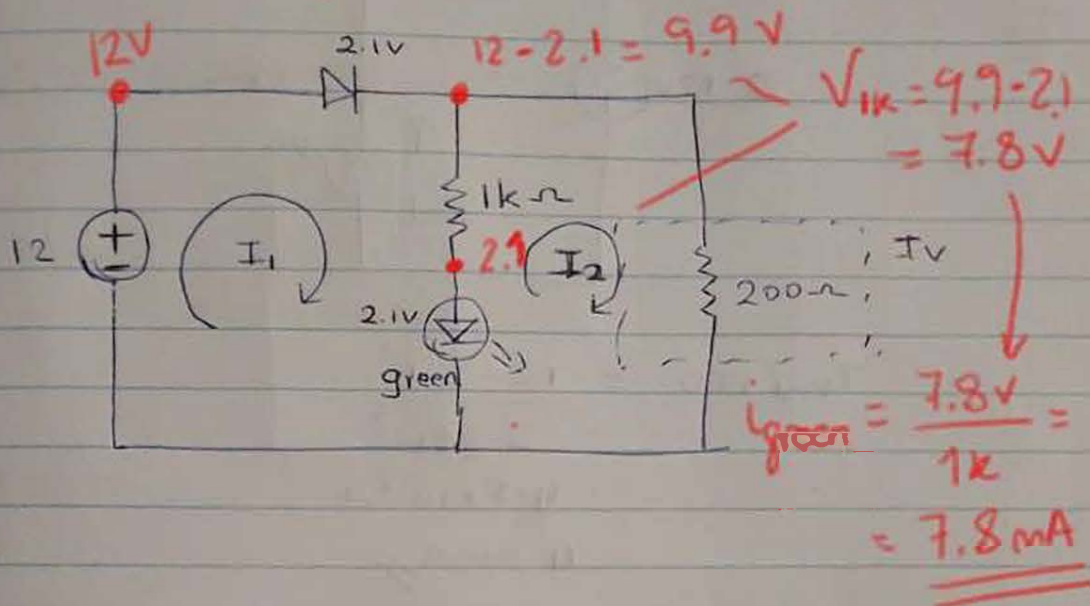


Q.11 V_i

Note (from Inma): Solution in red is much easier, but many students will use mesh, so it is good to have mesh solution too.

(a)

1/ normal



mesh 1

$$-12 + 2.1 + 2.1 + (I_1 - I_2)1000 = 0 \quad \text{--- (1)}$$

mesh 2

$$1200I_2 - 1000I_1 - 2.1 = 0 \quad \text{--- (2)}$$

$$1000I_1 - 1000I_2 = 7.8 \quad \text{--- (1)}$$

$$-1000I_1 + 1200I_2 = 2.1 \quad \text{--- (2)}$$

$$200I_2 = 9.9$$


$$I_2 = 0.0495A //$$

$$I_1 = 0.0573A //$$

$$I_{TV} = I_2 = 0.0495$$


$$I_{green LED} = I_1 - I_2 = 0.0078A //$$

ii/ Fault

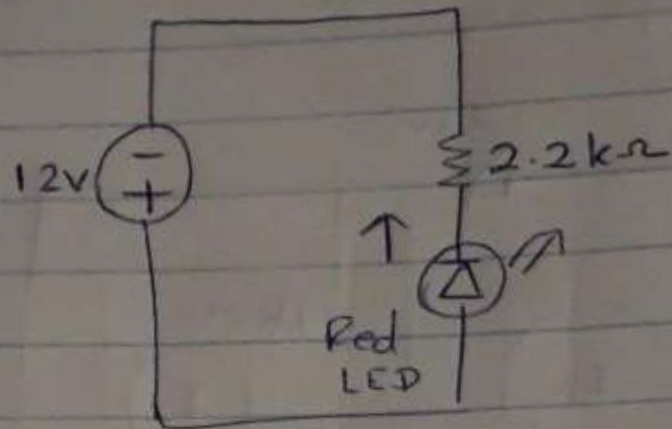

$$\begin{aligned} I_{\text{Red LED}} &= \frac{12 - 2.1}{2.2 \times 10^3} \\ &= 4.5 \times 10^{-3} \text{ A} \\ &= 4.5 \text{ mA} // \end{aligned}$$

Q1(b) V_1

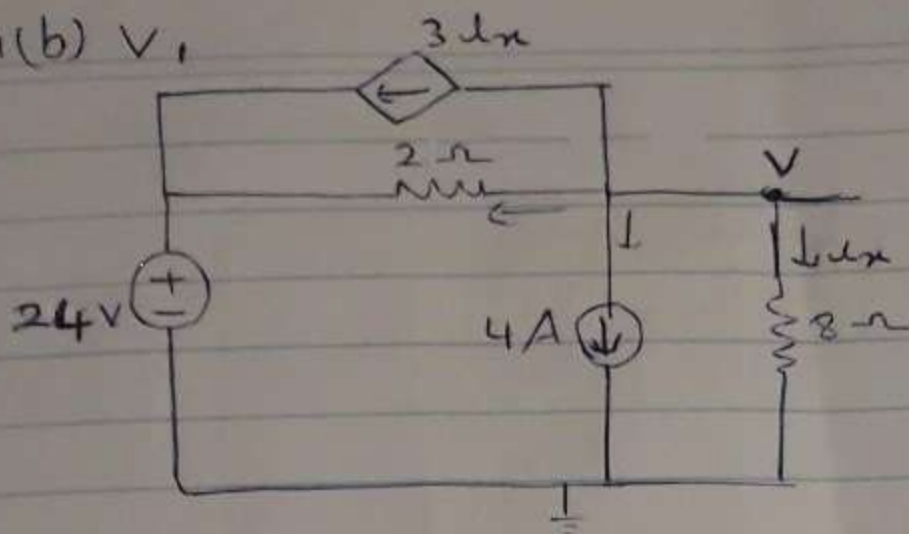

$$i_x = \frac{V}{8} \quad \text{--- (1)}$$

nodal

$$4 + i_x + \frac{V - 24}{2} + 3i_x = 0 \quad \text{--- (2)}$$

$$\text{(2)} \xrightarrow{\text{(1)}} 4 + \frac{V}{8} + \frac{V}{2} - \frac{24}{2} + \frac{3V}{8} = 0$$

$$\frac{V}{8} + \frac{V}{2} + \frac{3V}{8} = 8$$


$$\frac{V + 4V + 3V}{8} = 8$$

$$8V = 8 \times 8$$

$$V = 8V //$$

$$V_{th} = 8V$$

I_{sc} : $i_x = 0$

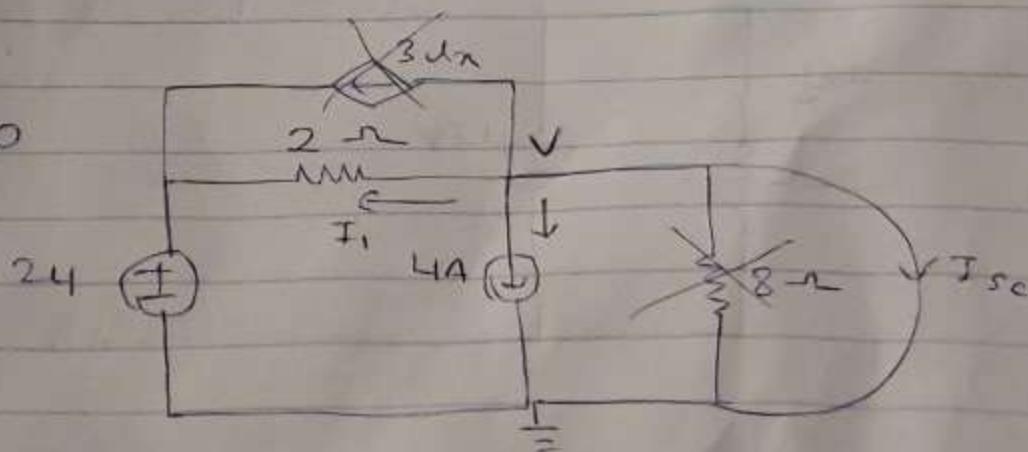

$$I_{sc} + 4 + I_1 = 0$$

$$I_{sc} + 4 + \frac{V - 24}{2} = 0$$


$$V=0$$

$$I_S + 4 - \frac{24}{2} = 0$$

$$I_S = 8A //$$


$$R_{No} = \frac{V_{th}}{I_S}$$

$$= \frac{8}{8} = 1\Omega$$

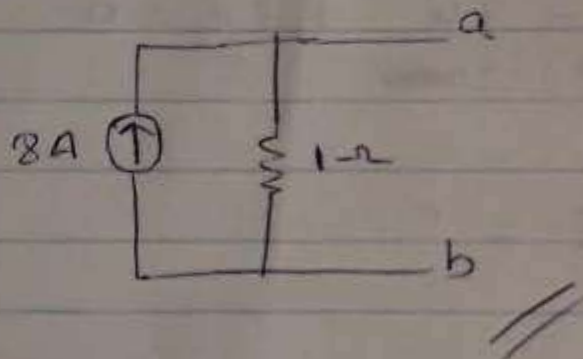

Qu2 (a)

Qu2 a) V_1

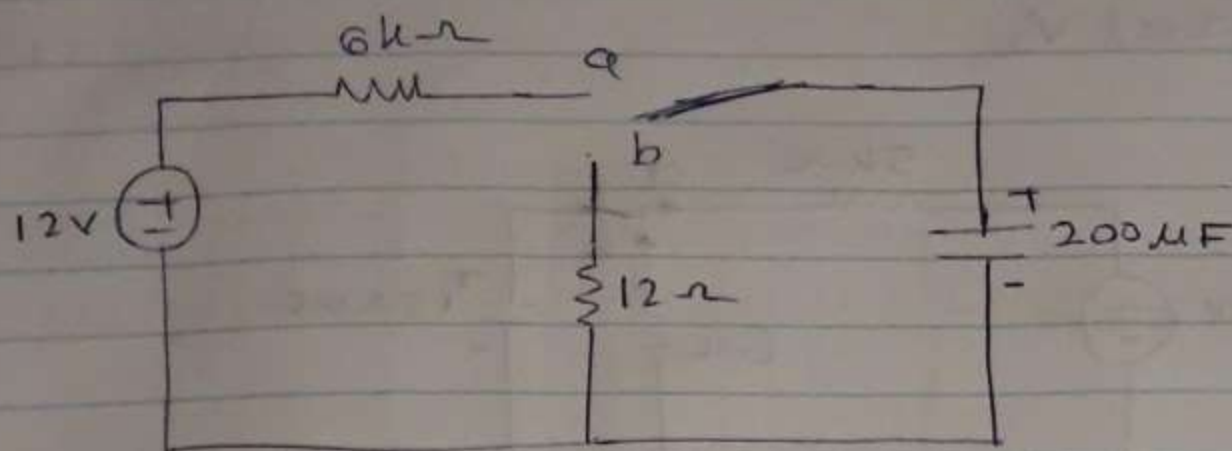

i/ $V_0 = 12V$


$$V(t) = V_0 e^{-t/RC}$$

$$V(t) = 12 \times e^{-t/0.0024}$$


$$\begin{aligned} \tau = RC &= 12 \times 200 \times 10^{-6} \\ &= 2400 \times 10^{-6} \\ &= 0.0024 \end{aligned}$$

$$V(t) = 12 \times e^{-\frac{0.0012}{0.0024}}$$

$$V(t) = 7.27V //$$

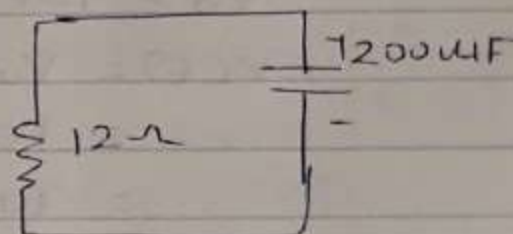



ii/

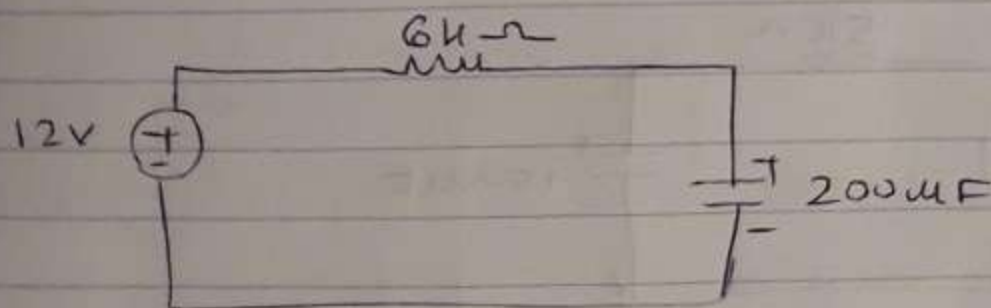

$$\begin{aligned} t &= 5\tau \\ &= 5 \times 1.2 \\ &= 6S // \end{aligned}$$

$$\begin{aligned} \tau = RC &= 6 \times 10^3 \times 200 \times 10^{-6} \\ &= 12 \times 10^5 \times 10^{-6} \\ &= 1.2S \end{aligned}$$


Q2b

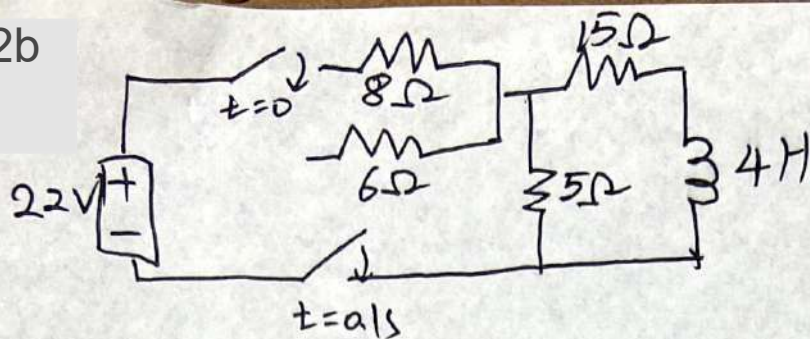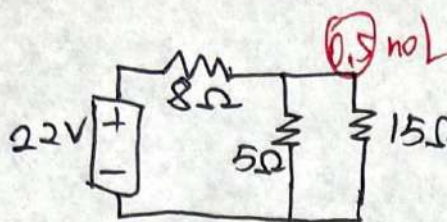 $t < 0$ 

$$I_1 = \frac{22}{8 + 5 \parallel 15} = 1.8723 \text{ (A)}$$

① calculate result

$$I_{o(0)} = I_1 \times \frac{5}{20} = 0.4681 \text{ (A)}$$

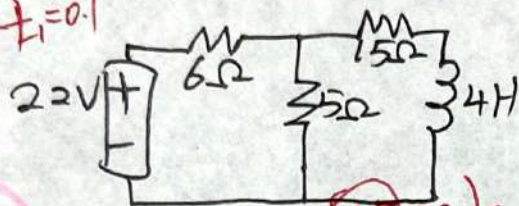 $0 < t < t_1 = 0.1$ 

$$i(t) = i(\alpha) + [i(0) - i(\alpha)] e^{-\frac{t}{\lambda_1}}$$

steady state.

$$I_1 = \frac{22}{6 + 5 \parallel 15} = 2.2564 \text{ (A)}$$

① calculate result

$$I_{o(\alpha)} = I_1 \times \frac{5}{20} = 0.5641 \text{ (A)}$$


$$\lambda_1 = \frac{L}{R} = \frac{4}{15 + 6 \parallel 5} = 0.2256$$

$$\text{formula } i_o(t) = i(\alpha) + [i(0) - i(\alpha)] e^{-\frac{t}{\lambda_1}} \text{ step}$$

$$= 0.5641 + [0.4681 - 0.5641] \cdot e^{-\frac{t}{0.2256}}$$

$$= 0.5641 - 0.096 e^{-4.4318t}$$

① Substitution

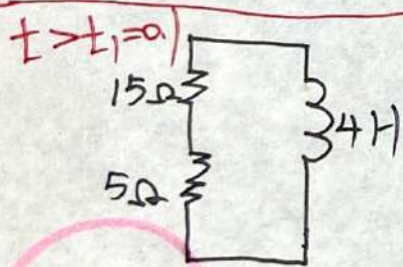

$$I_o(t) = I_{o(0)} e^{-\frac{(t-t_1)}{\lambda_2}}$$

$$i_o(0) = I_{o(\alpha)} + [i_o(0) - I_{o(\alpha)}] \cdot e^{-\frac{t_1}{\lambda_1}}$$

$$= 0.5641 - 0.096 e^{-4.4318 \times 0.1}$$

$$= 0.5025 \text{ (A)}$$

① initial condition

$$\lambda_2 = \frac{L}{R} = \frac{4}{15 + 5} = 0.2$$

$$I_o(t) = I_{o(0)} \cdot e^{-\frac{(t-t_1)}{\lambda_2}} \text{ formula}$$

$$= 0.5025 e^{-(0.5-5t)/0.2} \text{ time shift}$$

① Substitution

 $t = t_2 = 0.2$

$$I_{o(0.2)} = 0.5025 e^{(0.5-5 \times 0.2)}$$


$$= 0.3048 \text{ (A)}$$

① Substitution

① Calculation

Q3a)

(v1)

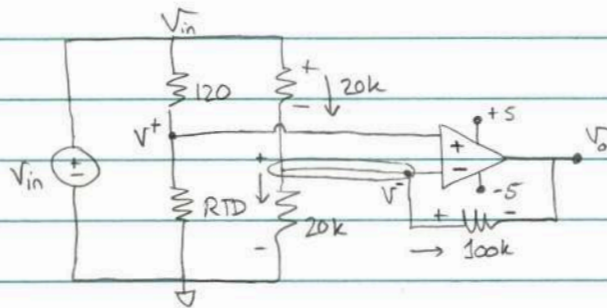

$$RTD = 130 \Omega$$

i) $V^+ = V^- = V_{in} \frac{130}{250} = 0.52 V_{in}$ ①

KCL @ V^- : $\frac{V_{in} - V^-}{20k} - \frac{V^-}{20k} - \frac{V^- - V_o}{100k} = 0$ ②

Substitute ① in ②: $\frac{(1-0.52)V_{in}}{2} - \frac{0.52V_{in}}{2} - \frac{0.52V_{in} - V_o}{10} = 0$

$$(5 \times 0.48 - 5 \times 0.52 - 0.52)V_{in} = -V_o$$

$$-0.72 V_{in} = +V_o$$


$$V_o = 0.72 V_{in}$$

ii) $V_o = 0.72 V_{in} = \pm 5$

$$|V_{in}| = 5/0.72 = 6.94 V$$

Q3b)


(v1)

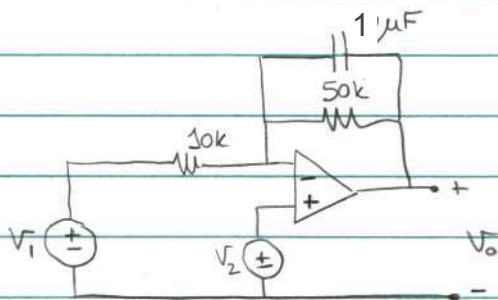

$$\begin{aligned} V_1 &= 3 \sin(t) \text{ A} \\ V_2 &= 4 \text{ V} \end{aligned}$$

We need to use superposition, since we have 2 sources with different frequencies


1.) Contribution of DC source

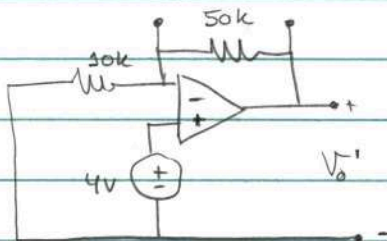

Non-inverting amplifier $V_o = \left(1 + \frac{R_f}{R_1}\right) V_{in}$

$$V_o' = \left(1 + \frac{50k}{30k}\right) 4 = 6 \times 4 = \underline{\underline{24 \text{ V}}}$$

2.) Contribution of AC source

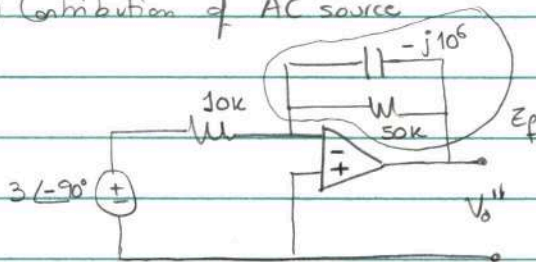

$$Z_c = -j \frac{1}{\omega c} = -j \frac{1}{1 \times 10^6} = -j 10^6 \Omega$$

Inverting amplifier $V_o = -\frac{Z_f}{Z_i} V_{in}$

$$V_o'' = -\frac{Z_f}{Z_i} \times 3 \angle -90^\circ$$

$$\text{where } Z_f = 50k \parallel (-j10^6) = \frac{5 \times 10^4 \times (-j) \times 10^6}{50k - j10^6} =$$

$$= \frac{5 \times 10^6 \angle -90^\circ}{5 - j100} = \frac{5 \times 10^6 \angle -90^\circ}{100.12 \angle -87.14^\circ} = 49940.07 \angle -2.86^\circ \Omega$$


$$V_o'' = \frac{49940.07 \angle -2.86^\circ \times 3 \angle -90^\circ}{30k} = \underline{\underline{14.98 \angle 87.14^\circ \text{ V}}}$$

3.) Add contributions in time domain

$$\underline{\underline{V_o(t) = 24 + 14.98 \cos(t + 87.14^\circ) \text{ V}}}$$

Q4 a)

(v1)

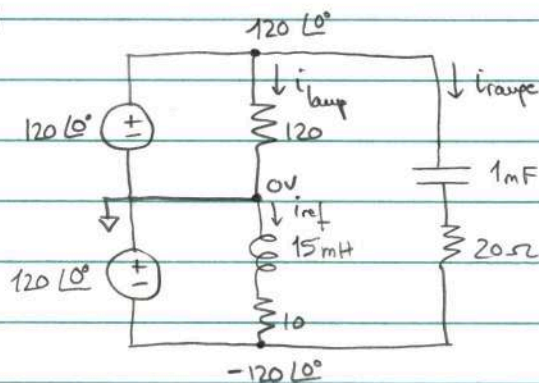

First, convert to phasor domain ($f = 60\text{Hz}$)

$$Z_L = j\omega L = j \times 2\pi 60 \times 15 \times 10^{-3} = j 5.65 \Omega$$

$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{2\pi 60 \times 10^{-3}} = -j 2.65 \Omega$$

Then, calculate currents:

$$I_{\text{lamp}} = \frac{120 \angle 0^\circ}{120} = 1 \text{ A}$$

$$I_{\text{ref}} = \frac{120 \angle 0^\circ}{10 + j 5.65} = \frac{120 \angle 0^\circ}{11.486 \angle 29.47^\circ} = 10.45 \angle -29.47^\circ \text{ A}$$


$$I_{\text{range}} = \frac{120 - (-120)}{20 - j 2.65} = \frac{240 \angle 0^\circ}{20.175 \angle -7.55^\circ} = 11.9 \angle 7.55^\circ \text{ A}$$

Finally, convert back to time domain:

$$i_{\text{lamp}} = \cos(120\pi t) \text{ A}$$

$$i_{\text{ref}} = 10.45 \cos(120\pi t - 29.47^\circ) \text{ A}$$
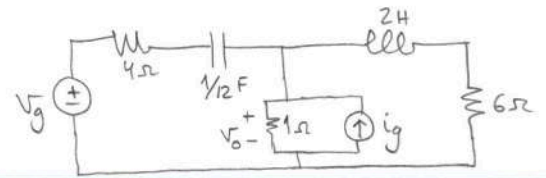
$$i_{\text{range}} = 11.9 \cos(120\pi t + 7.55^\circ) \text{ A}$$




$$V_g = 14 \sin 4t \text{ V}$$

$$i_g = 2 \cos 4t \text{ A}$$

Q4b)

(v1)

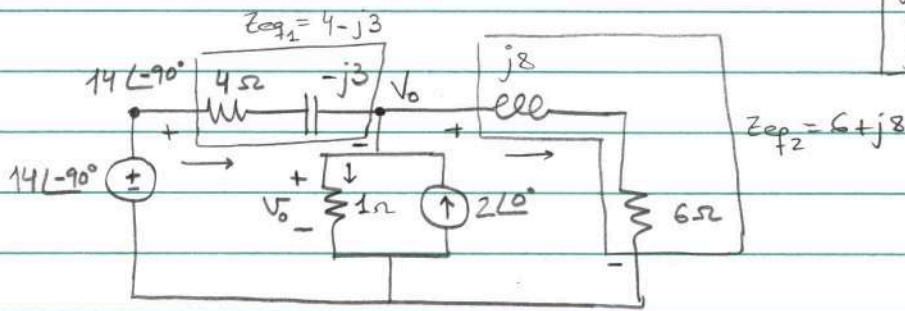

First, convert into phasor domain ($\omega = 4 \text{ rad/s}$)

$$v(t) = 14 \sin 4t \rightarrow V = 14 \angle -90^\circ$$

$$i(t) = 2 \cos 4t \rightarrow I = 2 \angle 0^\circ$$

$$Z_c = -j \frac{1}{\omega c} = -j \frac{1}{4 \times \frac{1}{2}} = -j3 \Omega$$

$$Z_L = j\omega L = j4 \times 2 = j8 \Omega$$

Then, use nodal analysis to find V_0 :

$$\frac{14 \angle -90^\circ - V_0}{4 - j3} - V_0 + 2 - \frac{V_0}{6 + j8} = 0$$

$$+ \left(\frac{+1}{4 - j3} + 1 + \frac{1}{6 + j8} \right) V_0 = + \left(2 + \frac{14 \angle -90^\circ}{4 - j3} \right)$$

$$\left(1 + \frac{1}{5 \angle -36.87^\circ} + \frac{1}{10 \angle 53.13^\circ} \right) V_0 = 2 + \frac{14 \angle -90^\circ}{5 \angle -36.87^\circ}$$

$$(1 + 0.2 \angle 36.87^\circ + 0.1 \angle -53.13^\circ) V_0 = 2 + 2.8 \angle -53.13^\circ$$


$$V_0 = \frac{2 + 1.68 - j2.24}{1 + 0.16 + j0.12 + 0.06 - j0.08} = \frac{3.68 - j2.24}{1.22 + j0.04} = \frac{4.31 \angle -31.33^\circ}{1.22 \angle 1.88^\circ} = 3.53 \angle -33.21^\circ \text{ V}$$

Finally, convert back to time domain:

$$V_0(t) = 3.53 \cos(4t - 33.21^\circ) \text{ V}$$

Q52)

(v1)

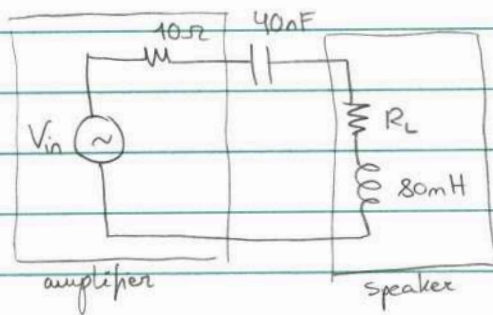

$$\boxed{\begin{array}{l} \text{Power in speaker} \\ |V_{in}| = 4.6 \text{ V}_{rms} \end{array}}$$

i) For MPT $Z_L = Z_{th}^*$, where $Z_L = R_L + j\omega L$
 $Z_{th} = 10 - j \frac{1}{\omega C}$

$$R_L = R_{th} \Rightarrow \boxed{R_L = 10 \Omega}$$

$$X_L = -X_{th} \Rightarrow j\omega L = \frac{1}{\omega C}$$

$$\omega^2 LC = 1 \Rightarrow \boxed{\omega = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{80 \times 10^{-3} \times 40 \times 10^{-9}}} = 17677.67 \text{ rad/s}}$$

ii) $V_{in} = 4.6 \text{ V}_{rms}$


$$\boxed{P_{\text{speaker}} = P_{10\Omega} + \underset{0}{P_{\text{parallel}}} = \frac{V_{10\Omega rms}^2}{10} = \frac{2.3^2}{10} = 0.529 \text{ W}}$$

Note: $P_{max} = \frac{|V_{th}|^2}{8R_{th}}$
 will give same result
 in questions for power in
 speaker

Use voltage division to find $V_{10\Omega rms}$: $V_{10\Omega rms} = V_{in} \frac{10}{20} = 2.3 \text{ V}_{rms}$

Q5 b)

(v5)

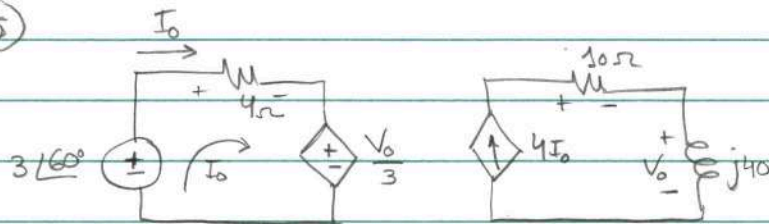

Power in 10Ω resistor

$$P_{10\Omega} = \frac{1}{2} V_{m10} I_{m10} = \frac{1}{2} \frac{V_{m10}^2}{10} = \frac{1}{2} I_{m10}^2 \times 10$$

$$I_{10\Omega} = 4I_o \quad (1)$$

Find equation for I_o from left mesh:

$$(KVL) -3\angle 60^\circ + 4I_o + \frac{V_o}{3} = 0 \quad (2), \text{ where } V_o = j40 \times 4I_o = j160I_o$$

$$-3\angle 60^\circ + 4I_o + j53.3I_o = 0$$

$$I_o = \frac{+3\angle 60^\circ}{4 + j53.3} = \frac{3\angle 60^\circ}{53.45 \angle 85.71^\circ} = 0.056 \angle -25.71^\circ$$

From (1),

$$I_{10\Omega} = 4I_o = 0.224 \angle -25.71^\circ \text{ A} \Rightarrow \boxed{P_{10\Omega} = \frac{1}{2} I_m^2 \times 10 = 5 \times 0.224^2 = 0.251 \text{ W}}$$