

Topic 4 recap

- A capacitor is a circuit element that stores energy in its electric field.
- The ratio of charge to voltage across a capacitor is its *capacitance* (F).

$$C = \frac{q}{v} \rightarrow q = Cv$$

- Current in a capacitor is proportional to the time rate of change of its voltage.

$$i = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

- Energy stored in a capacitor is proportional to the square of its voltage.

$$w_c = \frac{1}{2} Cv^2$$

- Capacitor acts as an open circuit to DC voltage.
- Parallel combination of capacitors is similar to series resistors.

$$C_{eq} = C_1 + C_2 + \dots + C_N$$

- Series combination of capacitors is similar to parallel resistors.



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \dots + \frac{1}{C_N}$$

Topic 4 recap

- Natural response of RC circuits
 - Behaviour of the circuit (in terms of voltage or current) due to initial energy stored.
 - If the capacitor has a initial voltage $v(0) = V_0$, the natural response of the RC circuit is:

$$v(t) = V_0 e^{-\frac{t}{RC}}$$

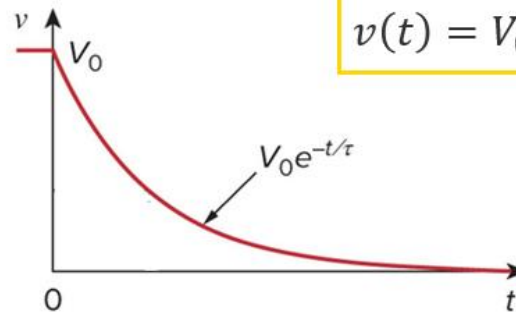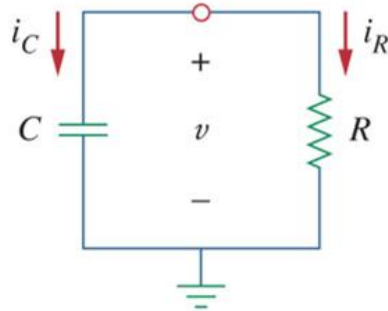- The natural response decay to zero exponentially.




$$v(t) = V_0 e^{-\frac{t}{RC}}$$

Topic 4 recap

- Time constant



- The speed at which the voltage decays is given by the *time constant*:

- Time constant is the time required for the response to decay to a factor of $1/e$ or **36.8%** of its **initial value** or to reach **63.2%** of its **final value**.
 - For an RC circuit $\tau = RC$.
 - After **5 time constant**, 5τ , the capacitor voltage is considered to have reached its final value.
 - The higher R and C, the longer it would take for the capacitor to charge or discharge.
 - The resistance for the time constant is the **Thevenin equivalent resistance** as seen from the capacitor terminals.

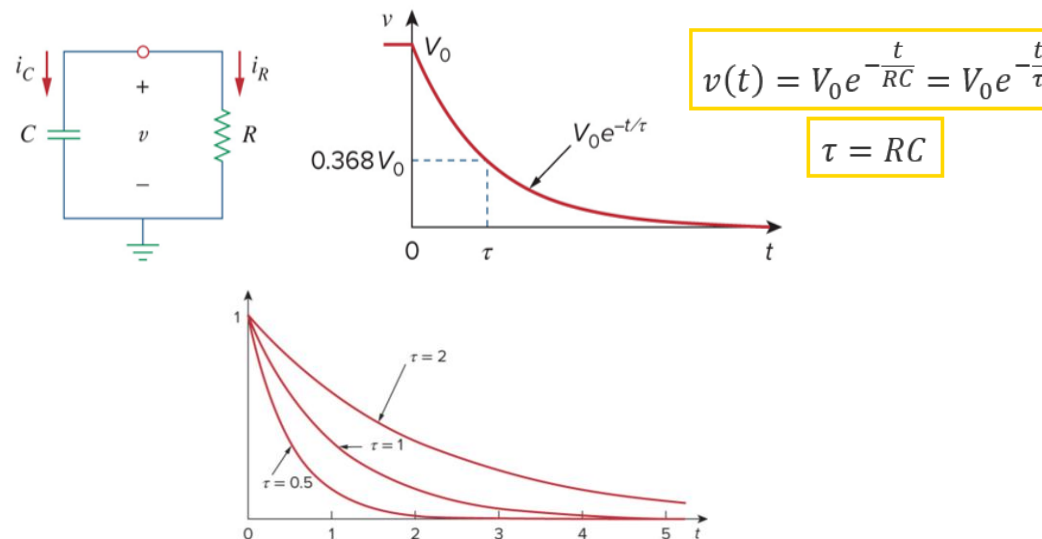

Topic 4 recap

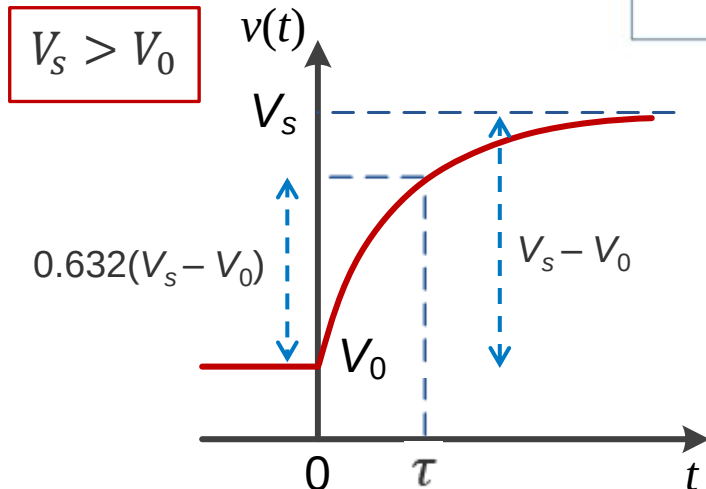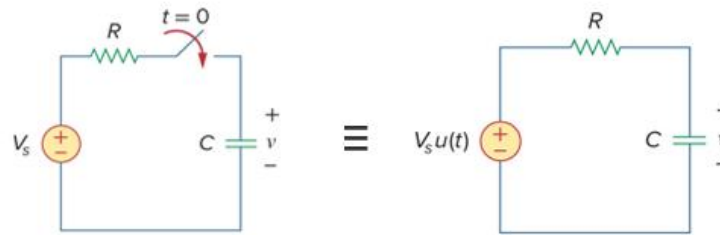- Step response of RC circuits
 - The unit step function can be used in electric circuits to model switching.
- $$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$
- The step response is the response to a sudden change in the input sources.
 - The capacitor voltage over time is obtained as an exponential function:



$$v(t) = V_s + (V_0 - V_s)e^{-\frac{t}{\tau}}, \quad t > 0$$
$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}, \quad t > 0$$

$$\tau = RC$$

Topic 4 recap

- Step response of RC circuits
 - If the initial voltage $v(0) = 0 \text{ V}$, the response is known as **forced response**.
 - The step response with non-zero initial condition is known as **complete response**.
 - It can be described as the sum of **transient** and **steady state responses**.
 - The general solution to the step response of RC circuits can be given as follows:
$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}, \quad t > 0$$
 - $v(0)$: **Initial voltage** at $t = 0$.
 - $v(\infty)$: **Final or steady-state value** at $t \rightarrow \infty$.
 - $\tau = R_{\text{Th}_\infty}C$: Time constant at $t \rightarrow \infty$.
 - If the switch changes position at time $t=t_0$ instead of $t=0$, there is a time delay in the response which can be expressed as time shift in the equation.
 - This method can be used for multiple switching at different times.

$$v(t) = v(\infty) + [v(t_0) - v(\infty)]e^{-\frac{(t-t_0)}{\tau}}, \quad t > t_0$$