
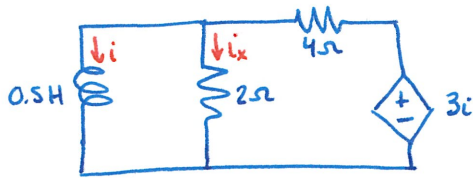


EXERCISE 2 (Natural response RL)

Find i and i_x if $i(0) = 10 \text{ A}$

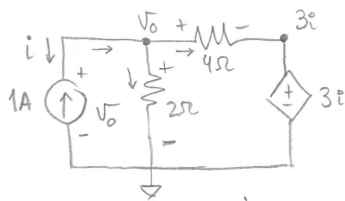

* First, calculate R_{th}



$$R_{th} = \frac{V_o}{i_o}$$

$$i_o = -1 \text{ A}$$

→ Nodal analysis:

$$1 - \frac{V_o}{2} - \frac{V_o - 3i}{4} = 0$$

$$1 - \frac{V_o}{2} - \frac{V_o}{4} + \frac{3}{4}i = 0 \Rightarrow -\frac{3}{4}V_o = -1 + \frac{3}{4}$$

$$-\frac{3}{4}V_o = -\frac{1}{4}$$


$$V_o = \frac{1}{3} \text{ V}$$

$$R_{th} = \frac{V_o}{i_o} = \frac{\frac{1}{3} \text{ V}}{1 \text{ A}} = \frac{1}{3} \Omega$$

* Then calculate time constant and natural response

$$\tau = \frac{L}{R_{th}} = \frac{0.5 \text{ H}}{1/3 \Omega} = \frac{3}{2} \text{ s}$$

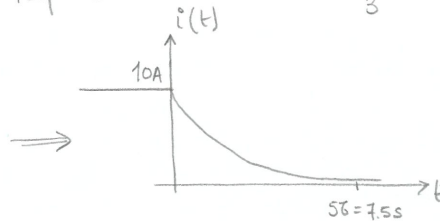
$$i(t) = I_0 e^{-t/\tau} = 10 e^{-\frac{2t}{3}} \text{ A}$$





$$i_x(t) = \frac{V_L(t)}{2} = \frac{1}{2} V_L(t) = \frac{1}{2} L \frac{di}{dt} = \frac{1}{2} \times \frac{1}{2} \times 10 \times \left(-\frac{2}{3}\right) e^{-\frac{2t}{3}} = -\frac{5}{3} e^{-\frac{2t}{3}} \text{ A}$$

EXERCISE 3 (Natural response RL)

Find $i(t)$ for $t > 0$

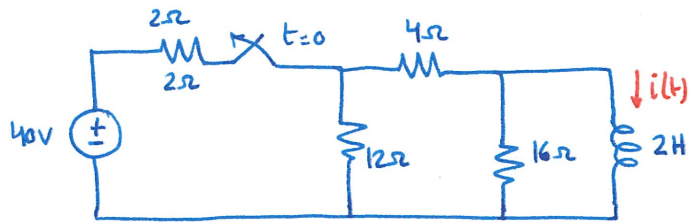

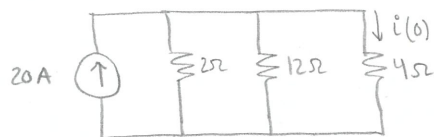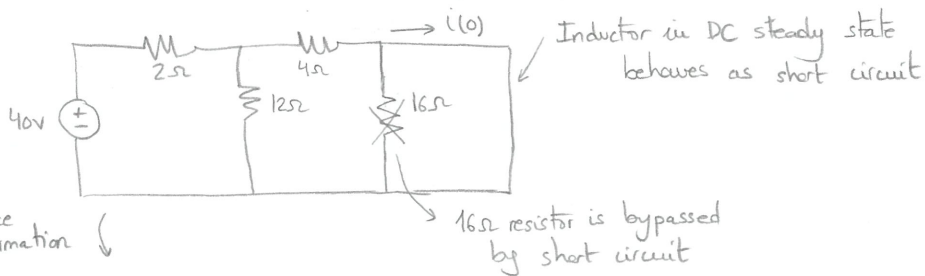* First, find the initial conditions ($t \leq 0$)



$$i(0) = 20 \frac{2 \parallel 12 \parallel 4}{4} = \frac{20}{4} \times \frac{12}{10} = 6A$$

↑
current divider

$$2 \parallel 12 \parallel 4 = \frac{1}{\frac{1}{2} + \frac{1}{12} + \frac{1}{4}} = \frac{1}{\frac{6+1+3}{12}} = \frac{12}{10} \Omega$$

* Then, update circuit and calculate natural response:




simplify


$$R_{eq} = R_{th} = (12+4) \parallel 16 = 8\Omega$$

$$\tau = \frac{L}{R_{th}} = \frac{2H}{8\Omega} = \frac{1}{4} s$$

$$i(t) = I_0 e^{-t/\tau} = 6 e^{-4t} A$$

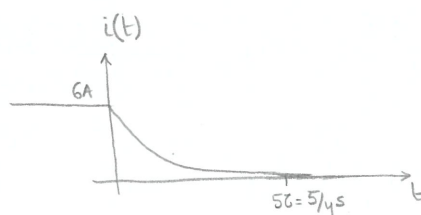


EXERCISE 4 (Step response RL)

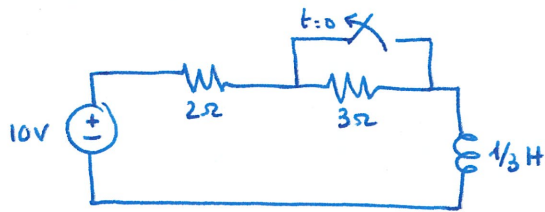

Find $i(t)$ for $t \geq 0$

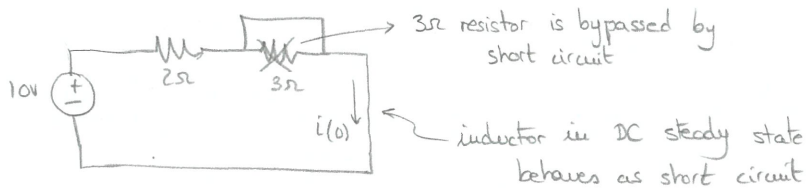
* First, calculate initial conditions ($t \leq 0$)



$$i(0) = \frac{10V}{2\Omega} = 5A$$

* Then, update circuit and calculate step response:

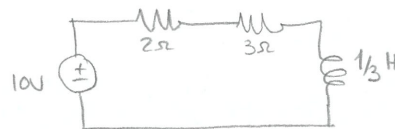
$$i(t) = i(\infty) + (i(0) - i(\infty))e^{-t/\tau}$$



We calculate $i(\infty) \rightarrow$ DC steady state again $\rightarrow$ L is short circuit




We calculate τ :

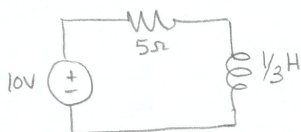


$$\tau = \frac{L}{R} = \frac{1/3 H}{5\Omega} = 1/15 s$$

$R_{th} = R$

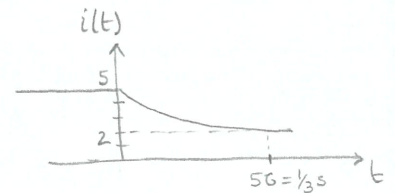
$$i(t) = i(\infty) + (i(0) - i(\infty))e^{-t/\tau} = 2 + (5 - 2)e^{-15t} = 2 + 3e^{-15t} A$$




EXERCISE 5 (Step response RL)

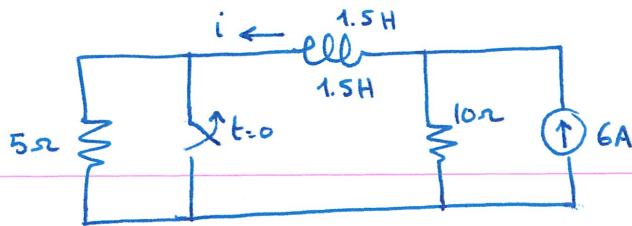

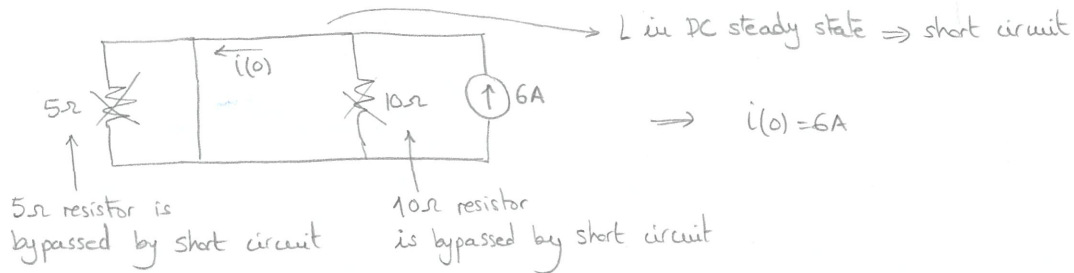
* First, calculate initial conditions $i(0)$ ($t \leq 0$)



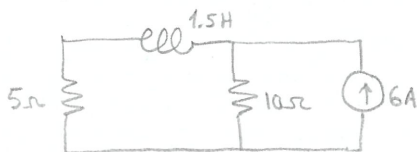
* Then, update circuit and calculate step response: $i(t) = i(\infty) - (i(0) - i(\infty))e^{-t/\tau}$



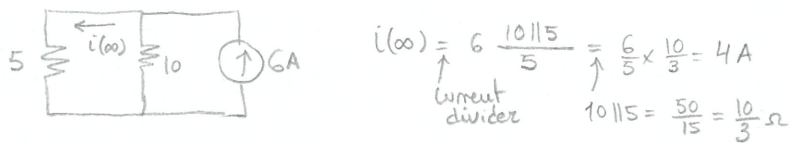We calculate $i(\infty) \rightarrow$ DC steady state again $\rightarrow$ L is short circuit



We calculate $\tau = \frac{L}{R_{th}}$:

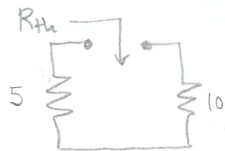

$$R_{th} = 5 + 10 = 15 \Omega$$

$$\tau = \frac{L}{R_{th}} = \frac{1.5H}{15\Omega} = 0.1s$$

$$i(t) = i(\infty) + (i(0) - i(\infty))e^{-t/\tau} = 4 + (6 - 4)e^{-t/0.1} = 4 + 2e^{-10t}$$

