



Family Name

Given Name

Student No.

Signature

THE UNIVERSITY OF NEW SOUTH WALES

School of Electrical Engineering & Telecommunications

MID-TERM EXAMINATION

Term 3, 2019

ELEC1111

Electrical and Telecommunications Engineering

TIME ALLOWED: 75 min

TOTAL MARKS: 100

TOTAL NUMBER OF QUESTIONS: 5

THIS EXAM CONTRIBUTES 25% TO THE TOTAL COURSE ASSESSMENT

Reading Time: 5 minutes.

This paper contains 5 pages.

Candidates must **ATTEMPT ALL** questions.

Answer each question in a **separate answer booklet**.

Marks for each question are indicated beside the question.

This paper **MAY NOT** be retained by the candidate.

Print your name, student ID and question number on the front page of each answer book.

Authorised examination materials:

Candidates should use their own UNSW-approved electronic calculators.

This is a closed book examination.

Assumptions made in answering the questions should be stated explicitly.

All answers must be written in ink. Except where they are expressly required, pencils **may only be used** for drawing, sketching or graphical work.

QUESTION 1 [15 marks]

- a. (9 marks) For the circuit shown in Figure 1,
- (7 marks) Calculate the equivalent resistance R_{eq} as seen from terminals $a-b$.
 - (2 marks) Find current i using the result of part (i).

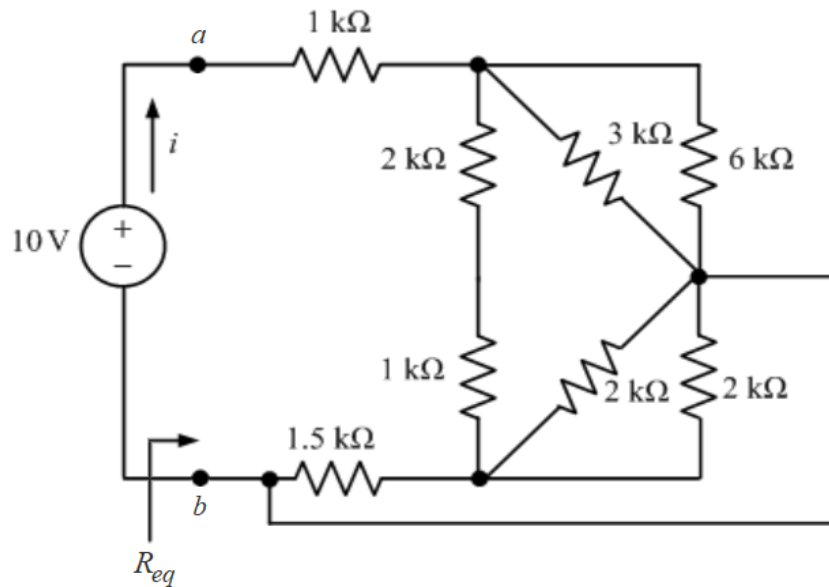


Figure 1

- b. (6 marks) An electric pencil sharpener rated 240 mW, 6 V is connected to a 9 V battery as shown in Figure 2. Calculate the value of the series-dropping resistor, R_x , needed to power the sharpener.

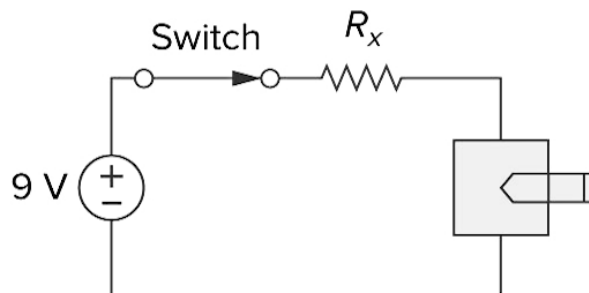


Figure 2

QUESTION 2 [25 marks]

a. (13 marks) For the circuit shown in Figure 3,

- (8 marks) Apply nodal analysis and write down the nodal equations using the labels provided. Note: Simplify the equations, but DO NOT solve them.
- (5 marks) Given the values of nodal voltages as $v_1 = 100\text{ V}$, $v_2 = 550\text{ V}$ and $v_3 = 400\text{ V}$, find the power in the 300 V voltage source.

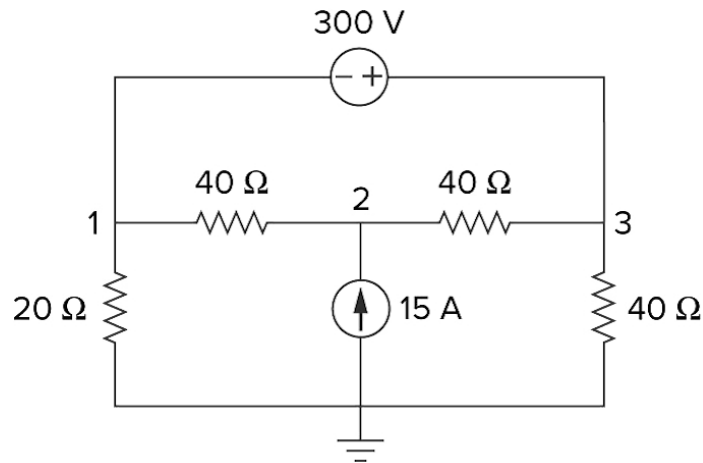


Figure 3

b. (12 marks) Bipolar transistors can serve as amplifiers, producing both current gain and voltage gain. The circuitry in the dashed box models a bipolar junction transistor and the whole circuit in Figure 4 models a transistor amplifier.

For the transistor amplifier shown in Figure 4, apply mesh analysis and write down the mesh equations using the labels provided. Note: Simplify the equations, but DO NOT solve them.

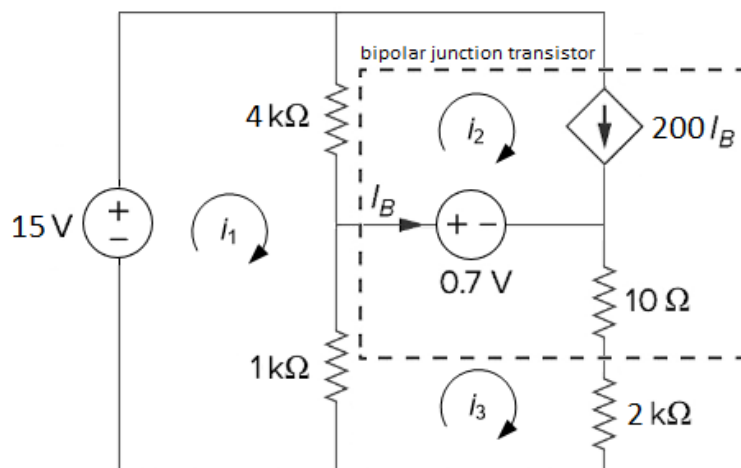


Figure 4

QUESTION 3 [15 marks]

For the circuit shown in Figure 5, use a succession of source transformations to find the voltage v_0 .

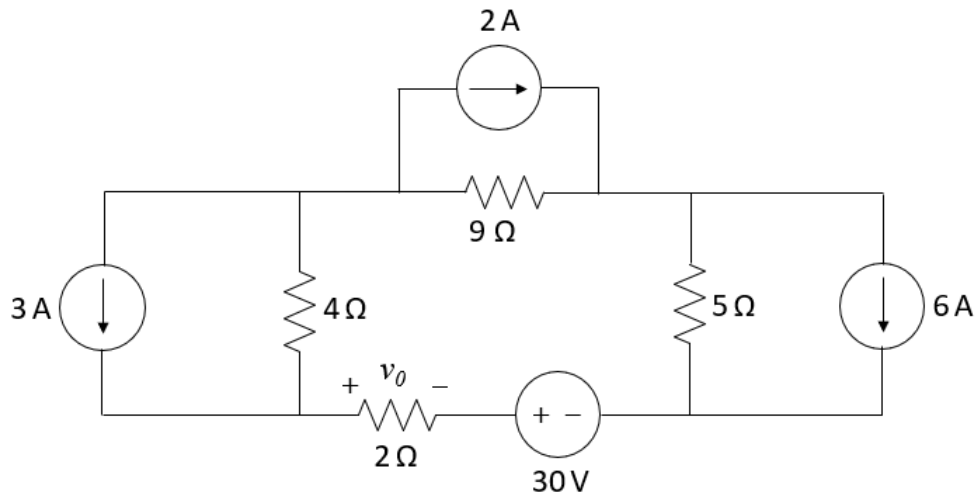


Figure 5

QUESTION 4 [20 marks]

The circuit shown in Figure 6 is being used to power a hot water heater. The heater can be modelled as a single resistor connected to terminals a - b .

- (9 marks)** Calculate the Thevenin voltage at terminals a - b .
- (9 marks)** Calculate the heater resistance that will ensure the maximum transfer of power from the circuit to the heater.
- (2 marks)** Find the maximum power that can be delivered to the heater.

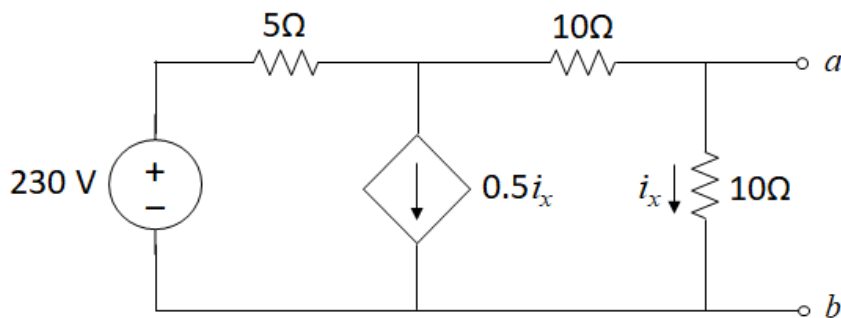


Figure 6

QUESTION 5 [25 marks]

- a. **(10 marks)** Find the voltage across the capacitor, v_C , and the current flowing through the inductor, i_L , in the circuit of Figure 7 under DC steady state conditions.

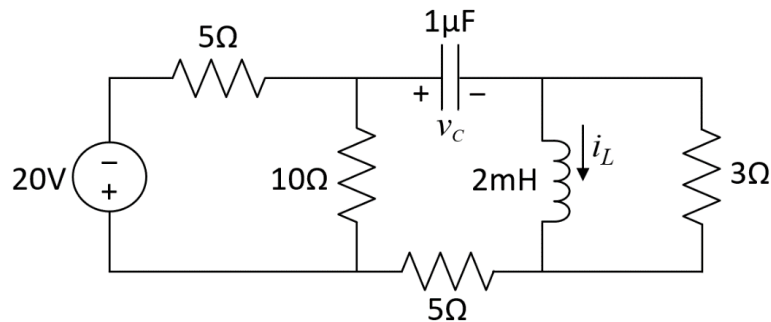


Figure 7

- b. **(15 marks)** The circuit in Figure 8 is designed to operate an alarm which activates when the current through it exceeds 0.1 mA.
- (10 marks)** Calculate the voltage across the capacitor for $t > 0$ s. Assume that the capacitor was initially discharged.
 - (5 marks)** How long does it take for the alarm to activate for the first time after the switch is closed?

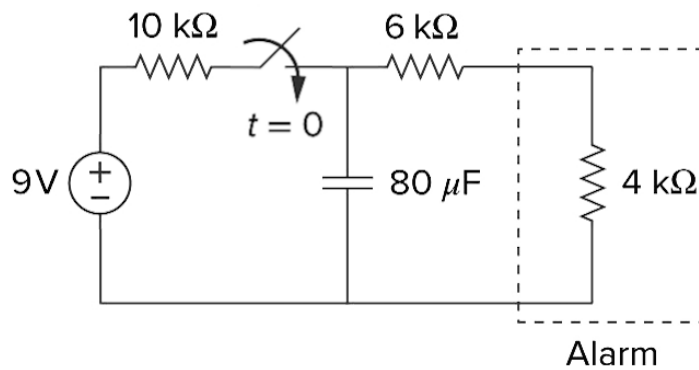


Figure 8