

Q1 (2020 T3 Midterm Exam Q5)

Find the voltage across the capacitors in the circuit of Figure 1 under DC steady state conditions.

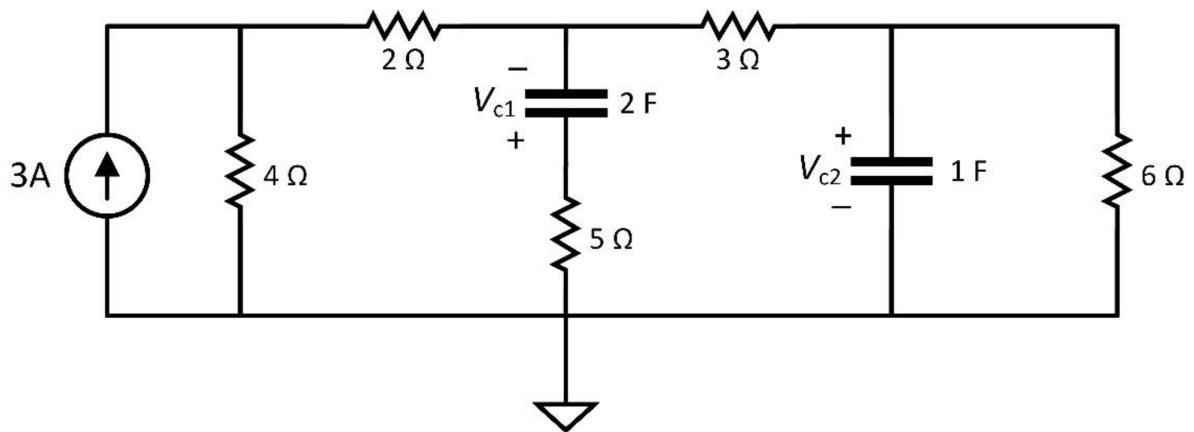


Figure 1

Answers: $V_{c1} = -7.2 \text{ V}$, $V_{c2} = 4.8 \text{ V}$

Q2 (Modified from 2022 T3 Midterm Exam Q5)

The switch in the circuit shown in Figure 2 was open for a long time. It closed at $t = 0$ s and after remaining closed for 5 ms, it opened again.

i) Calculate $v_c(t)$ for $0 \leq t < 5$ ms.

ii) Calculate $v_c(t)$ for $t \geq 5$ ms.

iii) Calculate the value of $i_c(t)$ at $t = 10$ ms.

iv) Determine the current flowing through the $20\ \Omega$ resistor for the time interval $0 \leq t < 5$ ms.

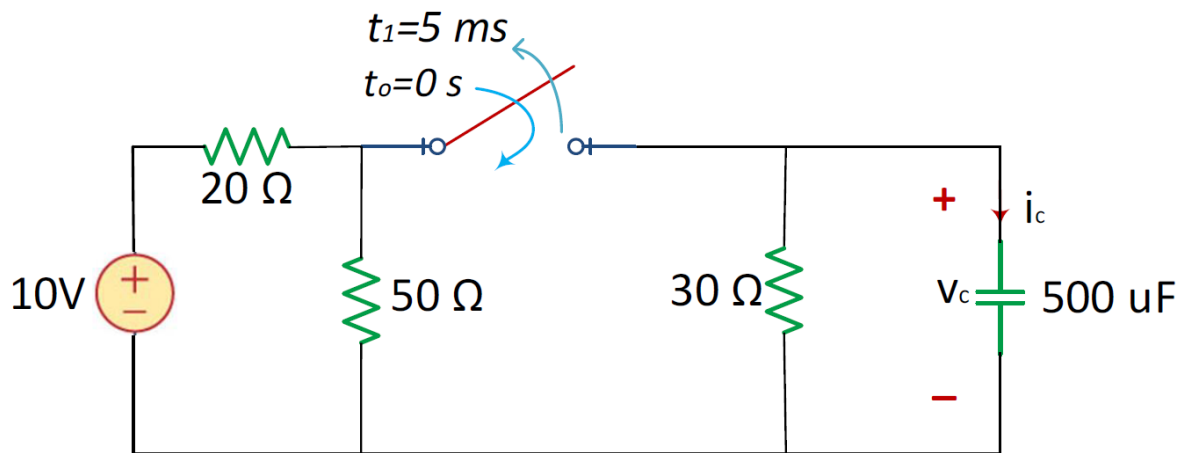


Figure 2

Answers:

i) $v_c(t) = 4.839(1 - e^{-206.65t})$ V,

ii) $v_c(t) = 3.117e^{-66.667(t-0.005)}$ V,

iii) $i_c(t=10\text{ms}) = -0.075$ A,

iv) $i_{20} = 0.5 - 0.242(1 - e^{-206.65t})$ A

Solution to the modified question:


The current flowing through the $20\ \Omega$ resistor for the time interval $0 \leq t < 5$ ms:

$$i_{20} = \frac{10 - V_c}{20\ \text{k}} = \frac{10 - 4.839(1 - e^{-206.65t})}{20} \text{ A}$$
$$= 0.5 - 0.242(1 - e^{-206.65t}) \text{ A}$$


Q3 (Sample exam question)

A phonograph pickup, stereo amplifier, and speaker are shown in Figure 3a and redrawn as a circuit model as shown in Figure 3b.

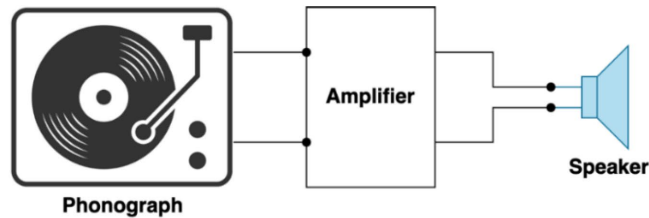- i) Calculate voltage v_x .
- ii) Determine the resistance R so that the voltage v_o across the speaker is 16 V.
- iii) Calculate the power in the dependent voltage source.



(a)

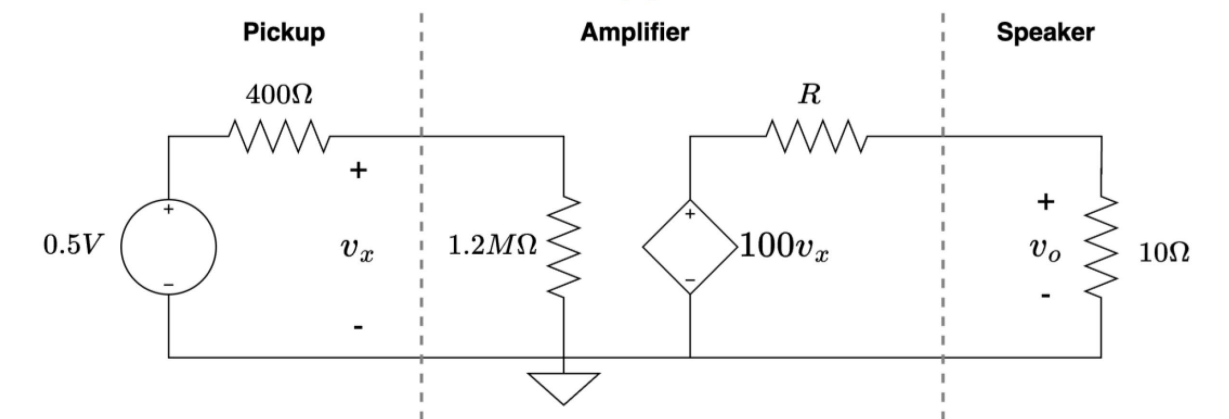


(b)

Figure 3

Answers: i) $v_x = 0.5 \text{ V}$, ii) $R = 21.25 \Omega$, iii) $P = -80 \text{ W}$

Solutions:

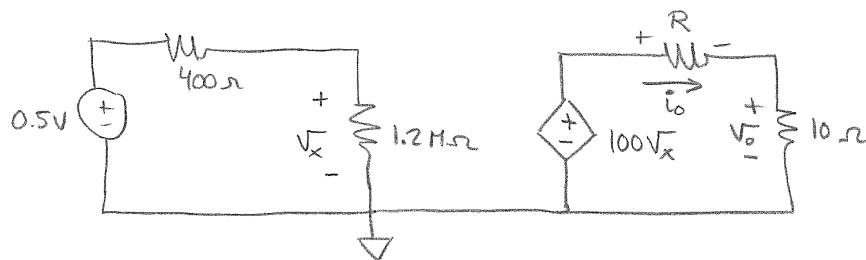

i)

$$V_o = 16V \Rightarrow i_o = \frac{V_o}{10} = \frac{16}{10} = 1.6A$$

KVL @ right mesh: $-100V_x + Ri_o + 10i_o = 0$

where $V_x = 0.5 \frac{1.2M}{1.2M + 400\Omega} = 0.49983V \approx 0.5V$
 ↑
 voltage divider

$$-100 \times 0.5 + (10 + R) \times 1.6 = 0$$

$$(10 + R) 1.6 = 50 \Rightarrow 10 + R = \frac{50}{1.6} = 31.25$$

$$\boxed{R = 31.25 - 10 = 21.25\Omega}$$

ii)

$$\boxed{P_{ds} = -V_{ds} \times i_{ds} = -100V_x \cdot i_o =}$$

$$= -100 \times 0.5 \times 1.6 = \boxed{-80W}$$

Q4 (Sample exam question)

Determine V_0 and the power in the voltage source P_s for the circuit illustrated in Figure 4 under the following conditions:

- i) When element X is a resistor with $R=3\text{k}\Omega$.
- ii) When element X is replaced by a short circuit.
- iii) When element X is an open circuit.


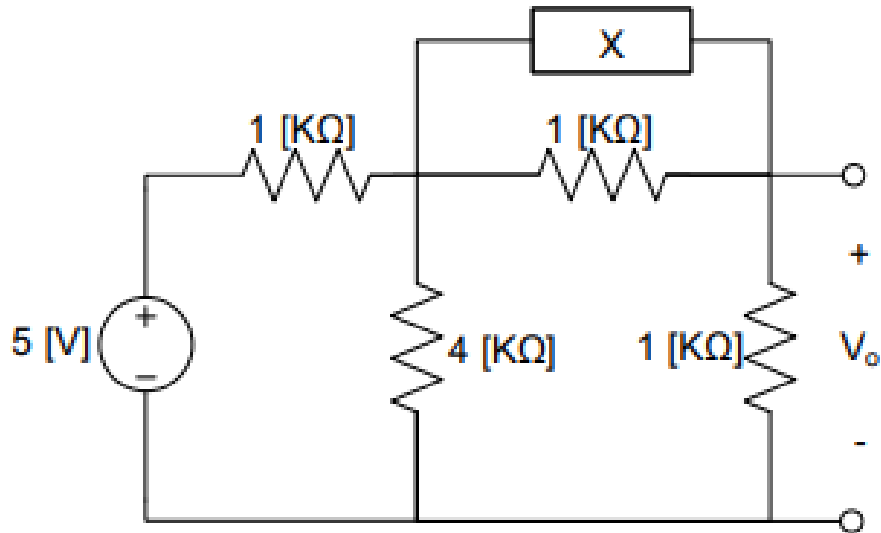
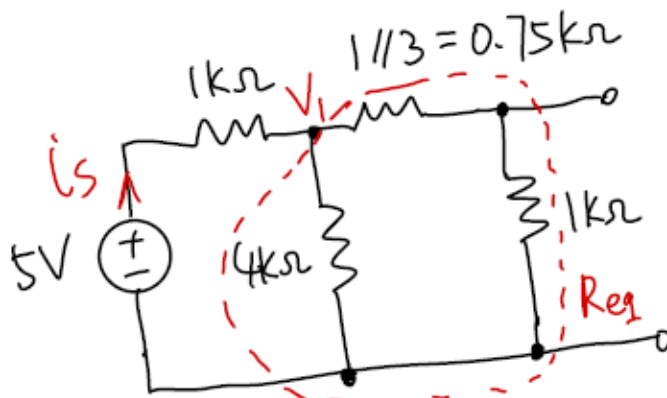


Figure 4

Answers: i) $V_0 = 1.57\text{ V}$, $P_s = -11.26\text{ mW}$, ii) $V_0 = 2.22\text{ V}$, $P_s = -13.9\text{ mW}$, iii) $V_0 = 1.43\text{ V}$, $P_s = -10.72\text{ mW}$

Solutions:

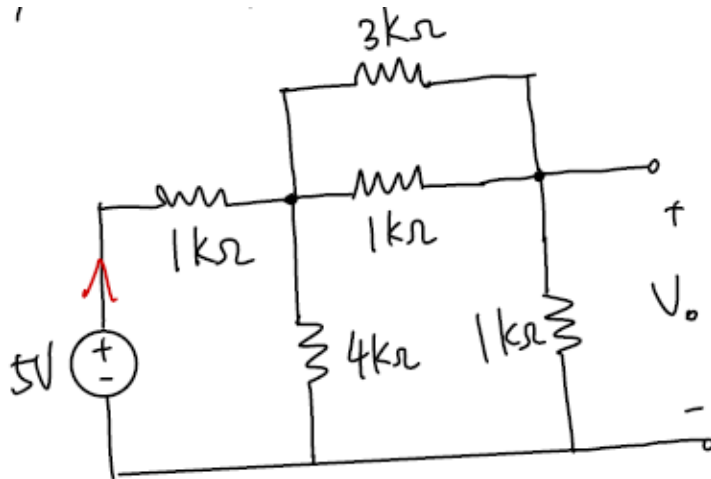i) When element X is a resistor with $R=3k\Omega$.



$$V_1 = 5 \times \frac{4k \parallel (0.75k + 1k)}{1k + 4k \parallel (0.75k + 1k)}$$

$$R_{eq} = \left(\frac{4 \times 1.75}{4 + 1.75} \right) k\Omega = 1.22 k\Omega$$

$$V_1 = 5 \times \frac{1.22 k\Omega}{2.22 k\Omega} = 2.748 V$$

↑ voltage divider

$$V_o = 2.748 \times \frac{1k}{0.75k + 1k} = 2.748 \times \frac{1}{1.75} = 1.57 V$$



↑ voltage divider

$$i_s = \frac{V_s - V_1}{1k} = \frac{5 - 2.748}{1000} = 2.252 mA$$

$$P_s = -V_s i_s = -5 \times 2.252 = -11.26 mW$$

↑ negative sign indicates "supplied"

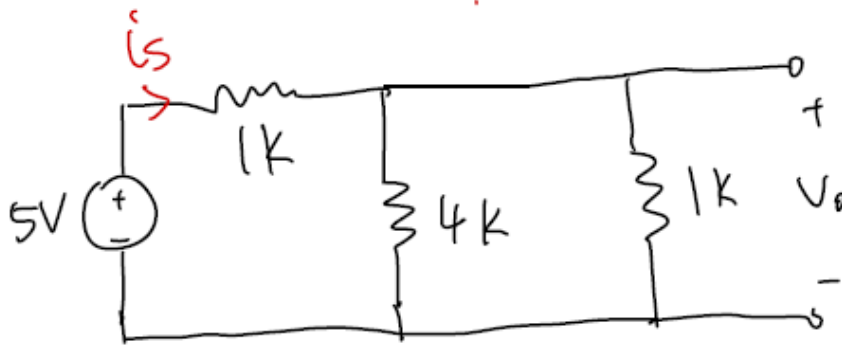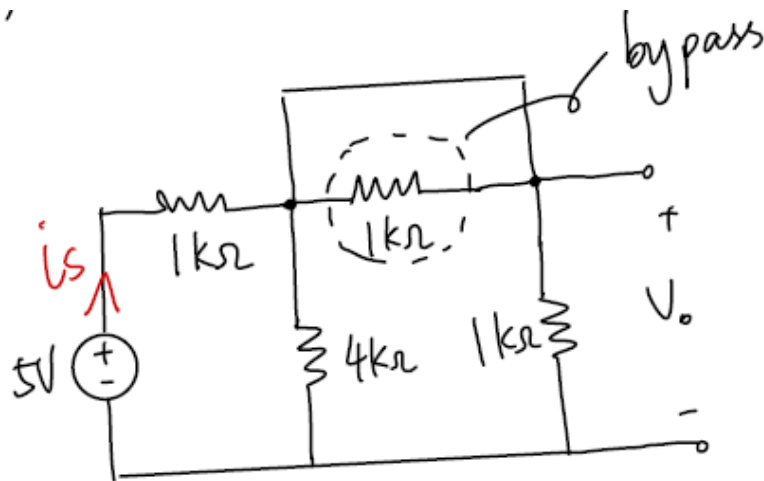ii) When element X is replaced by a short circuit.




$$V_o = 5 \times \frac{1k \parallel 4k}{1k + 1k \parallel 4k} = 5 \times \frac{0.8k}{1.8k} = 2.22 \text{ V}$$

↑ voltage divider

$$i_s = \frac{V_s - V_o}{1k} = \frac{5 - 2.22}{1k} = 2.78 \text{ mA}$$

$$P_s = -V_s i_s = -5 \times 2.78 = -13.9 \text{ mW}$$

iii) When element X is an open circuit.

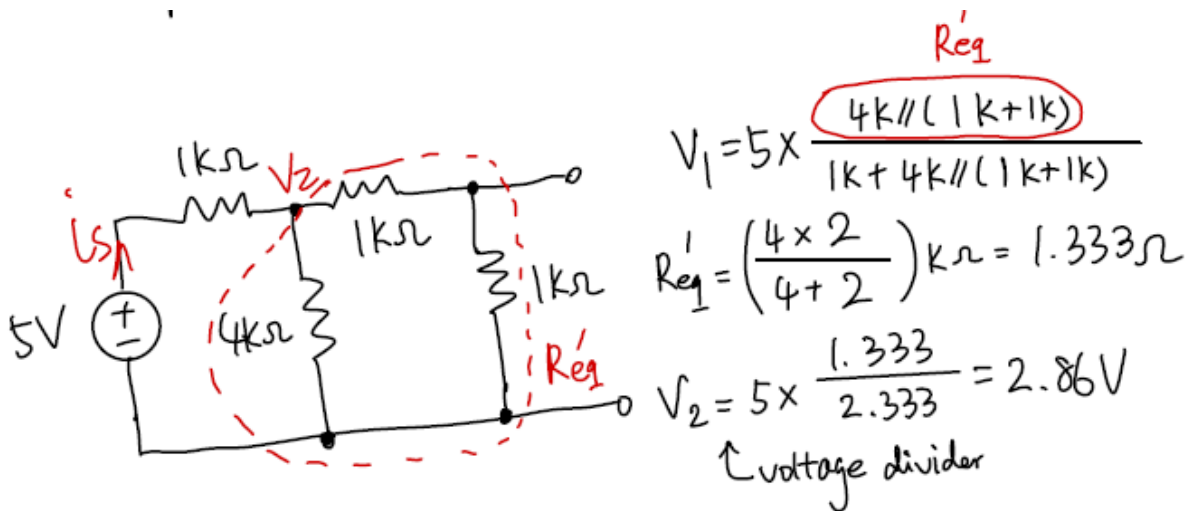

$$V_o = 2.86 \times \frac{1k}{1k + 1k} = 2.86 \times \frac{1}{2} = 1.43V$$

↑ voltage divider

$$i_s = \frac{V_s}{R_{eq} + 1k} = \frac{5}{2.333k} = 2.143mA$$

$$P_s = -V_s i_s = -5 \times 2.143 = -10.72mW$$