

Q1 (2020 T1 Final Exam Q3a)

In the circuit of Figure 1, calculate the voltage v_o if $v_s = 2$ V.

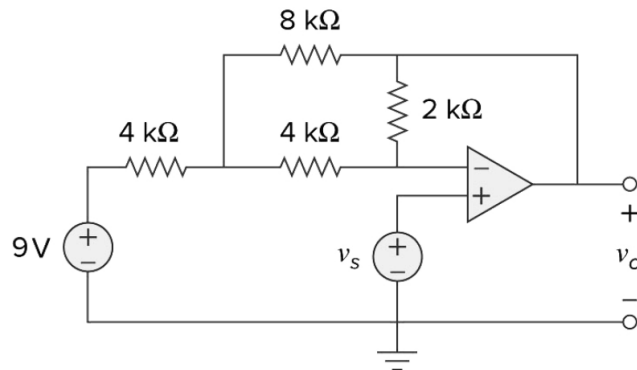


Figure 1

Answer: $v_o = 0.727$ V

Q2 (2021 T1 Final Exam Q3a)

Resistance temperature detectors (RTDs) are sensors used to measure temperature based on the resistance change. The most common type (PT100) has a resistance of $100\ \Omega$ at 0°C and $138.4\ \Omega$ at 100°C . The circuit shown in Figure 2 is used to convert the information from the RTD into something meaningful for an analog-to-digital converter (ADC).

- Calculate the voltage v_o as a function of v_{in} when the RTD has a value of $130\ \Omega$.
- How large can be the value of v_{in} before the amplifier saturates?

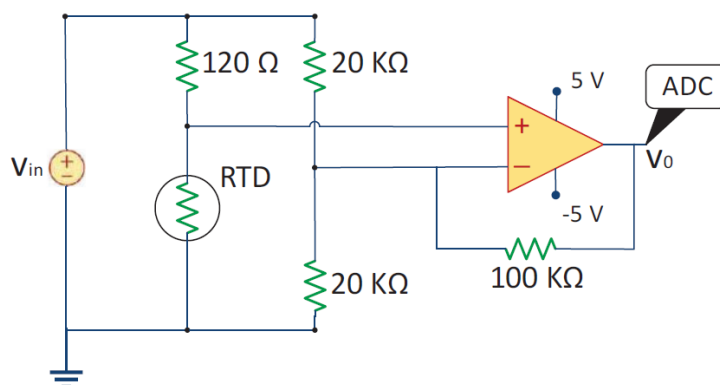


Figure 2

Answers: i) $v_o = 0.72v_{in}$, ii) $|v_{in}| = 6.94$ V

Q3 (2023 T1 Final Exam Q3a)

For the circuit shown in Figure 3,

i) Find i_a .

ii) Find the value of the right voltage source (i.e., v_2) for which $i_a = 0$.

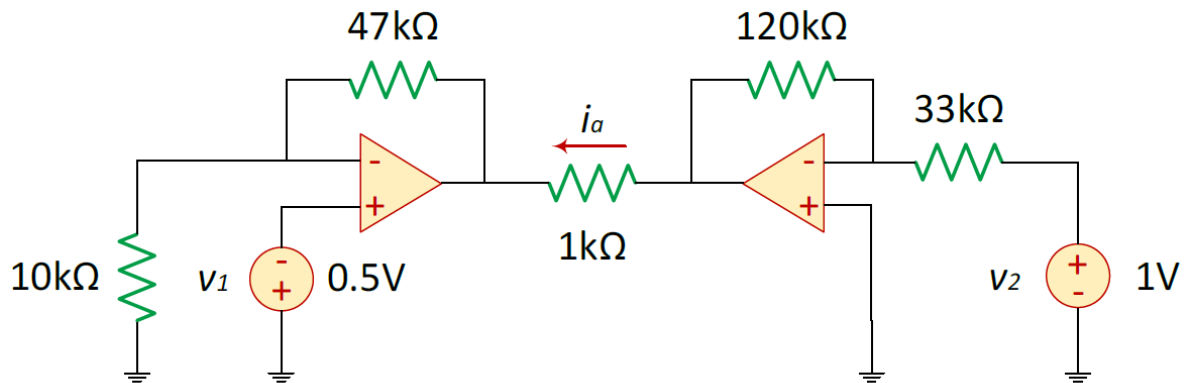


Figure 3

Answers: i) $i_a = -0.79 \text{ mA}$, ii) $v_2 = 0.783 \text{ V}$.

Q4 (2022 T1 Final Exam Q3a)

Calculate i_o in the op amp circuit shown in Figure 4.

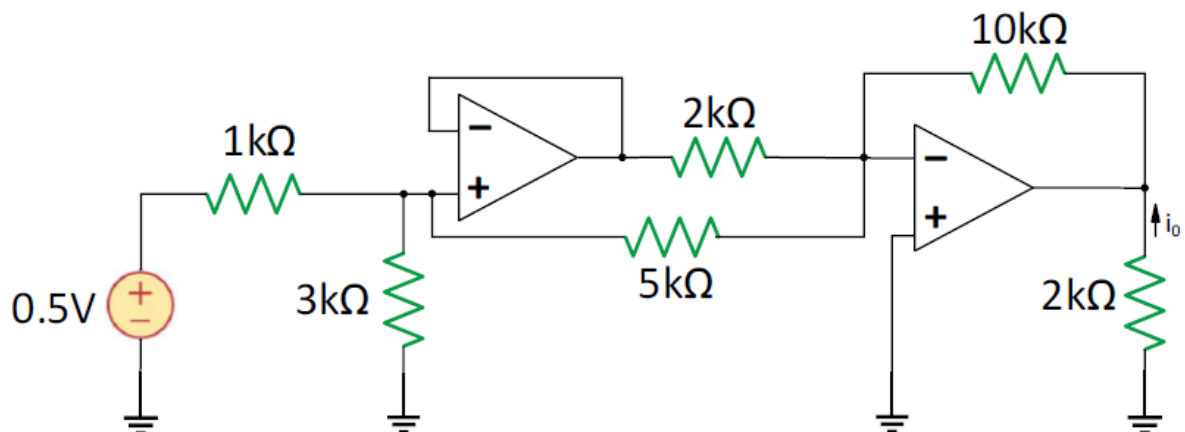


Figure 4

Answer: $i_o = 1.141 \text{ mA}$