

Topic 8: AC Circuits II

1. Write nodal equations for the following circuits:

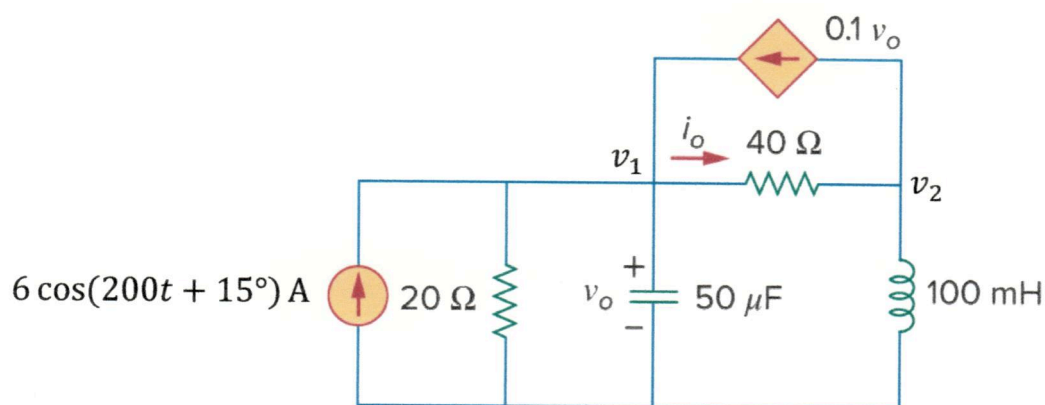


Fig. 1

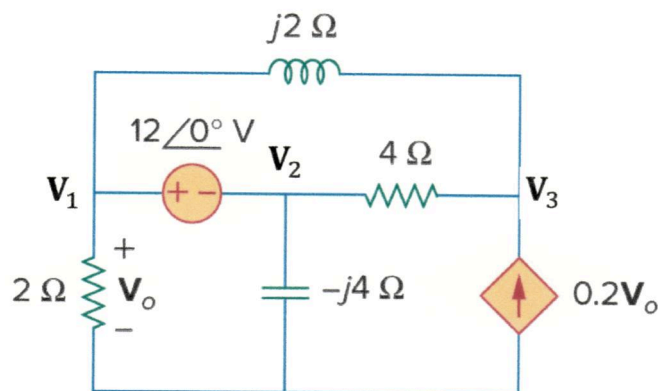


Fig. 2

Answer:

a) Fig. 1:
$$\begin{cases} (-2.5 + j1)V_1 - 2.5V_2 = 579.5 + j155.3 \\ 3V_1 + (1 - j2)V_2 = 0 \end{cases}$$

b) Fig. 2:
$$\begin{cases} (2 - j2)V_1 + (1 + j)V_2 + (-1 + j2)V_3 = 0 \text{ V} \\ (0.8 - j2)V_1 + V_2 + (-1 + j2)V_3 = 0 \text{ V} \\ V_1 - V_2 = 12 \end{cases}$$

Solution: Transform the circuit into phasor domain


$$\omega = 200 \text{ rad/s}$$

$$6 \angle (200t + 15^\circ) \text{ A} = 6 \angle 15^\circ \text{ A}$$

$$100 \text{ mH} \rightarrow j\omega L = j20 \Omega \rightarrow 6 \angle 15^\circ \text{ A}$$

$$50 \text{ } \mu\text{F} \rightarrow -j \frac{1}{\omega C} = -j100 \Omega$$

Note that $V_0 = V_1$

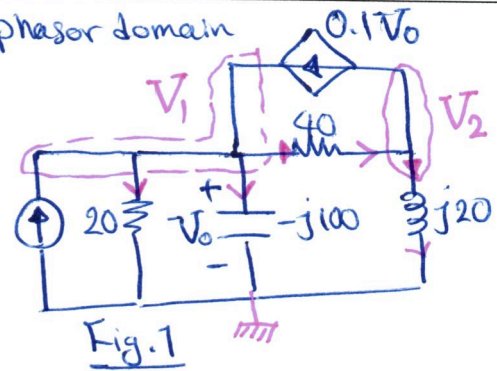

*KCL @ node 1: $6 \angle 15^\circ + 0.1V_0 = \frac{V_1}{20} + \frac{V_1}{-j100} + \frac{V_1 - V_2}{40} \xrightarrow{\times 100}$

$$600 \angle 15^\circ + 10V_1 = 5V_1 + jV_1 + 2.5V_1 - 2.5V_2$$

Transfer to Polar form

$$(-2.5 + j1)V_1 - 2.5V_2 = \frac{600 \angle 15^\circ}{579.5} + j \frac{600 \sin 15^\circ}{155.3}$$

*KCL @ node 2: $\frac{V_1 - V_2}{40} = 0.1V_1 + \frac{V_2}{j20} \xrightarrow{\times 40} V_1 - V_2 = 4V_1 - j2V_2$
 $\Rightarrow 3V_1 + (1 - j2)V_2 = 0$


We have a supernode between V_1 and V_2

Note that $V_0 = V_1$

*KCL @ supernode:

$$\frac{V_3 - V_2}{4} = \frac{V_2}{-j4} + \frac{V_1}{2} + \frac{V_1 - V_3}{j2} \xrightarrow{\times 4} V_3 - V_2 = jV_2 + 2V_1 - j2V_1 + j2V_3$$
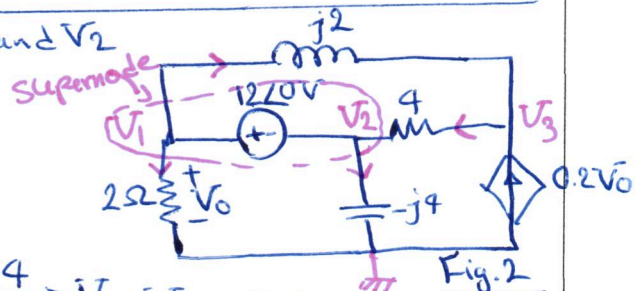
$$\Rightarrow (2 - j2)V_1 + (1 + j)V_2 + (-1 + j2)V_3 = 0$$



*KCL @ node 3:

$$0.2V_1 + \frac{V_1 - V_3}{j2} = \frac{V_3 - V_2}{4} \xrightarrow{\times 4} 0.8V_1 - j2V_1 + j2V_3 = V_3 - V_2$$

$$(0.8 - j2)V_1 + V_2 + (-1 + j2)V_3 = 0$$

*Extra equation due to supernode (Voltage Source)

$$V_1 - V_2 = 12$$

2. Write mesh equations for the following circuits:

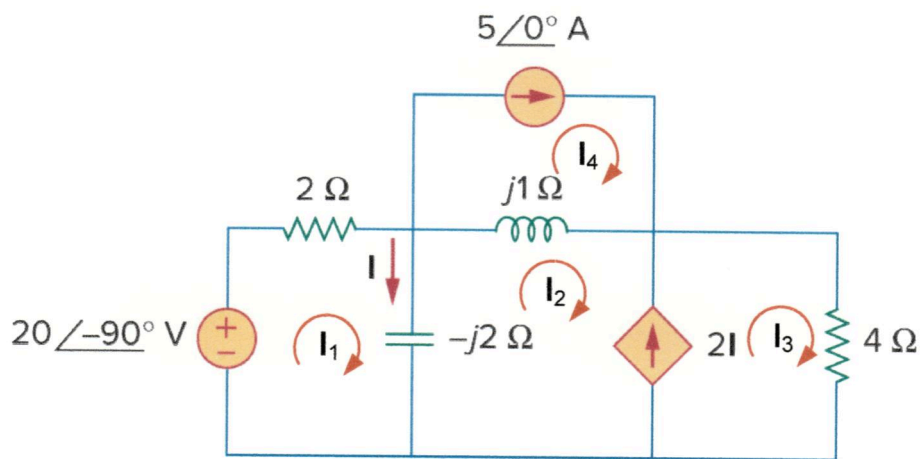


Fig. 1

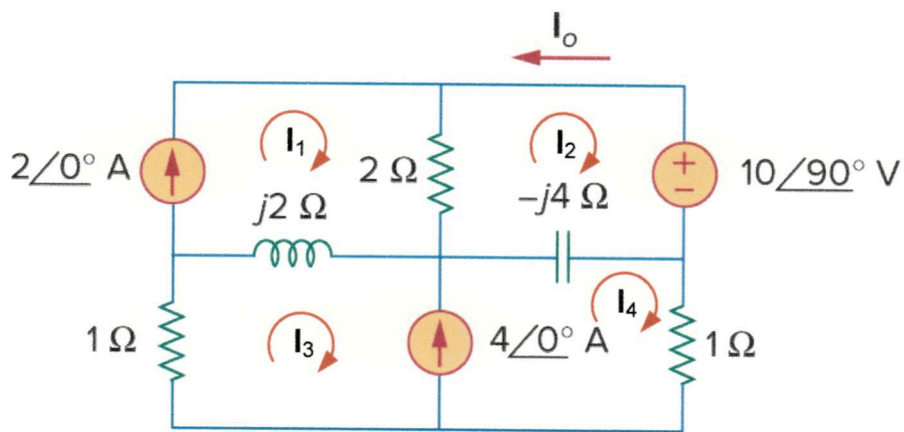


Fig. 2

Answer:

a) Fig. 1:
$$\begin{cases} (1-j)I_1 + jI_2 = -j10 \\ j2I_1 - jI_2 + 4I_3 = j5 \\ 2I_1 - I_2 - I_3 = 0 \\ I_4 = 5 \end{cases}$$

b) Fig. 2:
$$\begin{cases} I_1 = 2 \\ (1-j2)I_2 + j2I_4 = 2-j5 \\ j4I_2 + (1+j2)I_3 + (1-j4)I_4 = j4 \\ I_3 - I_4 = -4 \end{cases}$$

Solution: We have a supermesh between I_2 and I_3 :


$$I_4 = 5A$$

* KVL in mesh 1:

$$j20 + 2I_1 + (-j2)(I_1 - I_2) = 0$$

$$\Rightarrow j10 + I_1 - jI_1 + jI_2 = 0$$

$$\Rightarrow (1 - j)I_1 + jI_2 = -j10$$

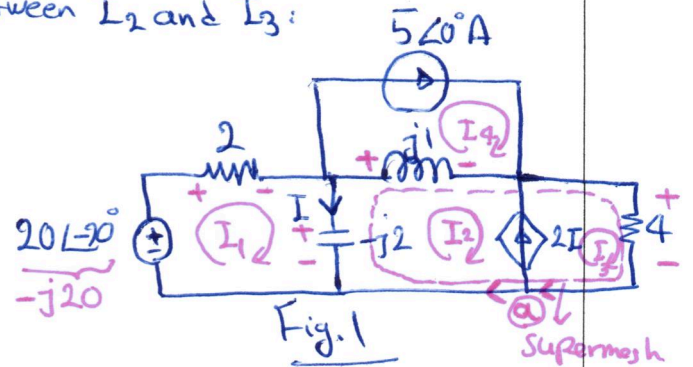

* KVL in Supermesh: $-(-j2)(I_1 - I_2) + j1(I_2 - I_4) + 4I_3 = 0$

$$\Rightarrow j2I_1 - j2I_2 + jI_2 - j5 + 4I_3 = 0$$

$$\Rightarrow j2I_1 - jI_2 + 4I_3 = j5$$

* KCL @ node a: $I_3 = 2I_1 + I_2$ Note that $I = I_1 - I_2 \rightarrow I_3 = 2I_1 - 2I_2 + I_2$

$$\Rightarrow 2I_1 - I_2 - I_3 = 0$$

Clearly in Fig. 2 $\rightarrow I_1 = 2A$


and we have supermesh again

* KVL in mesh 2:

$$j10 + (-j4)(I_2 - I_4) + 2(I_2 - I_1) = 0$$

$$-j4I_2 + j4I_4 + 2I_2 = 4 - j10 \xrightarrow{\times 1/2}$$
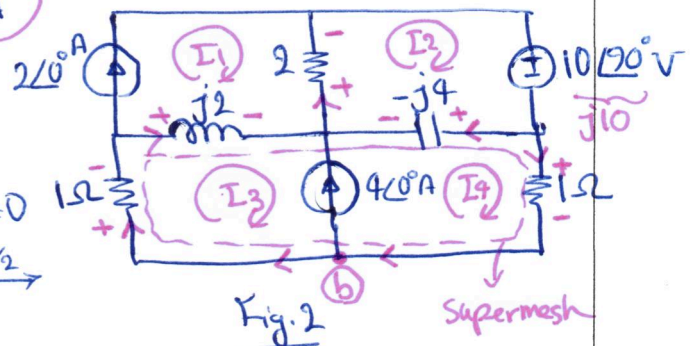
$$\Rightarrow (1 - j2)I_2 + j2I_4 = 2 - j5$$



* KVL in Supermesh: $1I_3 + j2(I_3 - I_1) - (-j4)(I_2 - I_4) + 1I_4 = 0$

$$\Rightarrow I_3 + j2I_3 - j4 + j4I_2 - j4I_4 + I_4 = 0$$

$$\Rightarrow j4I_2 + (1 + j2)I_3 + (1 - j4)I_4 = j4$$

* KCL @ node b

$$I_4 = 4 + I_3 \Rightarrow I_3 - I_4 = -4$$

3. Use superposition principle to find i_x and v_x in the following circuits

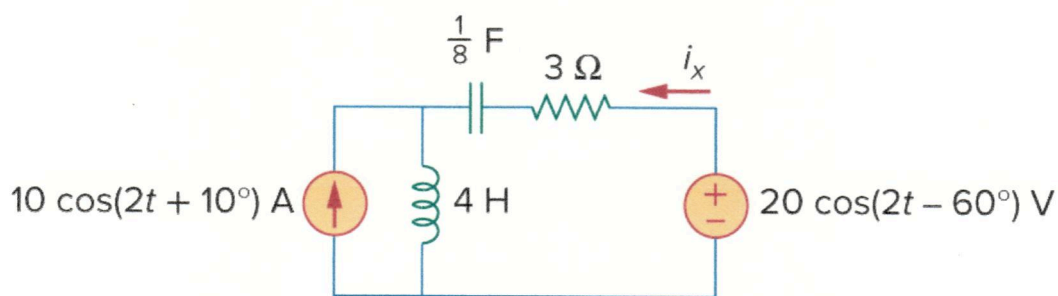


Fig. 1

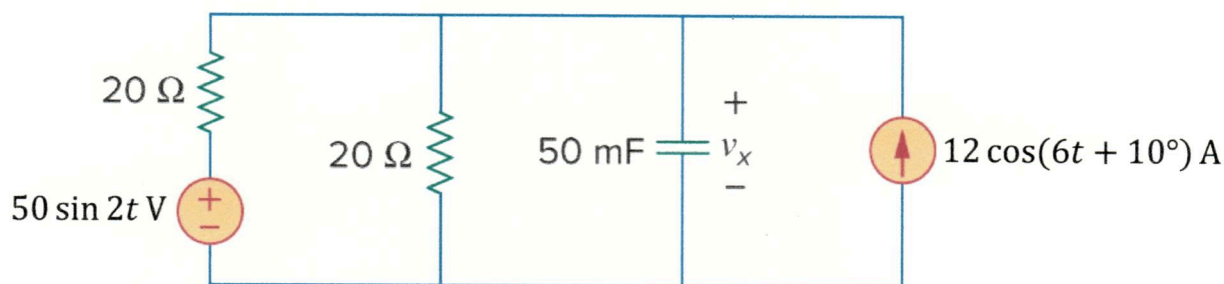


Fig. 2

Answer:

a) Fig. 1: $i_x(t) = 19.804 \cos(2t - 129.17^\circ) \text{ A}$

b) Fig. 2: $v_x(t) = [17.678 \cos(2t - 135^\circ) + 37.95 \cos(6t - 61.57^\circ)] \text{ V}$

Solution: For Fig. 1, transform it into phasor domain and Note that Frequencies are the same.

$\omega = 2 \text{ rad/s}$

$10 \cos(2t + 10^\circ) \rightarrow 10 \angle 10^\circ \text{ A}$

$20 \cos(2t - 60^\circ) \rightarrow 20 \angle -60^\circ \text{ V}$


$4 \text{ H} \rightarrow j\omega L = j8 \Omega$

$\frac{1}{8} \text{ F} \rightarrow \frac{-j}{\omega C} = -j4 \Omega$

$\Rightarrow I_x = I_{x1} + I_{x2}$


$\begin{cases} I_{x1}: \text{due to } 20 \angle -60^\circ \text{ V} \\ I_{x2}: \text{due to } 10 \angle 10^\circ \text{ A} \end{cases}$

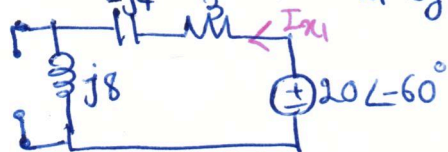Draw the circuit for I_{x1} by setting $10 \angle 10^\circ \text{ A}$ to zero



All impedances are in series $\rightarrow$

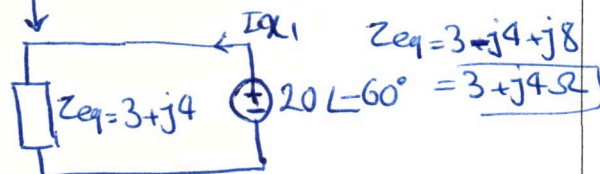$\Rightarrow I_{x1} = \frac{20 \angle -60^\circ}{3 + j4} \text{ A}$




$I_{x1} = -1.57 - j3.67 \text{ A}$

Keep it in rectangular form as it is going to be added to I_{x2} later.

$\rightarrow$ next page

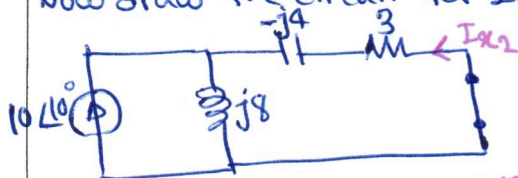Now draw the circuit for I_{x2} by turning off $20\angle 60^\circ V$



Note that we can use current division but I_{x2} will be in opposite direction

$$\Rightarrow I_{x2} = - \frac{j8 \angle 80^\circ}{3 - 4j + j8} \times 10 \angle 10^\circ = \frac{8 \angle -90^\circ \times 10 \angle 10^\circ}{3 + j4} = \frac{80 \angle -80^\circ}{3 + j4}$$

$$\Rightarrow I_{x2} = -10.93 - j11.67 A$$

$$\text{Thus } I_x = I_{x1} + I_{x2} = -12.51 - j15.35 = 19.8 \angle -129.17^\circ A$$

Note that we are allowed to add I_{x1} and I_{x2} in phasor domain because they are due to sources with same frequency

$$\Rightarrow i_x(t) = 19.8 \cos(2t - 129.17^\circ) A$$

For Fig. 2, Note that frequencies are NOT the same.

Thus $V_x = V_{x1} + V_{x2}$ but $V_x \neq V_{x1} + V_{x2}$ in phasor domain


V_{x1} due to $50 \sin 2t V$

V_{x2} due to $12 \cos(6t + 10^\circ) A$

* Draw the circuit in phasor domain for $V_{x1} \rightarrow 50 \sin 2t = 50 \cos(2t - 90^\circ) \rightarrow 50 \angle -90^\circ$
by setting the current source to zero

$$\omega = 2 \text{ rad/s}$$
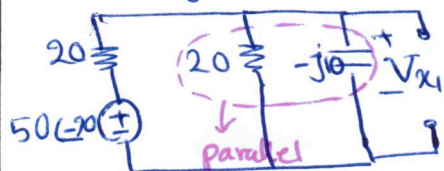
$$50 \text{ mF} \rightarrow \frac{-j}{\omega C} = -j10 \Omega$$




Voltage division

$$V_{x1} = \frac{4 - j8}{20 + 4 - j8} \times 50 \angle -90^\circ V$$

$$20 \parallel -j10 = \frac{20 \times (-j10)}{20 - j10} = 4 - j8 \Omega$$

$$\Rightarrow V_{x1} = 17.67 \angle -135^\circ V \rightarrow v_{x1} = 17.67 \cos(2t - 135^\circ) V$$

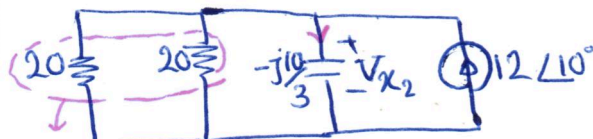
* Draw the circuit in phasor domain for $V_{x2} \rightarrow \omega = 6 \text{ rad/s}$



Parallel $20 \parallel 10 = 10 \Omega$

$$12 \cos(6t + 10^\circ) \rightarrow 12 \angle 10^\circ$$
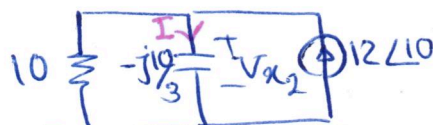
$$50 \text{ mF} \rightarrow \frac{-j}{\omega C} = -j10/3 \Omega$$



Current division


$$I = \frac{10}{10 - j10/3} \times 12 \angle 10^\circ = 11.38 \angle 28.4^\circ A$$

$$\rightarrow v_{x2}(t) = 37.95 \cos(6t - 61.5^\circ) V$$

$$V_{x2} = -j10/3 \times I = 37.95 \angle -61.5^\circ$$


$$\Rightarrow v_x = v_{x1} + v_{x2} = [17.67 \cos(2t - 135^\circ) + 37.95 \cos(6t - 61.5^\circ)] V$$

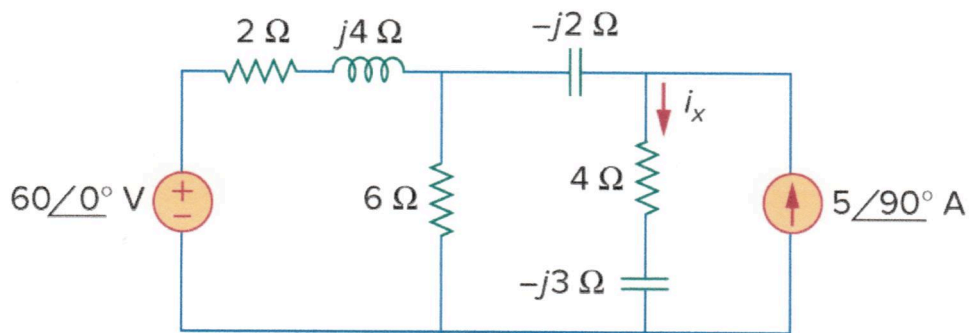4. Use source transformation to find I_x in the following circuit.




Answer: $I_x = 5.238\angle 17.35^\circ \text{ A}$


Solution:

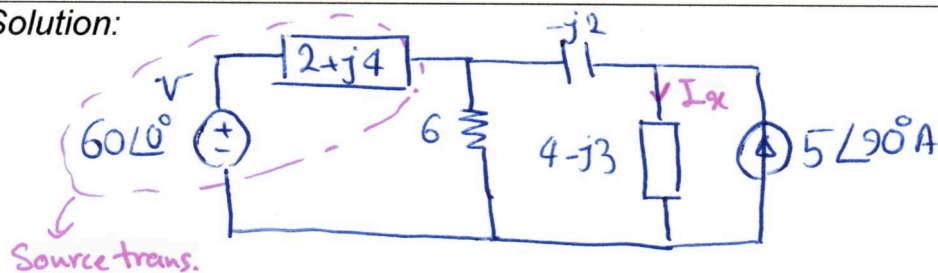
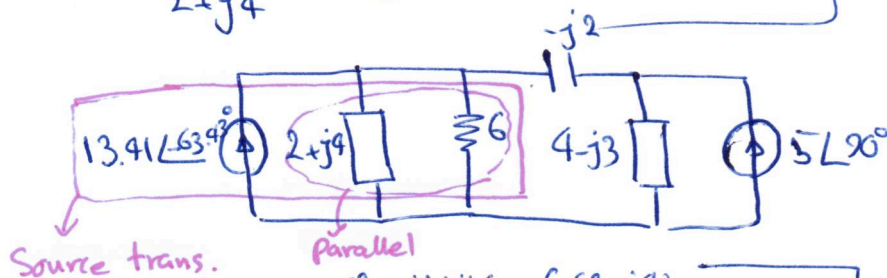
$$I_{S_1} = \frac{60\angle 0^\circ}{2+j4} = 6-j12 = 13.41\angle -63.43^\circ \text{ A}$$



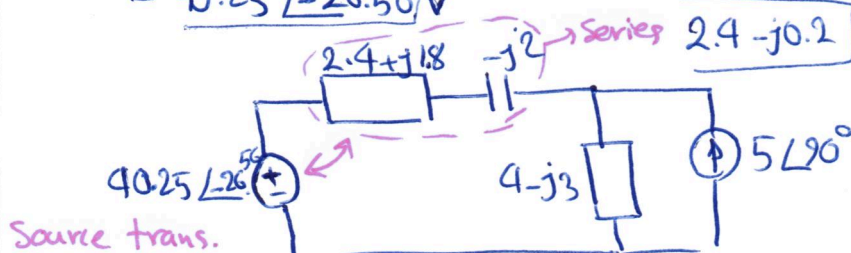
$$V_s = (2.4 + j1.8) \times 13.41\angle -63.43^\circ = 40.25\angle -26.56^\circ \text{ V}$$



$$I_{S_2} = \frac{40.25\angle -26.56^\circ}{2} = 20.125\angle -26.56^\circ \text{ A}$$


→ next page

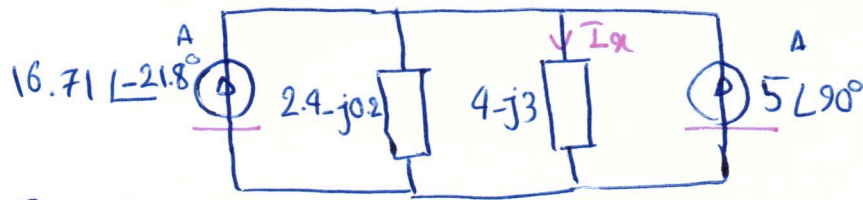

Current Sources have the same direction and connected to the same nodes
So add them

$$I_{S_3} = 16.71 \angle -21.8^\circ + 5 \angle 90^\circ = 15.56 \angle -4.44^\circ \text{ A}$$


use rectangular form

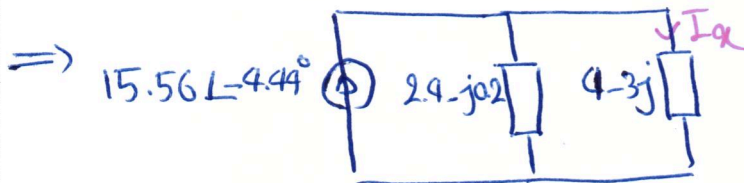

Using current division:
$$I_x = \frac{2.4 - j0.2}{4 - j3 + 2.4 - j0.2} \times I_{S_3}$$

$$= 5.23 \angle 17.3^\circ \text{ A}$$


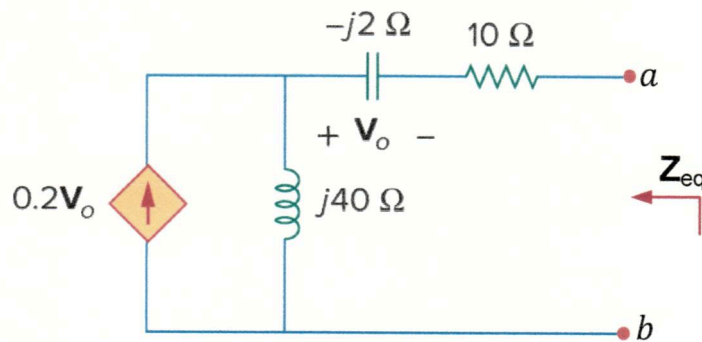
5. Calculate the equivalent impedance of the following circuit from the terminals a-b.



Answer: $Z_{eq} = -6 + j38 \Omega$.

Solution: Due to having one dependent current source and no independent source, we must connect an external source.

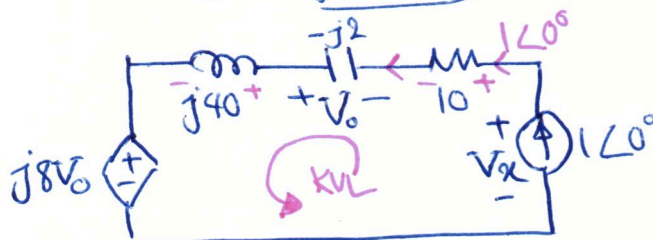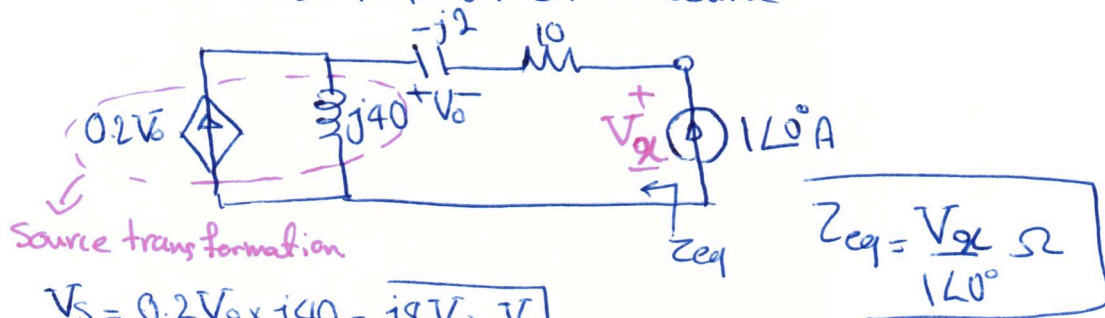Here we use a $1\angle 0^\circ$ A phasor current source




*KVL: $-\bar{V}_x + 10 \times 1\angle 0^\circ - \bar{V}_o + j40 \times 1\angle 0^\circ + j8V_o = 0$

Note that $V_o = -(-j2) \times 1\angle 0^\circ = j2 \text{ V}$ (polarity and direction are opposite of passive sign convention).

$\Rightarrow \bar{V}_x = 10 - j2 + j40 + j16$


$= -6 + j38 \text{ V} \Rightarrow Z_{eq} = \frac{-6 + j38}{1} = -6 + j38 \Omega$

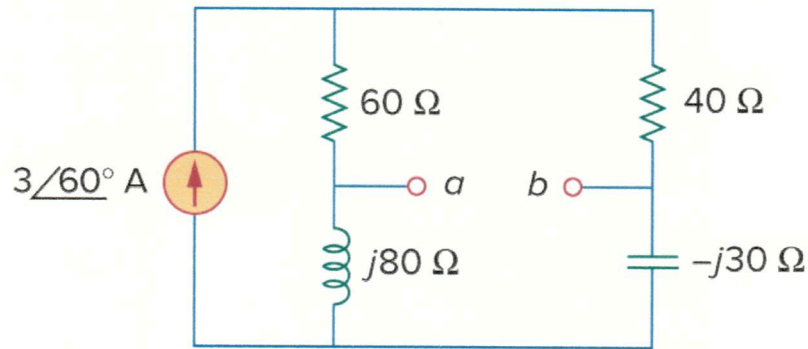6. For the following circuit, find the Thevenin and Norton equivalent circuits



Answer: $Z_{eq} = 20 + j40 \Omega = 44.72 \angle 63.43^\circ \Omega$, $V_{Th} = 134 \angle 123.4^\circ V$,
 $I_N = 3 \angle 60^\circ A$

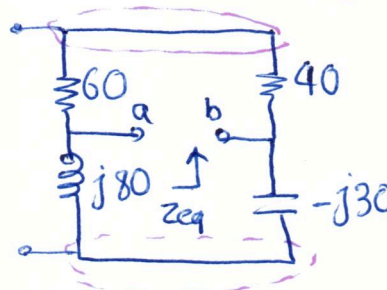Solution: First find $Z_{Th} = Z_{eq} = Z_N$ by setting all independent sources to zero:



$$\begin{cases} 60 \Omega \text{ in series with } 40 \Omega \\ j80 \Omega \text{ in series with } -j30 \Omega \end{cases}$$

$$60 + 40 = 100 \Omega$$

$$+j80 - j30 = j50 \Omega$$


$\Rightarrow$

acts like inductor $\leftarrow j50$

$$Z_{eq} \Rightarrow Z_{eq} = 100 \parallel j50 = \frac{100 \times j50}{100 + j50}$$

$$\Rightarrow Z_{eq} = 20 + j40 \Omega = 44.72 \angle 63.43^\circ \Omega = Z_{Th} = Z_N$$

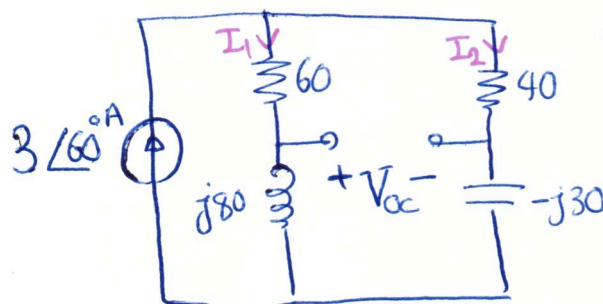In this circuit, it is easier to find V_{Th} and then $I_N = \frac{V_{Th}}{Z_{Th}}$



$$V_{Th} = V_{op}$$

Use current division:


$$I_1 = \frac{40 - j30}{60 + j80 + 40 - j30} \times 3 \angle 60^\circ$$

$\rightarrow$ next page for I_2

$$I_2 = \frac{60 + j80}{40 + j30 + 60 + j80} \times 3 \angle 60^\circ$$

$$\Rightarrow \begin{cases} I_1 = \frac{40 - j30}{100 + j50} \times 3 \angle 60^\circ \\ I_2 = \frac{60 + j80}{100 + j50} \times 3 \angle 60^\circ \end{cases} \rightarrow \begin{aligned} I_1 &= 1.34 - j0.08 \text{ A} \\ &= 1.34 \angle -3.43^\circ \text{ A} \\ I_2 &= 0.16 + j2.67 \text{ A} \\ &= 2.68 \angle 86.56^\circ \text{ A} \end{aligned}$$

Now write KVL:

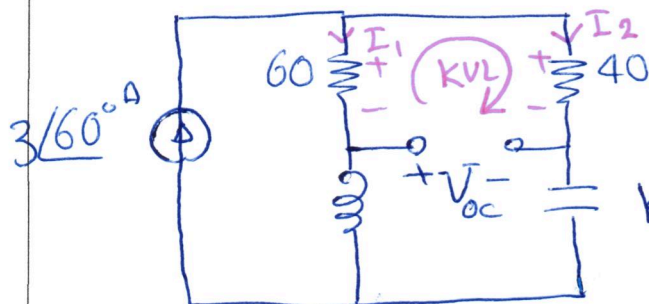



use rectangular form for I_1 and I_2 as in KVL they are being multiplied by a real number and being added.

$$\text{KVL: } -V_{oc} - 60I_1 + 40I_2 = 0$$


$$\Rightarrow V_{oc} = -60(1.34 - j0.08) + 40(0.16 + j2.67)$$

$$\Rightarrow V_{oc} = V_{Th} = -74 + j111.6 \text{ V} = 134 \angle 123.4^\circ$$
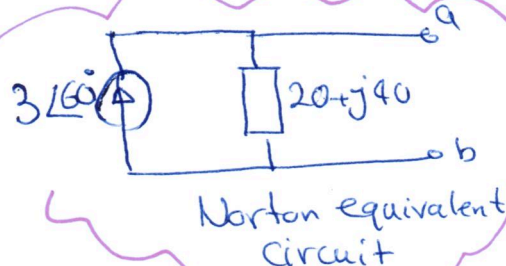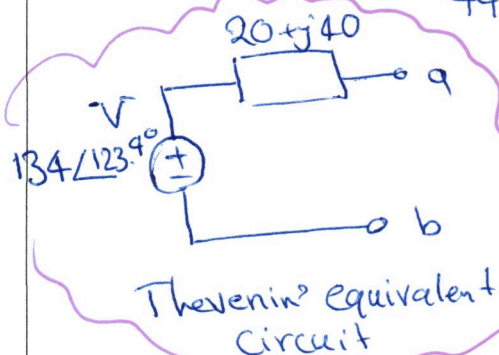
$$\text{Thus } I_N = \frac{V_{Th}}{Z_{Th}} = \frac{134 \angle 123.4^\circ}{44.72 \angle 63.43^\circ} \approx 3 \angle 60^\circ \text{ A}$$




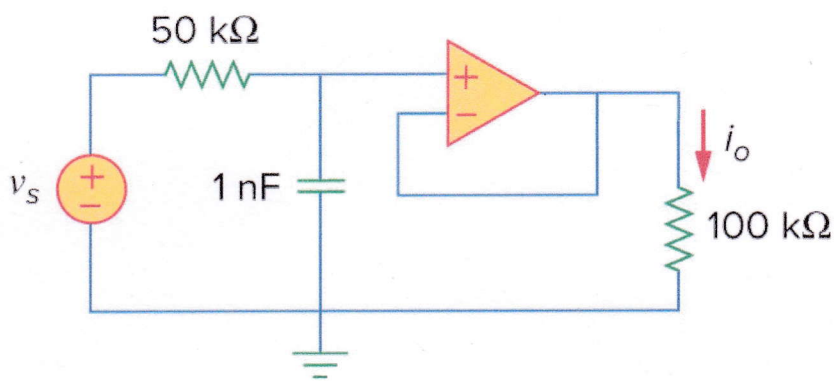7. Find $i_o(t)$ in the Op Amp circuit shown below if $v_s = 4 \cos(10^4 t)$ V



Answer: $i_o(t) = 35.78 \cos(10^4 t - 26.56^\circ) \mu\text{A}$

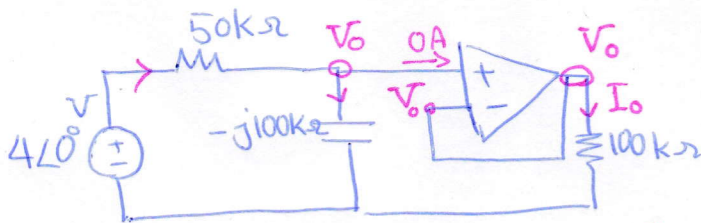Solution: Transform the circuit to phasor domain $v_s = 4 \cos(10^4 t) \rightarrow V_s = 4 \angle 0^\circ \text{ V}$
 $1 \text{ nF} \rightarrow -j \frac{1}{\omega C} \xrightarrow{\omega = 10^4 \text{ rad/s}} -j \frac{1}{10^4 \times 10^{-9}} = -j100 \text{ k}\Omega$
 $\Rightarrow$ negative feedback and ideal op amp $\Rightarrow V^- = V^+ = V_o$




KCL at non-inverting node: $\frac{4 - V_o}{50 \text{ k}} = \frac{j V_o}{j100 \text{ k}} \xrightarrow{\times 100 \text{ k}} 8 - 2V_o = j V_o$
 $\Rightarrow (2 + j) V_o = 8 \Rightarrow V_o = \frac{8}{2 + j} = 3.578 \angle -26.56^\circ \text{ V}$

$\Rightarrow I_o = \frac{V_o}{100 \text{ k}} = 35.78 \angle -26.56^\circ \mu\text{A}$


$\Rightarrow i_o(t) = 35.78 \cos(10^4 t - 26.56^\circ) \mu\text{A}$

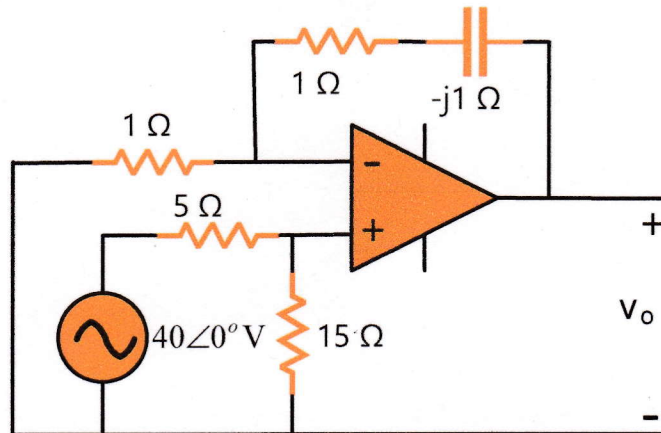8. (Final Exam – Summer, 2016-17) For the circuit shown in below, calculate the output voltage V_o .



Answer: $V_o = 67.08\angle(-26.56^\circ) \text{ V} = 60 - j30 \text{ V}$

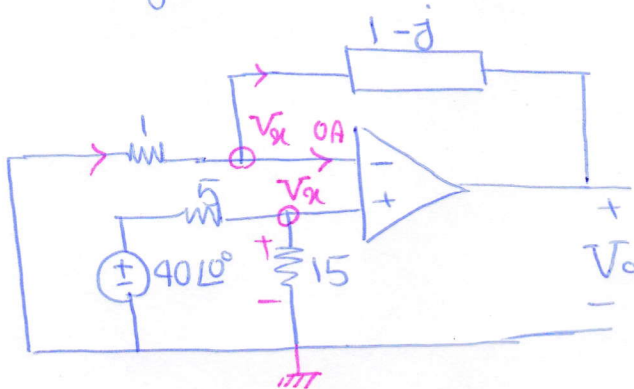
Solution: Negative feedback and ideal op amp $\rightarrow V^- = V^+$



Find V_x using voltage division at non-inverting node:

$$V_x = \frac{15}{5+15} \times 40\angle 0^\circ = 30\angle 0^\circ \text{ V}$$

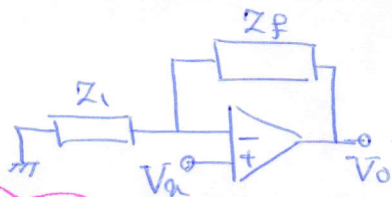Now we can use either Nodal analysis or non-inverting amplifier formula because



$$\begin{cases} Z_f = 1-j \Omega \\ Z_i = 1 \Omega \end{cases}$$

$$\frac{V_o}{V_x} = \left(1 + \frac{Z_f}{Z_i}\right) \Rightarrow V_o = (1 + 1-j) 30\angle 0^\circ$$


$$\Rightarrow V_o = 60 - j30 \text{ V} = 67.08\angle -26.56^\circ \text{ V}$$

Using Nodal analysis by writing KCL at inverting node:

$$\frac{0 - V_x}{1} = \frac{V_x - V_o}{1-j} \Rightarrow -(1-j)V_x = V_x - V_o \rightarrow V_o = (1-j)V_x + V_x$$

$$\Rightarrow V_o = (2-j)V_x = (2-j)30\angle 0^\circ = 60 - j30 \text{ V} = 67.08\angle -26.56^\circ \text{ V}$$

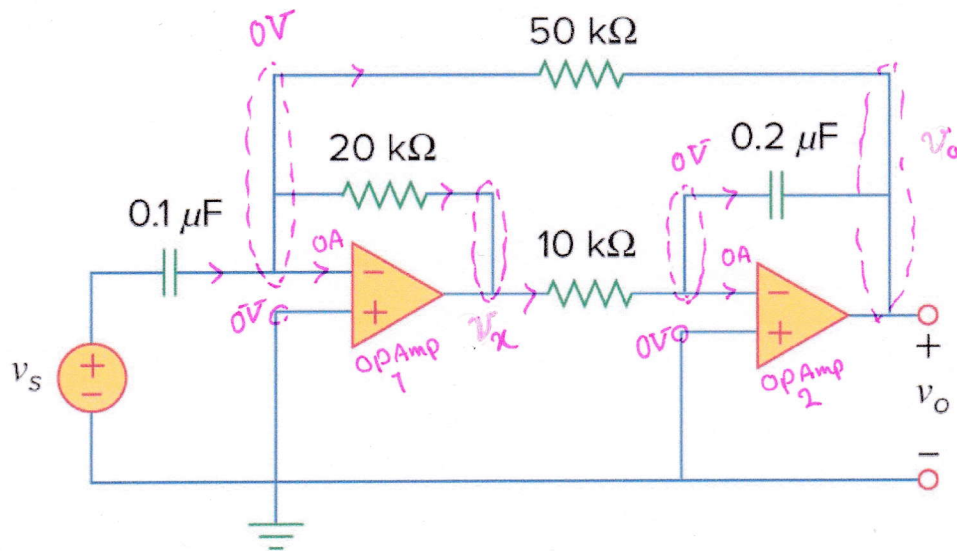9. Calculate $v_o(t)$ for the Op Amp circuit shown below if $v_s = 12 \cos(10^3 t - 60^\circ) \text{ V}$




Answer: $v_o(t) = 11.767 \cos(10^3 t - 71.31^\circ) \text{ V}$

Solution: Draw the circuit in phasor domain

$$v_s = 12 \cos(10^3 t - 60^\circ) \rightarrow \bar{V}_s = 12 \angle -60^\circ \text{ V}$$

$$\omega = 10^3 \text{ rad/s} \rightarrow 0.1 \mu\text{F} \rightarrow \frac{-j}{\omega C} = -j10 \text{ k}\Omega$$
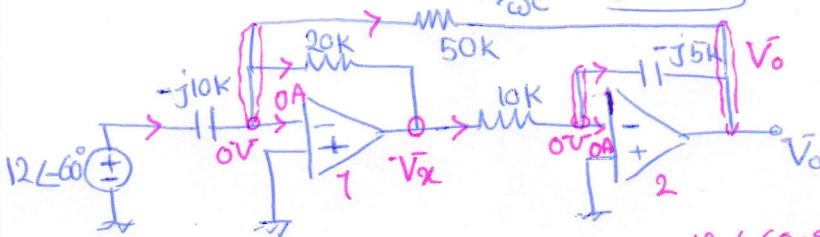
$$0.2 \mu\text{F} \rightarrow \frac{-j}{\omega C} = -j5 \text{ k}\Omega$$



* KCL at inverting node of Op Amp 1

$$\frac{j(12 \angle -60^\circ - 0)}{-j10} = \frac{0 - \bar{V}_x}{20\text{k}} + \frac{0 - \bar{V}_o}{50\text{k}} \times 100\text{k}$$

$$120 \angle 30^\circ = -5 \bar{V}_x - 2 \bar{V}_o \Rightarrow \bar{V}_x = -24 \angle 30^\circ - 0.4 \bar{V}_o \quad \text{--- (I)}$$

* KCL at inverting node of Op Amp 2

$$\frac{\bar{V}_x - 0}{10\text{k}} = \frac{j(0 - \bar{V}_o)}{-j5\text{k}} \times 10\text{k} \Rightarrow \bar{V}_x = -j2 \bar{V}_o \quad \text{--- (II)}$$

Substitute

$$\text{--- (II) } \rightarrow -j2 \bar{V}_o = -24 \angle 30^\circ - 0.4 \bar{V}_o \rightarrow \bar{V}_o = \frac{-24 \angle 30^\circ}{0.4 - j2} = \frac{24 \angle (30^\circ - 180^\circ)}{0.4 - j2}$$

$$\Rightarrow \bar{V}_o = 11.767 \angle -71.31^\circ \text{ V} \Rightarrow v_o(t) = 11.767 \cos(10^3 t - 71.31^\circ) \text{ V}$$