

Q1 (Sample exam question)

The circuit in Figure 1 is operating under DC steady state conditions.

- i) If $R = 10 \Omega$, determine the voltage across the capacitor, v_c , and the current through the inductor, i_L .
- ii) Calculate the energy stored in the capacitor and the inductor in this situation (i.e., when $R = 10 \Omega$).
- iii) Calculate the value of R that will make the energy stored in the capacitor the same as the energy stored in the inductor.

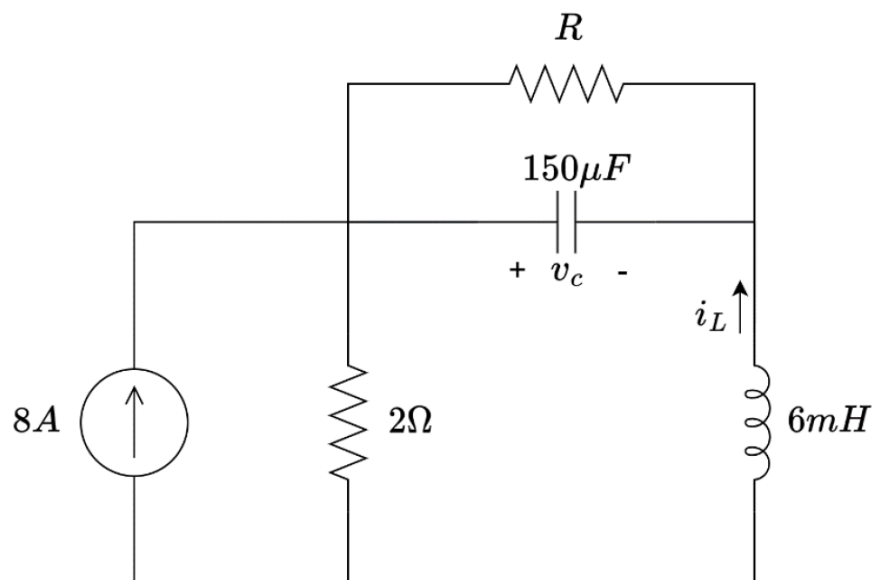


Figure 1

Answers: i) $v_c = 13.33 \text{ V}$, $i_L = -1.333 \text{ A}$, ii) $W_c = 0.0133 \text{ J}$, $W_L = 0.00533 \text{ J}$, iii) $R = 6.32 \Omega$

Q2 (2021 T1 Final Exam Q2b)

Switch 1 (SW1) in Figure 2 was in position a for a long time before moving to position b at $t=0$. After 0.1 seconds, the voltage source is disconnected from the circuit by opening Switch 2 (SW2).

- i) Calculate $i_0(t)$ for $0 \leq t < 0.1\text{s}$.
- ii) Calculate $i_0(t)$ for $t \geq 0.1\text{s}$.
- iii) Calculate the value of i_0 at $t = 0.2\text{s}$.

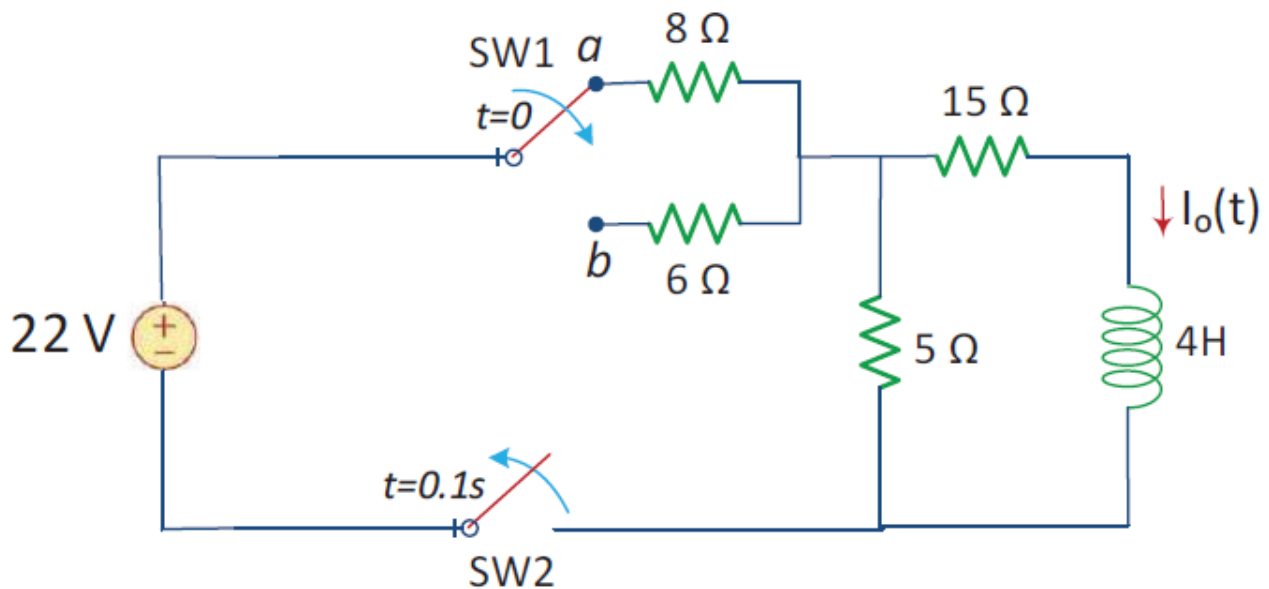


Figure 2

Answers: i) $i_0(t) = 0.564 - 0.096e^{-4.43t} \text{ A}$, ii) $i_0(t) = 0.5025e^{-5(t-0.1)} \text{ A}$, iii) $i_0(0.2) = 0.305 \text{ A}$

Q3 (2020 T1 Final Exam Q2a)

A magnetically controlled switch is called a relay. A relay is essentially an electromagnetic device used to open or close a switch that controls another circuit (see Figure 3(a)). The coil circuit is an RL circuit like that in Figure 3(b), where R and L are the resistance and inductance of the coil.

A certain relay has a resistance of 200Ω and an inductance of 500 mH . The relay contacts close when the current through the coil reaches 175 mA . What time elapses between the application of 110V to the coil (when S_1 closes at $t = 0$) and contact closure?

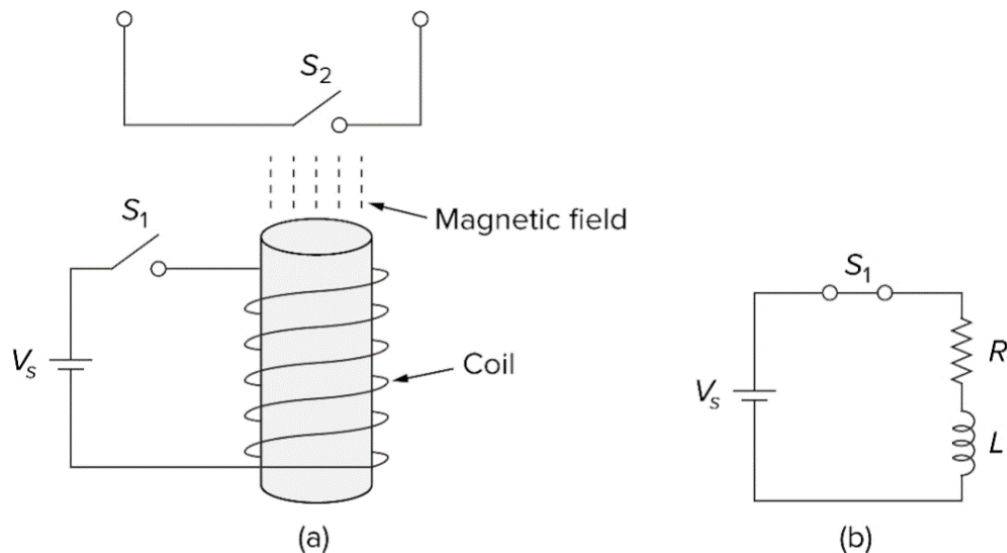


Figure 4

Answer: $957.5\text{ }\mu\text{s}$

Q4 (Sample exam question)

The switch in the RL circuit shown in Figure 4 was closed for a long time before opening at $t = 0\text{ s}$.

i) Derive the expression for $i_L(t)$ for $t \geq 0\text{ s}$.

ii) Calculate the value of $v_L(t)$ at $t = 5\text{ ms}$.

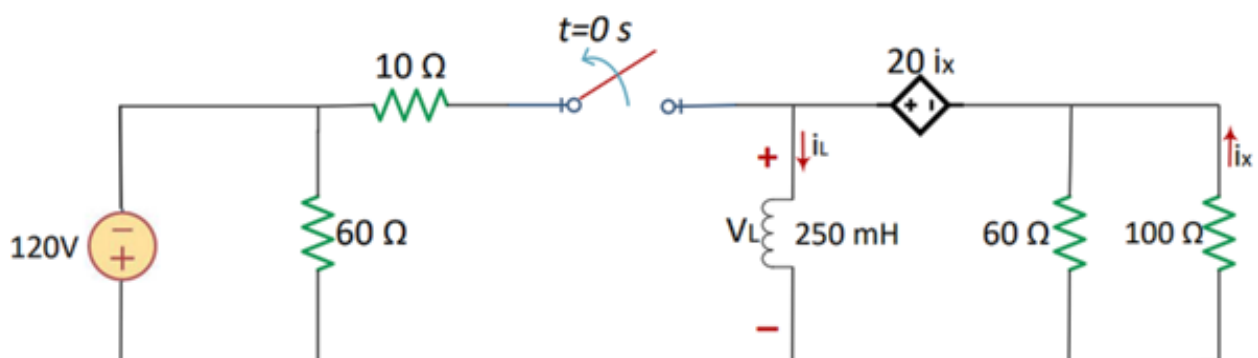


Figure 4

Answers: i) $i_L(t) = -12e^{-120t}\text{ A}$, ii) $v_L(t = 0.005) = 197.57\text{ V}$