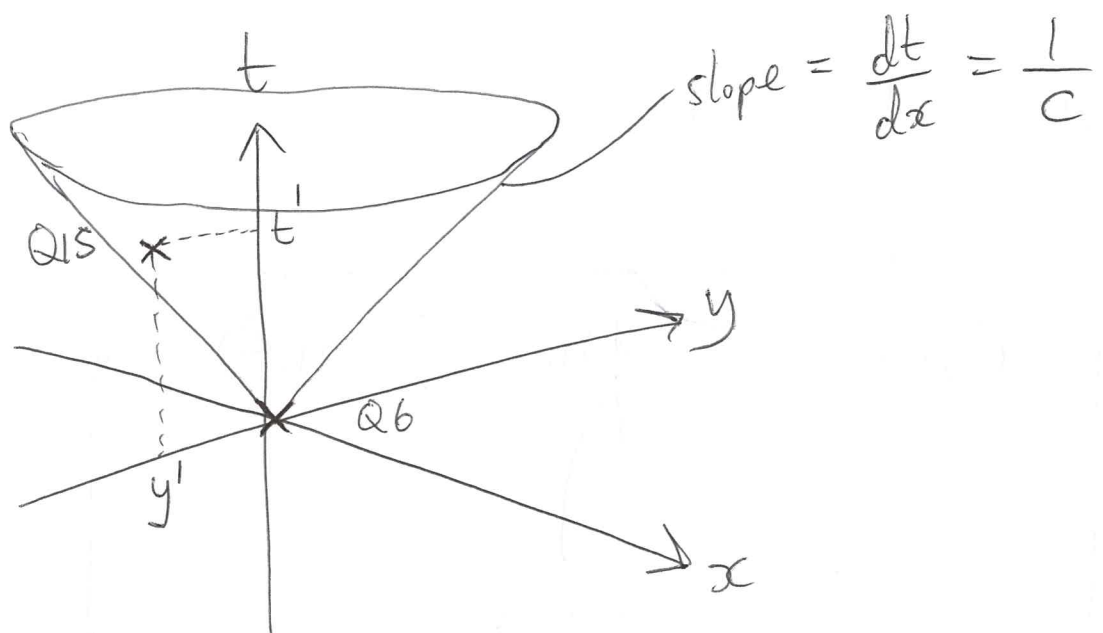





At $t=0$: Signal leaves $Q6$

At $t=t'$: Signal reaches $Q15$


$$y' \leq ct'$$

$$L_e = \frac{L}{cT} \ll 1 \Rightarrow \text{lumped elements relevant}$$


Distributed elements:

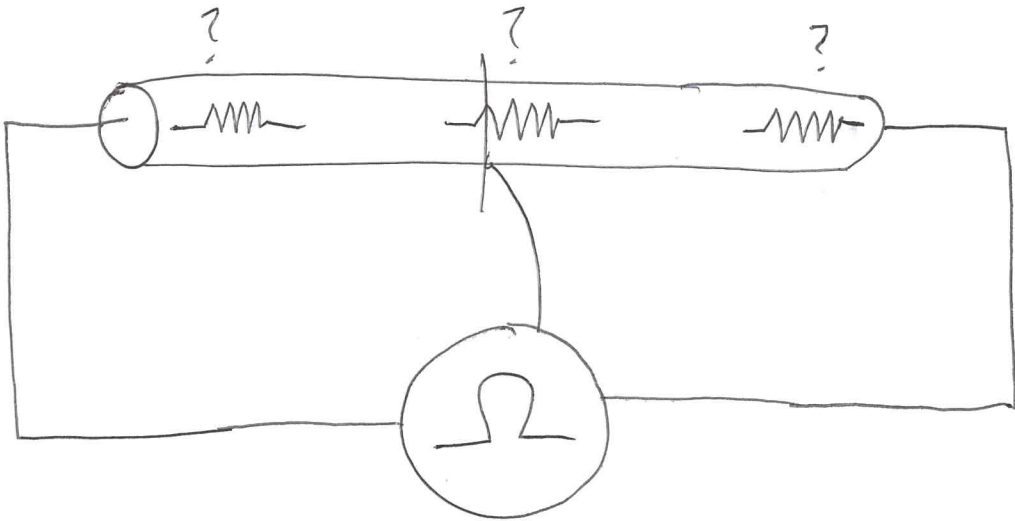

$$[R] = \frac{\Omega}{m}$$


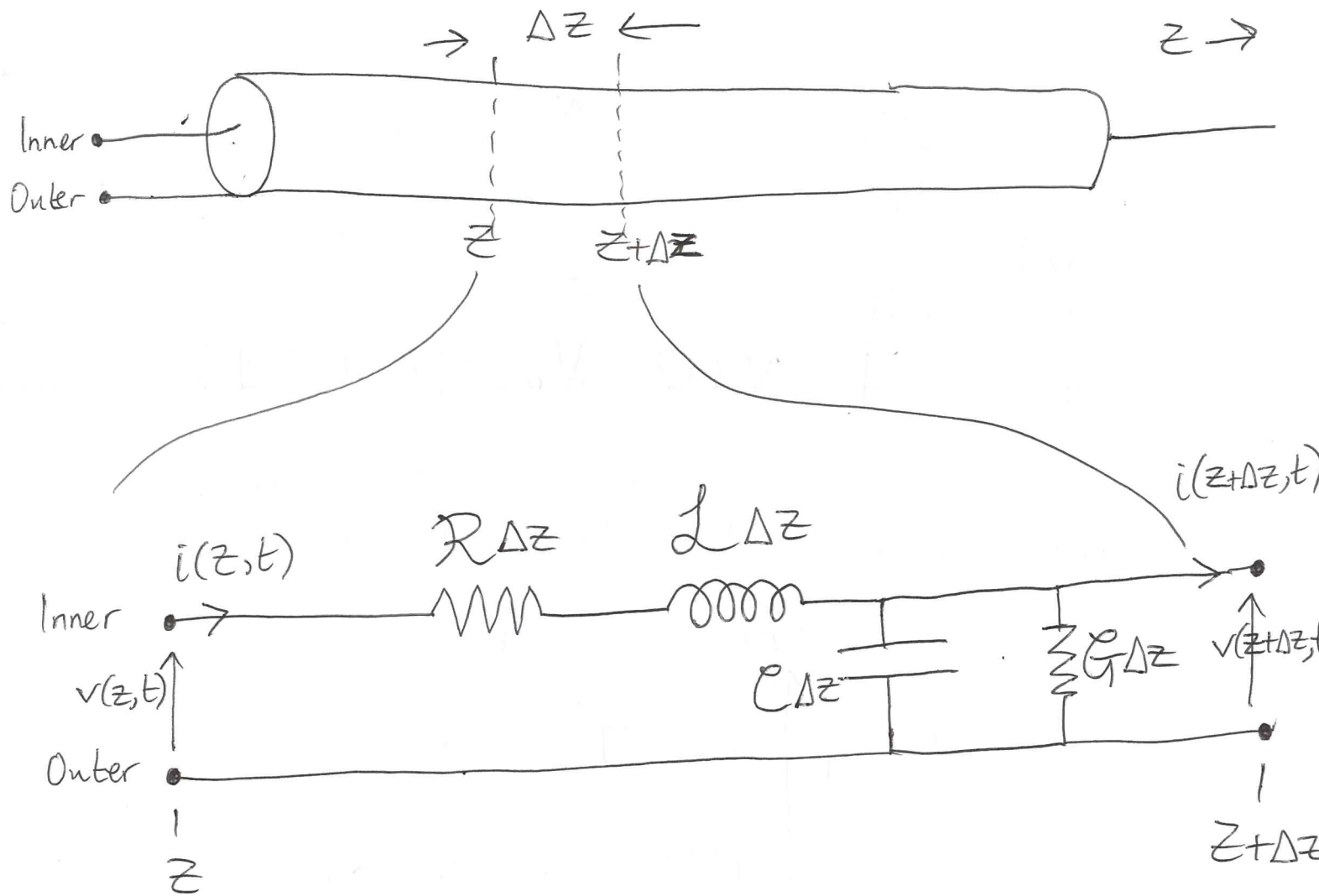


Perfect cable: $G = R = 0$

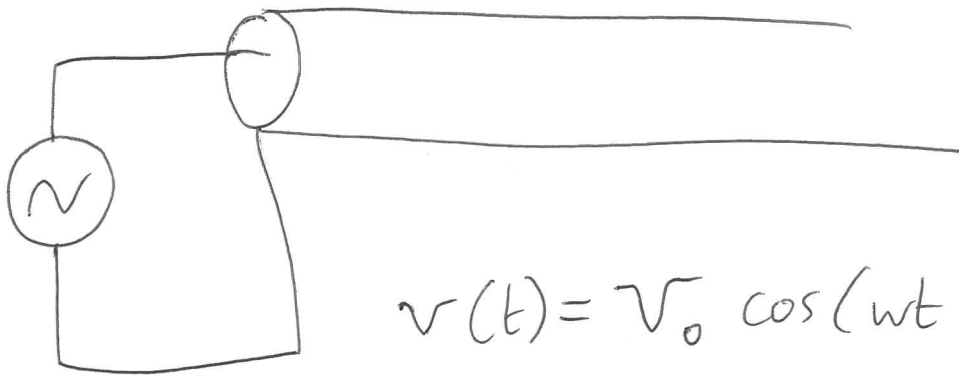

$$v(t) = V_0 \cos(\omega t + \phi)$$

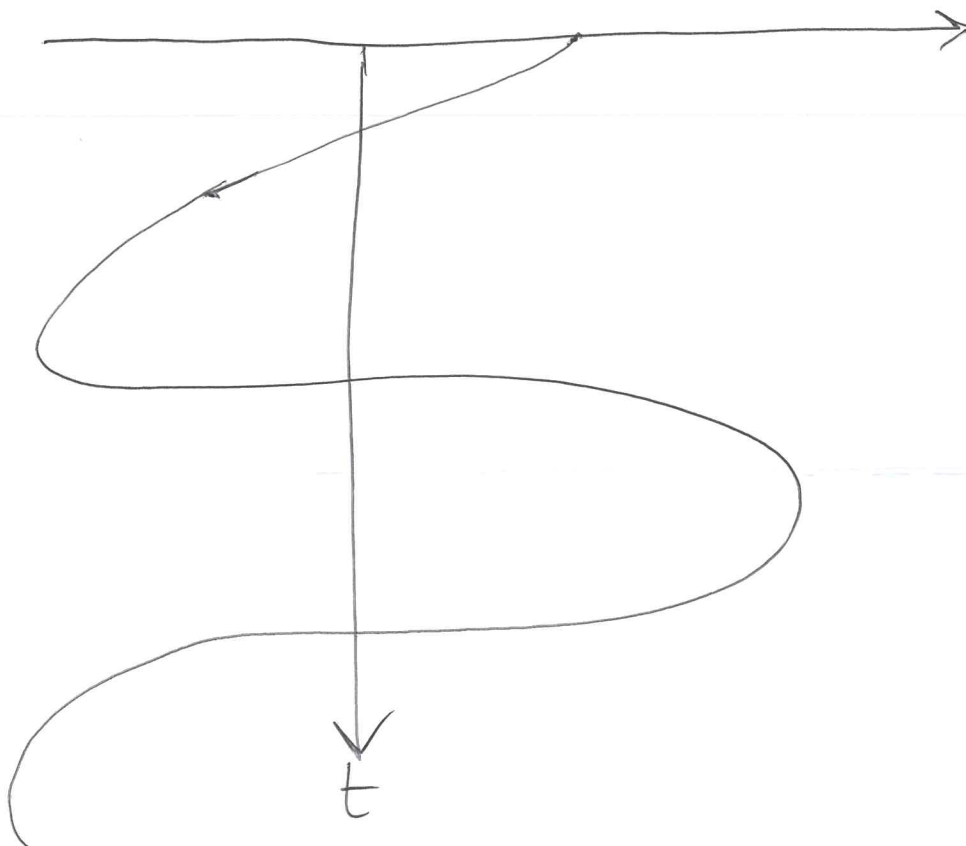
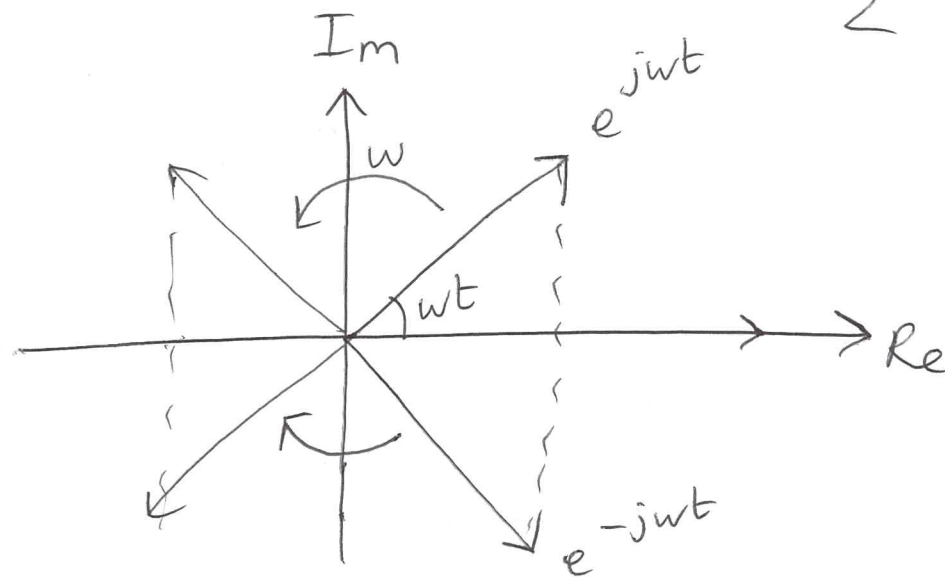
Euler's formula: $\cos(\omega t) = \frac{e^{j\omega t} + e^{-j\omega t}}{2}$



$$v(t) = v_0 \cos(\omega t + \phi)$$

$$v(t) = \operatorname{Re} \{ V e^{j(\omega t + \phi)} \}$$



$e^{jx} = \cos x + j \sin x$

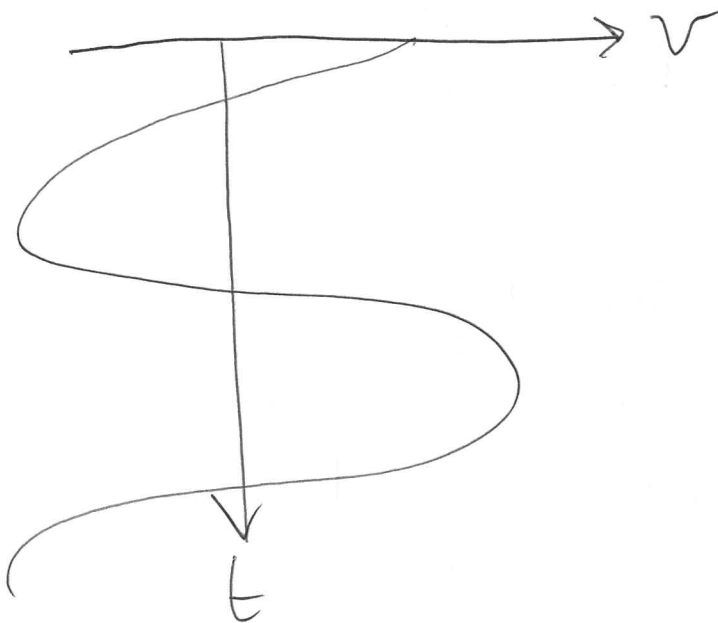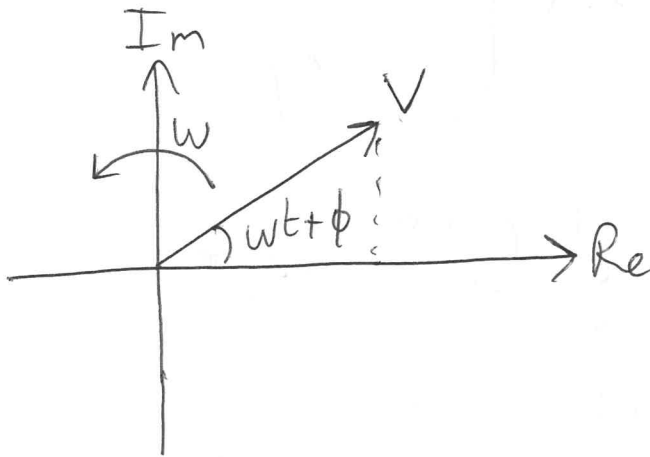

$$\frac{dv(t)}{dt} = \operatorname{Re} \left\{ \frac{d}{dt} V e^{j(\omega t + \phi)} \right\}$$

$$= j\omega \operatorname{Re} \{ V e^{j(\omega t + \phi)} \}$$

$$\therefore \frac{dV}{dt} = j\omega V$$

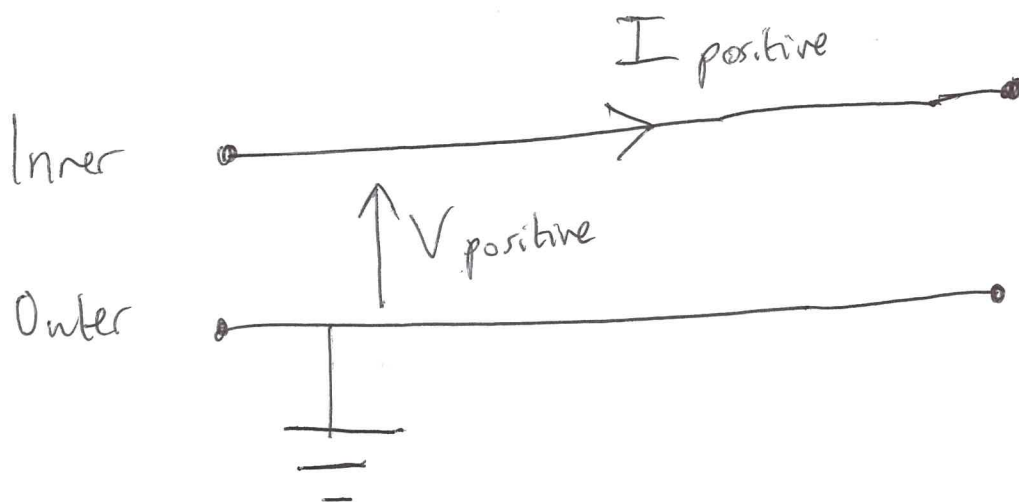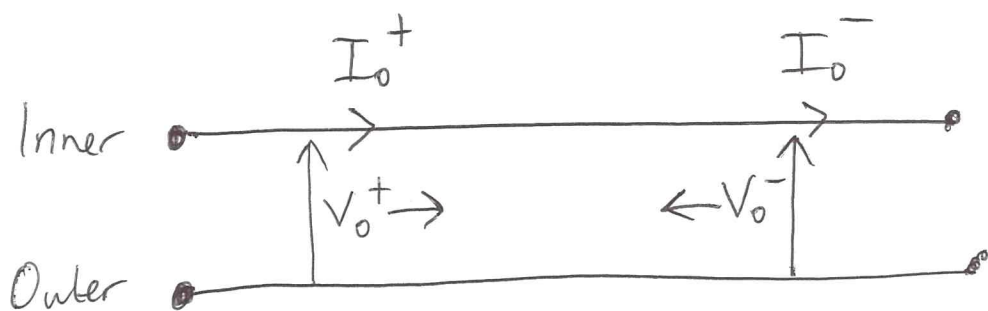

$$\frac{d^2 V(z)}{dz^2} = \gamma^2 V(z)$$

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$\frac{dV(z)}{dz} = -V_0^+ \gamma e^{-\gamma z} + V_0^- \gamma e^{+\gamma z}$$

$$\begin{aligned} \frac{d^2 V(z)}{dz^2} &= \gamma^2 V_0^+ e^{-\gamma z} + \gamma^2 V_0^- e^{+\gamma z} \\ &= \gamma^2 V(z) \end{aligned}$$