


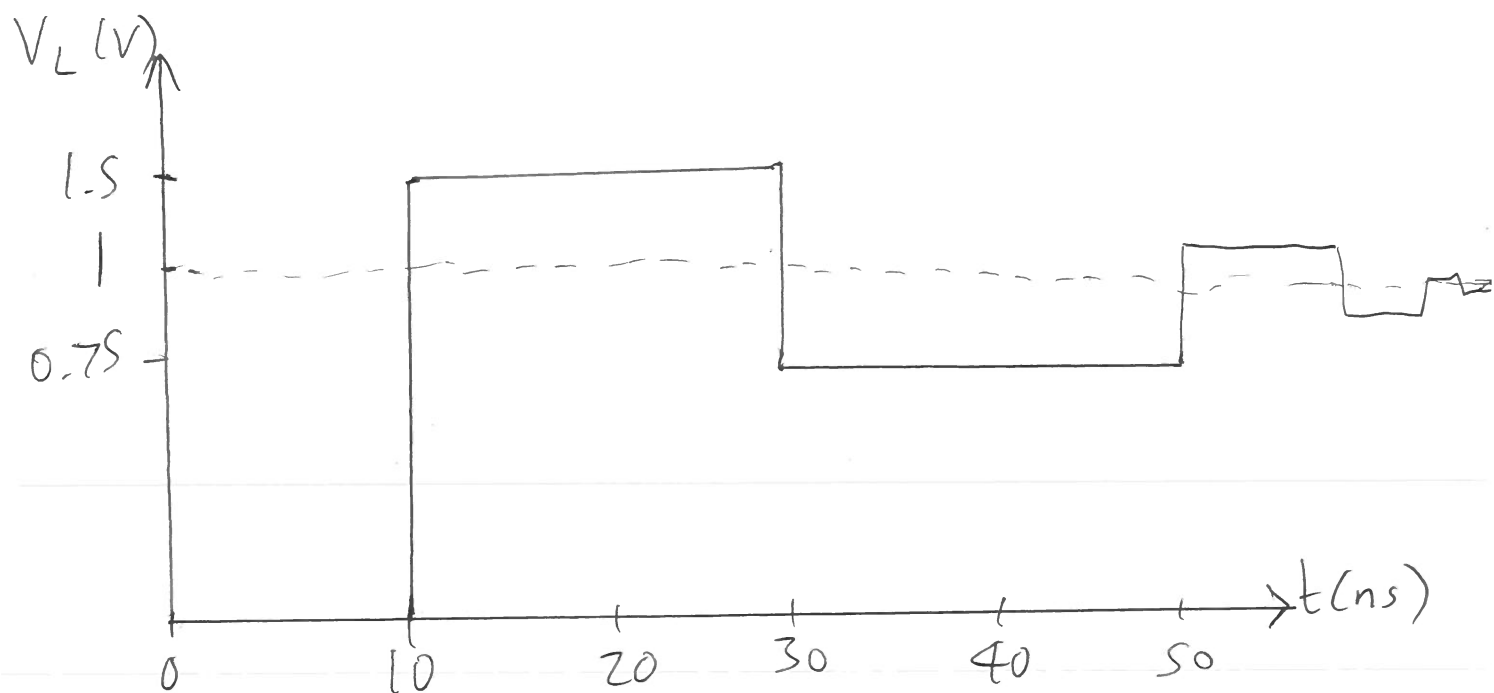
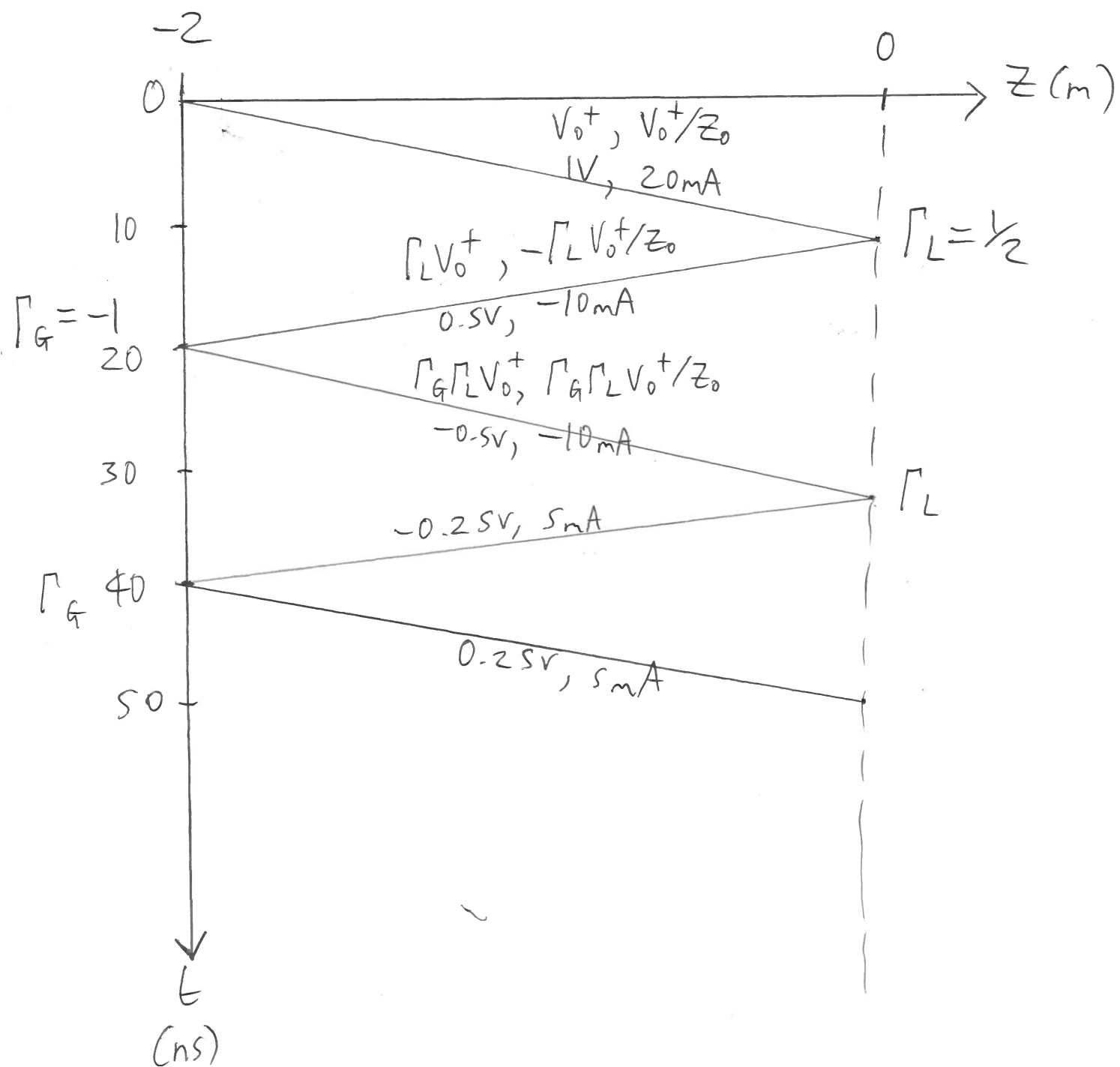


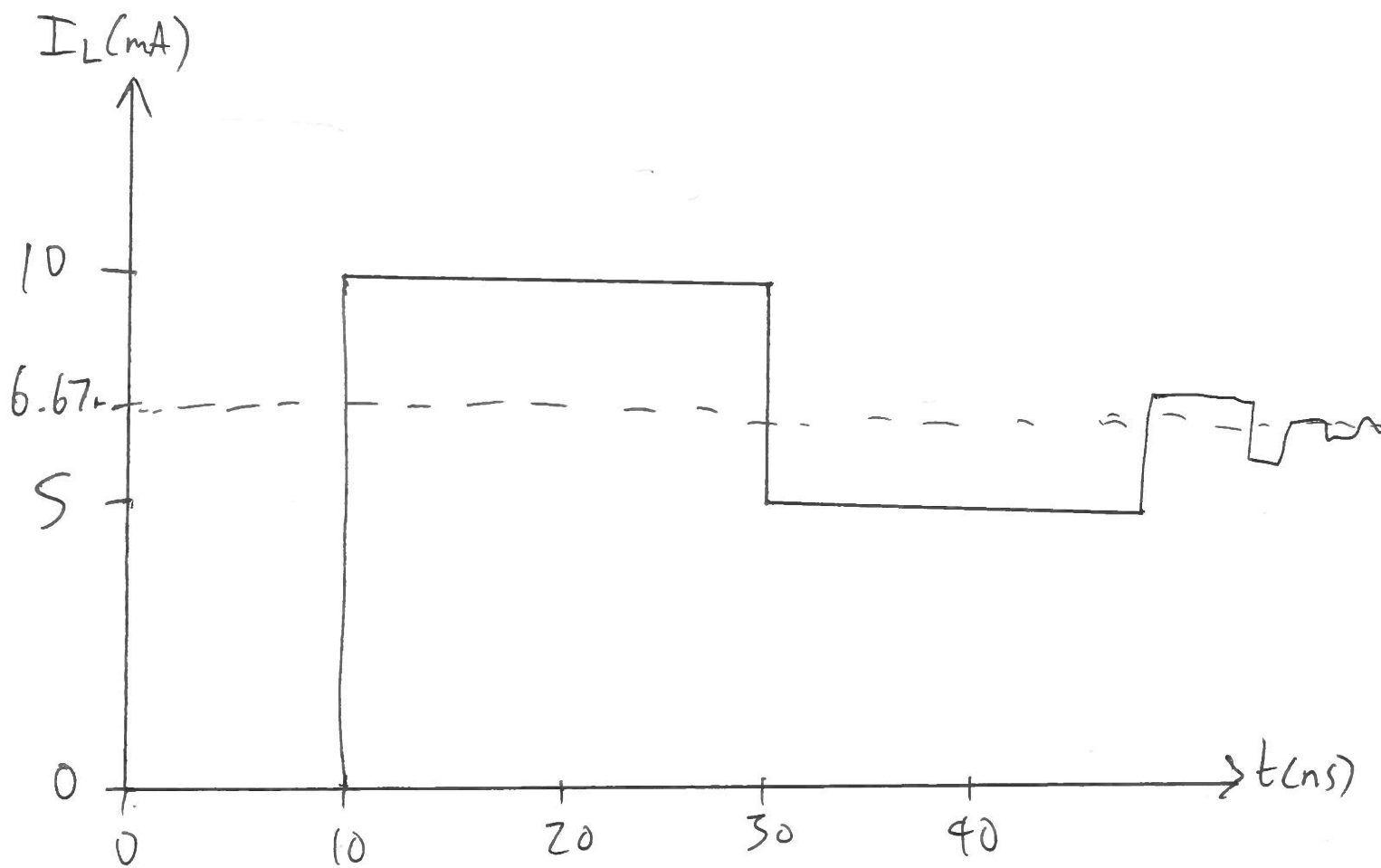

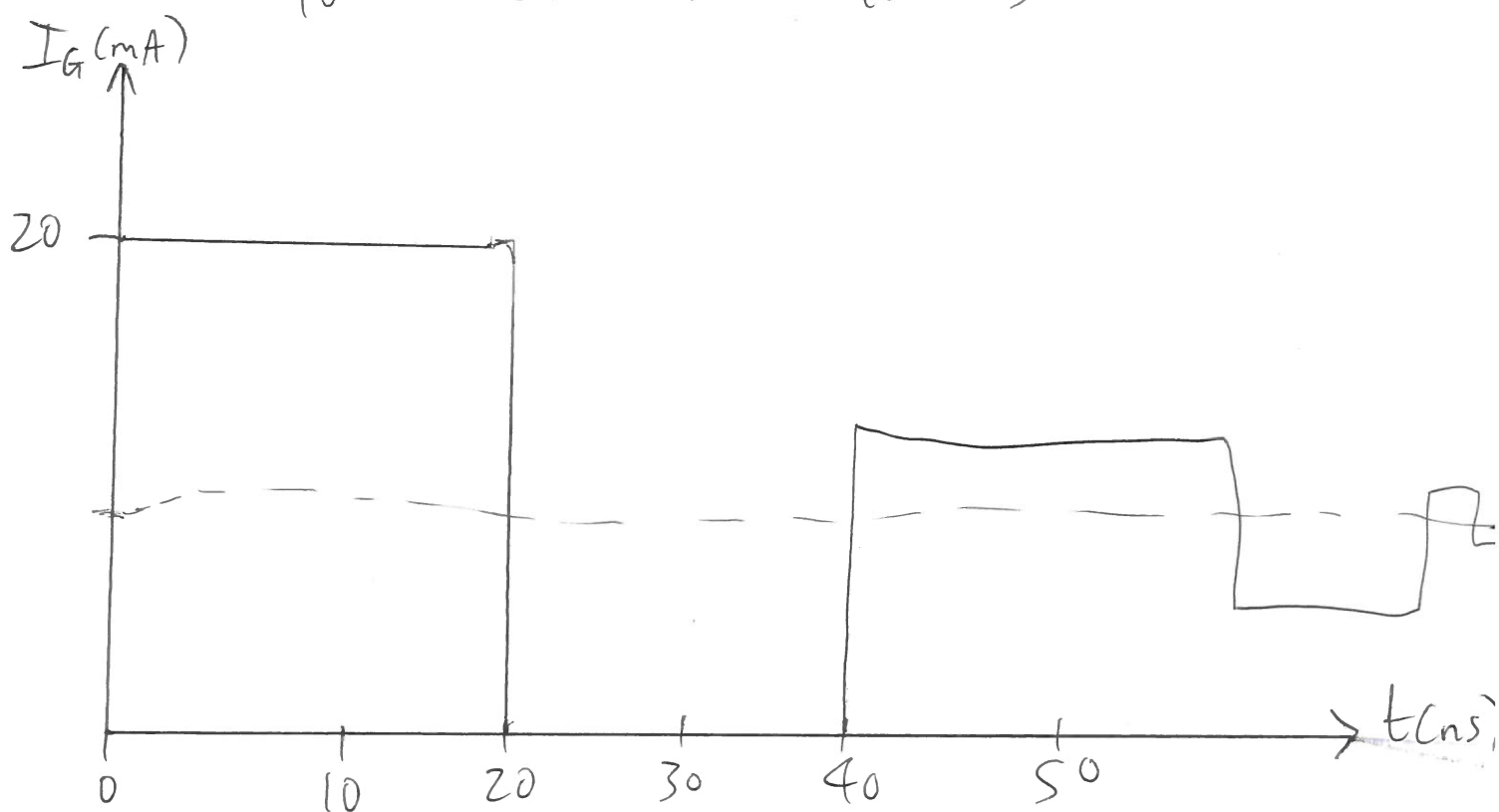

$$I_L(t \rightarrow \infty) = \frac{1V}{150\Omega} = 6.67\text{mA}$$

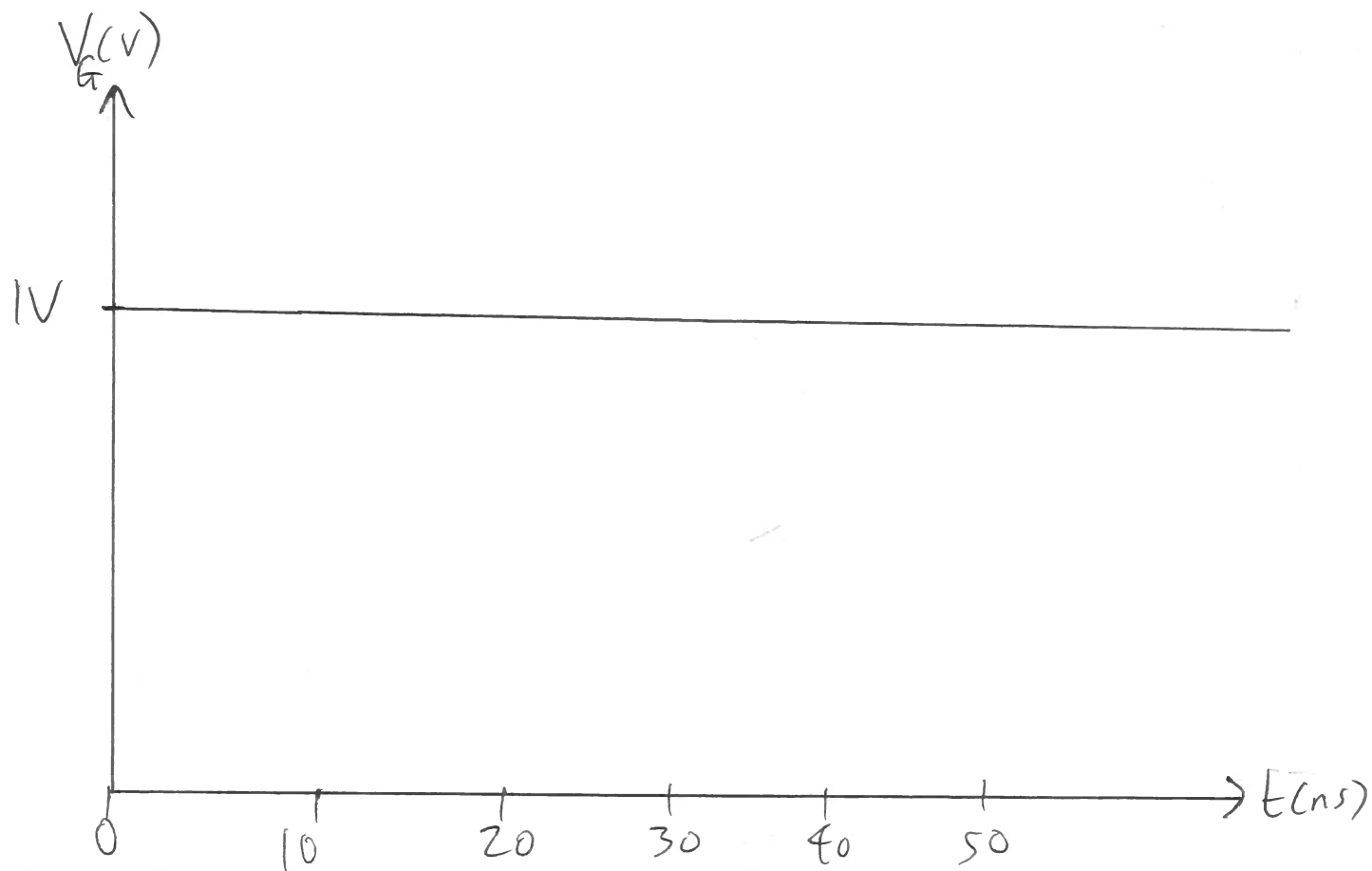
$$V = IR \Rightarrow R_L = \frac{V_L}{I_L} = 150\Omega$$



$$t = \infty : I_G \rightarrow I_L = 6.67 \text{ mA}$$



Time-domain reflectometry

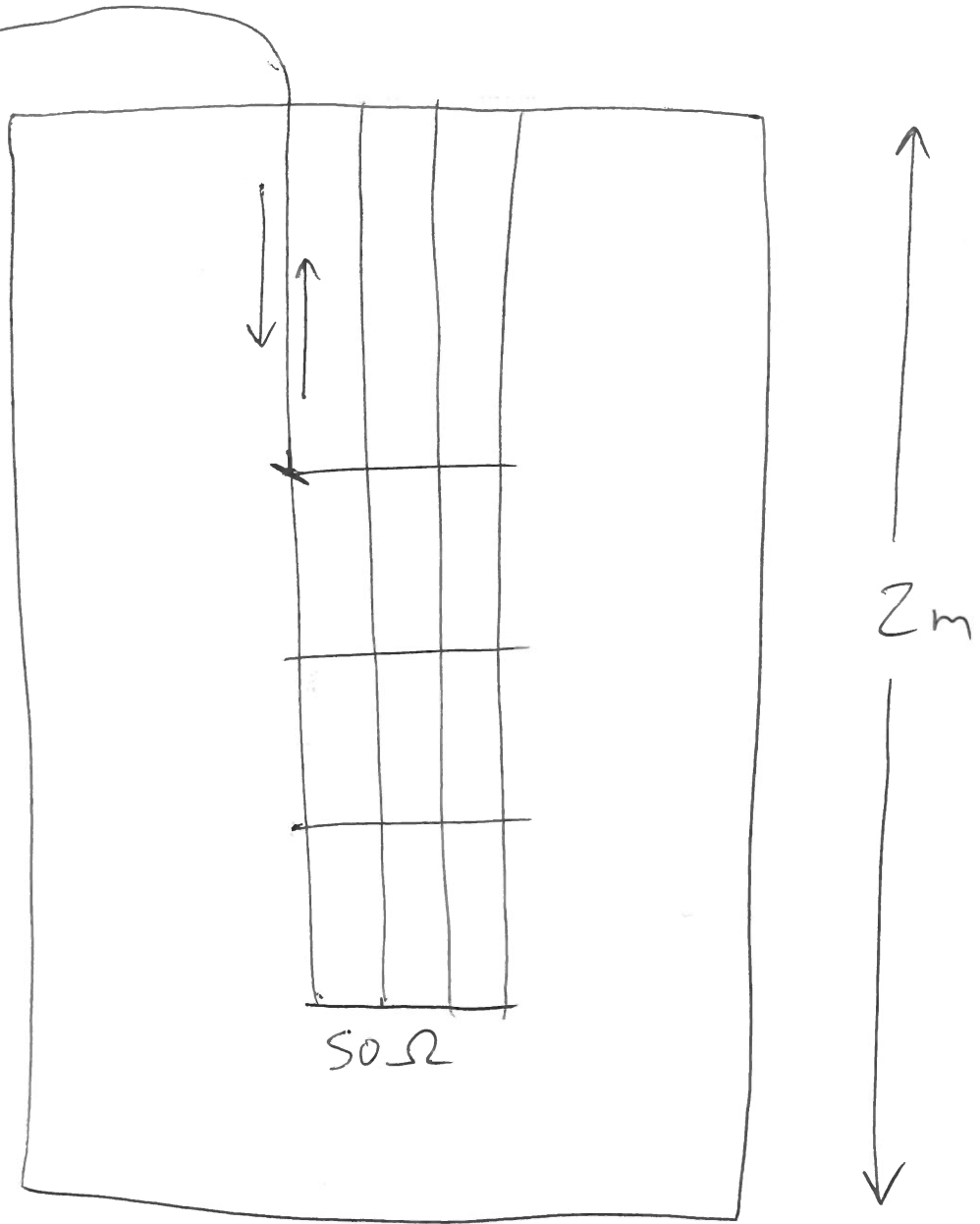

$$d = v_p t = 2 \times 10^8 \times 5 \times 10^{-9} = 1 \text{ m}$$


1) Lumped impedance:



$$Z = \frac{V}{I}$$

Can measure with
DC multimeter


2) Characteristic impedance:

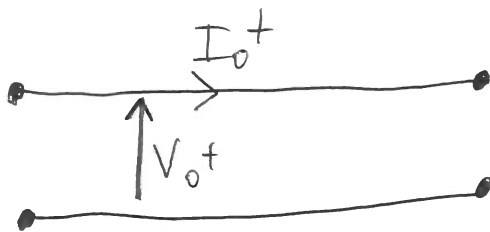

$$Z_0 = \frac{V_0^+}{I_0^+}$$

Can't measure
with multimeter

3) Input impedance:

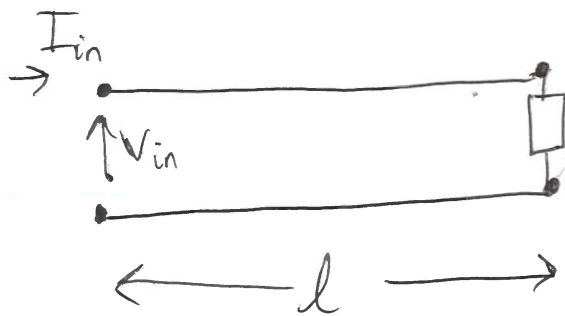

$$Z_{in} = \frac{V_{in}}{I_{in}}$$

Can measure with
AC multimeter

